

Solution


EE101 Winter 2019 Quiz #1

January 15, 2019

Name _____


Student ID _____

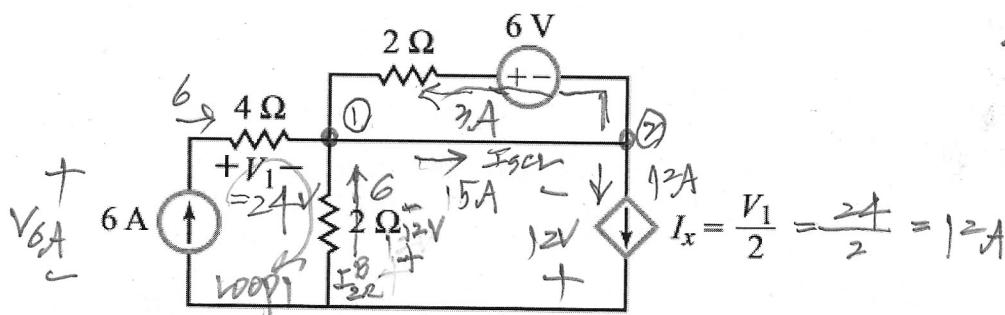Problem (10 points) For the circuit below, (1) find the voltage across the 6A current source with an appropriate polarity. (2) Find the total power generated in the circuit.



KCL at ②
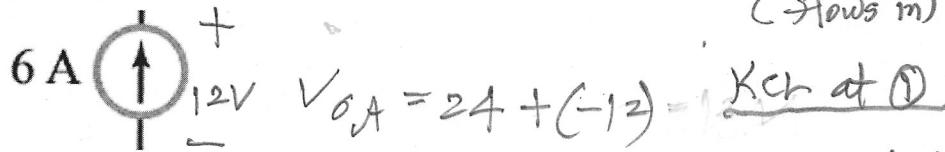
$$\begin{aligned} \bullet V_1 &= 6A \times 4\Omega = 24V \\ \bullet I_X &= \frac{V_1}{2} = 12A \\ \bullet I_{short\ circuit\ line} &= ? \\ 3A + 12A + I_{short\ circuit\ line} &= 0 \\ \Rightarrow I_{short\ circuit\ line} &= -15A \\ (\text{flows in}) \end{aligned}$$



Answer (1) (6 points)

Voltage = 12 [V]

Mark the Polarity to the source figure with + and - signs.

$$\begin{aligned} 6A + 3A + \frac{I_B^B}{2\Omega} - 15A &= 0 \\ I_{2\Omega}^B &= 6A \\ \text{Thus } V_{2\Omega}^B &= 12V \end{aligned}$$

KVL Loop 1:

$$-V_{6A} + 24V - 12V = 0$$

$$\Rightarrow V_{6A} = 12V$$

Answer (2) (4 points)

Total power generated in the circuit = 234 [W].

$$P_{6A} = -6 \times 12 = -72W$$

$$P_{IX} = -12 \times 12 = -144W$$

$$P_{6V} = -3 \times 6 = -18W$$

$$\underline{\underline{-234W}}$$

Power consumed

$$P_{4\Omega} = 6^2 \cdot 4\Omega = 36 \times 4 = 144W$$

$$P_{2\Omega} = 3^2 \cdot 2\Omega = 18W$$

$$P_{2\Omega}^B = 6^2 \cdot 2 = 72W$$

Sum 234W

Total sum = 0 (conservation of power)