

EE 101 Lecture 11-12, Feb 14, 2019  
 Quiz 6 on Feb 19 based on HW 6.

Topics covered so far

Ohm's Law, KCL & KVL  
 equivalent circuits, Norton's & Thevenin's  
 Nodal analysis, Mesh analysis  
 BJT circuits, Op Amp circuits

↓  
 Mos circuits

**RC & RL circuits**

HW # 6 (for Quiz 6)

- |              |          |
|--------------|----------|
| [1] Prob 5-1 | [6] 5-17 |
| [2] 5-3      | [7] 5-18 |
| [3] 5-4      | [8] 5-19 |
| [4] 5-15     |          |
| [5] 5-16     |          |

[Prob] Express  $v_o$  in terms of  $v_1$  &  $v_2$


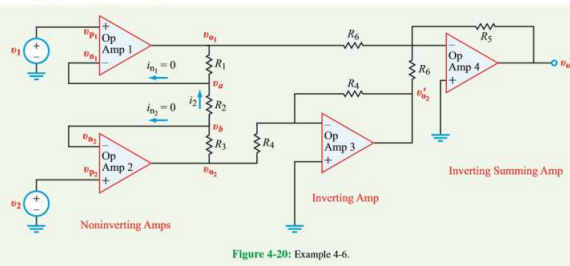


Figure 4-20: Example 4-6.

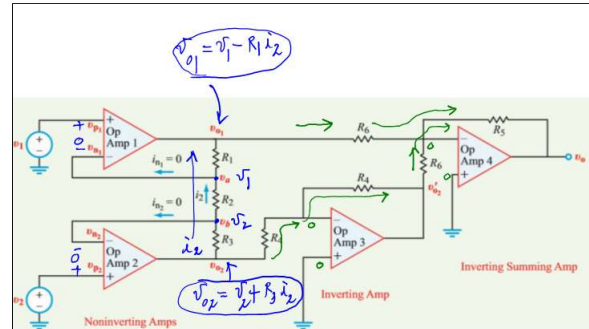

Since  $i_{n1} = i_{n2} = 0$  (op-amp current constraint),

$$i_2 = \frac{v_b - v_a}{R_2} = \frac{v_2 - v_1}{R_2},$$

and

$$v_{o2} - v_{o1} = i_2(R_1 + R_2 + R_3) = \left(\frac{R_1 + R_2 + R_3}{R_2}\right)(v_2 - v_1). \quad (4.50)$$

Op amp 3 is a standard inverting amplifier, so we can use Table 4-3(c) to obtain

$$v_{o3} = -\left(\frac{R_4}{R_3}\right)v_{o2} = -v_{o2}.$$

Op amp 4 is an inverting summing amplifier (Table 4-3(c)) with output

$$\begin{aligned} v_o &= -\frac{R_5}{R_6}(v_{o1} + v_{o3}) \\ &= \frac{R_5}{R_6}(v_{o1} - v_{o2}) \\ &= \frac{R_5}{R_6}(v_{o2} - v_{o1}) = R_5 \left(\frac{R_1 + R_2 + R_3}{R_6 R_2}\right)(v_2 - v_1). \end{aligned} \quad (4.51)$$

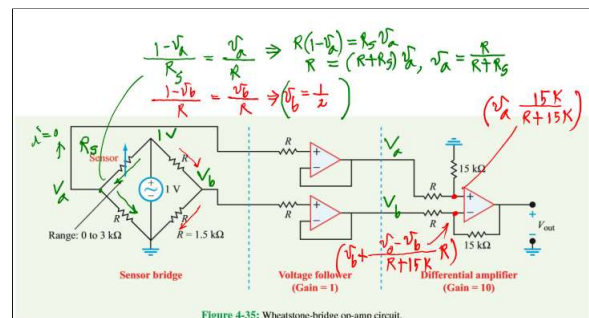
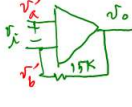


Figure 4-35: Wheatstone-bridge op-amp circuit.

$$\begin{aligned} v_s &= v_3 - v_0 \\ v_s &= A v_x = A(v_3 - v_0) \\ (1+A)v_0 &= A v_s \\ \frac{v_0}{v_s} &= \frac{A}{1+A} \\ \frac{v_0}{v_s} &\rightarrow 1 \end{aligned}$$

$$A \left[ \frac{15K}{R+15K} v_a - \left( v_b + \frac{v_a - v_b}{R+15K} R \right) \right] = v_o$$


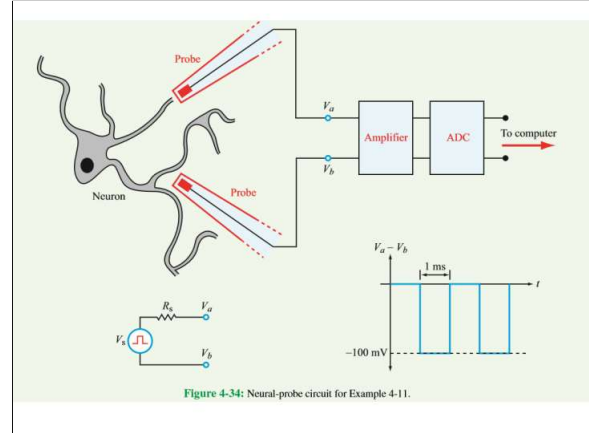
$$A \left[ \frac{15K}{R+15K} v_a - \left( - \frac{R}{R+15K} \right) v_b \right] = \left[ 1 + \frac{AR}{R+15K} \right] v_o$$

$$A \frac{15K}{R+15K} [v_a - v_b] - \left( 1 + A \frac{R}{R+15K} \right) v_o$$


As  $A \rightarrow \infty$

$$v_o = \frac{15K}{R} (v_a - v_b)$$

where  $v_b = \frac{1}{z}$ ,  $v_a = \frac{R}{R+R_S} \times 1$   
 when  $R_S = R$  then  $v_a = \frac{1}{z} + v_a - v_b = 0 \Rightarrow v_o = 0$


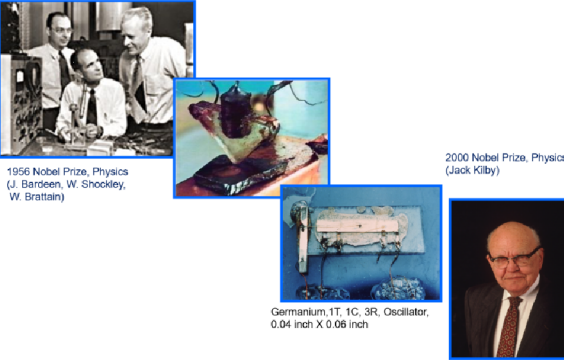
### Transistor Invention (1948) to Integrated Circuit (1958)




1956 Nobel Prize, Physics (J. Bardeen, W. Shockley, W. Brattain)

2000 Nobel Prize, Physics (Jack Kilby)


Germanium 1T, 1C, 3R, Oscillator, 0.04 inch X 0.06 inch

### First Successful Operation of MOS Transistor


Dawon Kahng (May 4, 1931- May 13, 1992)

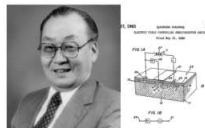

- SNU (BS), Ohio State Univ. (Ph.D. 1959)
- Dr. Kahng, with M. Atalla, fabricated a MOSFET using a gate insulator formed from high quality SiO<sub>2</sub> grown by a new high-pressure steam oxidation process at Bell Labs (1960)
- First successful demonstration of MOSFET was a major milestone in semiconductor technology
- Invented in 1967 a field effect memory, the first nonvolatile silicon memory (floating gate memory)
- Became Founding President of NEC, Princeton, NJ in 1988




Simon Sze

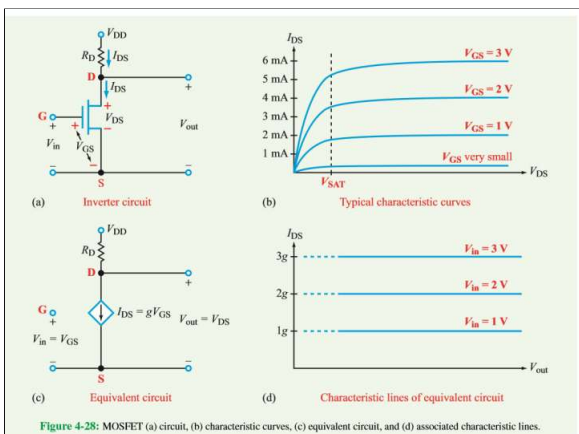
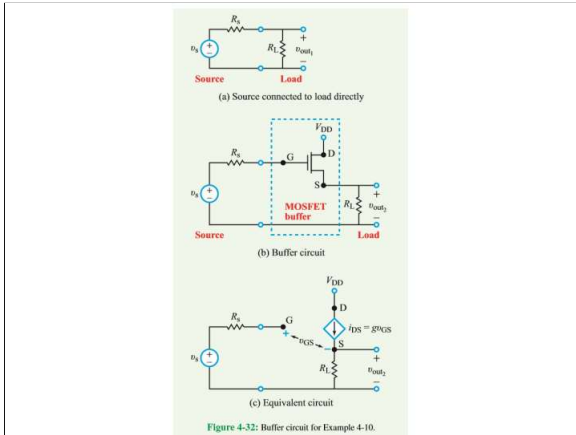
### 4-11 The MOSFET as a Voltage-Controlled Current Source

In earlier sections, we demonstrated how op amps can be used to build buffers and amplifiers. We now examine how to realize the same outcome using MOSFETs. The simplest model of a MOSFET, which stands for *metal-oxide semiconductor field-effect transistor*, is shown in Fig. 4-27(a). The vast majority of commercial computer processors are built with MOSFETs; as mentioned in Technology Brief 1 on nanotechnology, a 2010 Intel Core processor contains over 1 billion independent MOSFETs. A MOSFET has three terminals: the *gate* (G), the *source* (S), and the *drain* (D). Actually, it has a fourth terminal, namely its body (B), but we will ignore it for now because for many applications it is simply connected to the ground terminal. The circuit symbol for the MOSFET may look somewhat unusual, but it is actually a stylized depiction of the physical cross section of a real MOSFET. In a real MOSFET, the gate



**(b) With MOSFET Buffer**

For the circuit in Fig. 4-32(c), in which the MOSFET has been replaced with its equivalent circuit, KVL gives

$$-v_s + v_{GS} + v_{out2} = 0.$$

Also,

$$v_{out2} = I_{DS} R_L = g R_L v_{GS} = g R_L (v_s - v_{out2})$$

Simultaneous solution of the two equations gives

$$\Rightarrow v_{out2} = \left( \frac{g R_L}{1 + g R_L} \right) v_s.$$



With  $g = 10 \text{ A/V}$  and in order for  $v_{out2}$  to be no less than  $0.99 v_s$ , it is necessary that

$$R_L \geq 9.9 \Omega,$$



which is three orders of magnitude smaller than the requirement for the unbuffered circuit.



**Section 4-11: MOSFET**

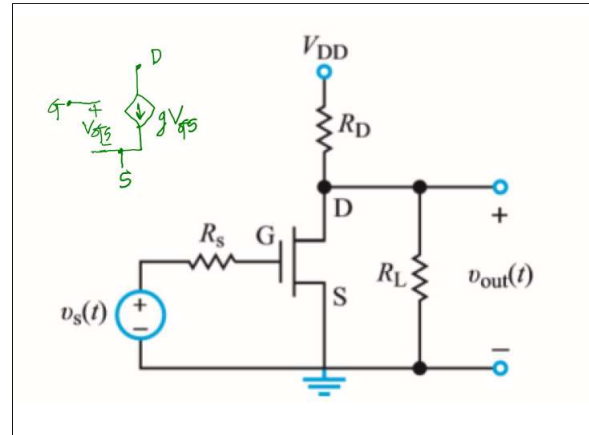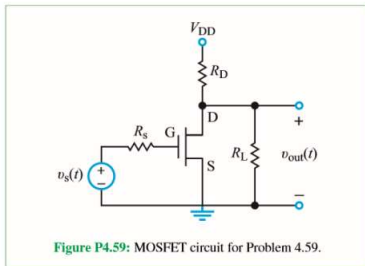4.59 In Example 4-9, we analyzed a common-source amplifier without a load resistance. Consider the amplifier in Fig. P4.59; it is identical to the circuit in Fig. 4-31, except that we have added a load resistor  $R_L$ . Obtain an expression for  $v_{out}$  as a function of  $v_s$ .



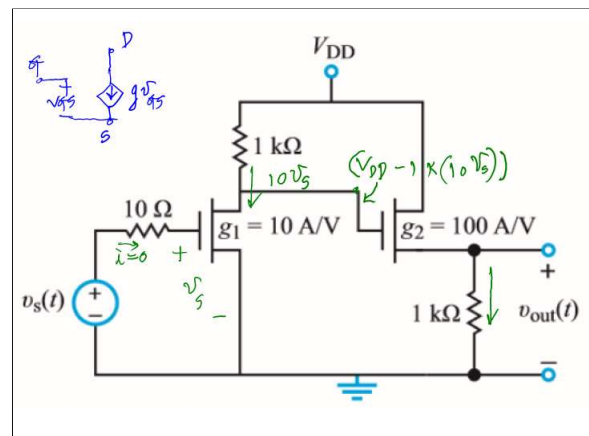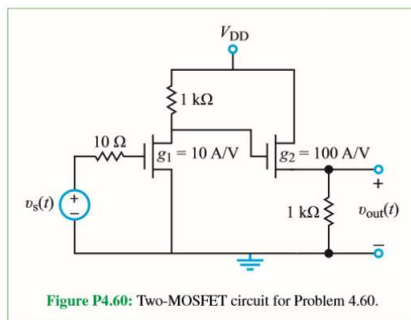\*4.60 Determine  $v_{out}(t)$  as a function of  $v_s(t)$  for the circuit in Fig. P4.60. Assume  $V_{DD} = 2.5 \text{ V}$ .



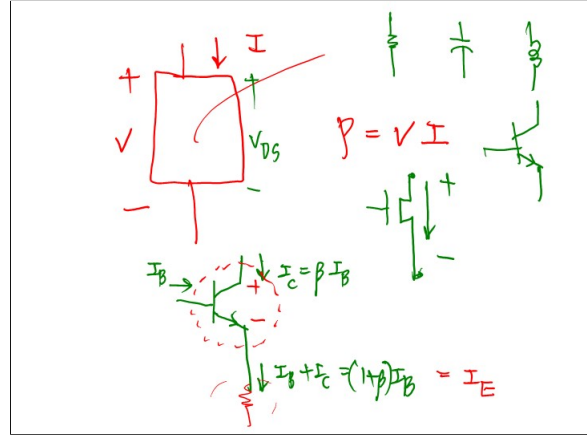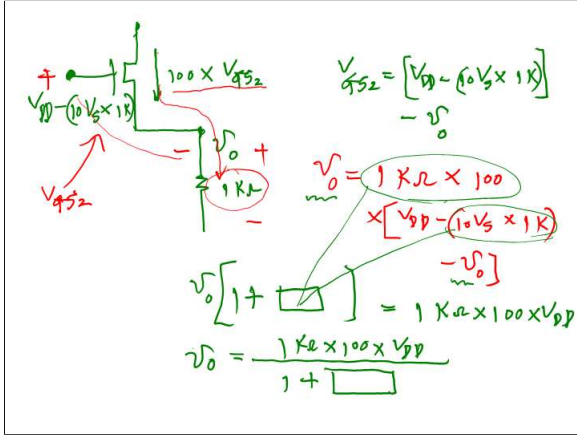

## RC and RL First-Order Circuits

**Contents**

- Overview, 249
- 5-1 Nonperiodic Waveforms, 250
- 5-2 Capacitors, 258
- 5-3 Supercapacitors, 265
- 5-4 Inductors, 269
- 5-4 Response of the RC Circuit, 275
- 5-5 Response of the RL Circuit, 287
- 5-6 Hard Disk Drives (HDDs), 293
- 5-6 RC Op-Amp Circuits, 295
- 5-7 Capacitive Sensors, 301
- 5-7 Application Note: Parasitic Capacitance and Computer Processing Speed, 305
- 5-8 Analyzing Circuit Response with Multisim, 310
- Summary, 313
- Problems, 314

**Objectives**

Learn to:

- Use mathematical functions to describe several types of nonperiodic waveforms.
- Define the electrical properties of a capacitor, including the  $i-v$  relationship and energy equation.
- Combine multiple capacitors when connected in series or in parallel.
- Define the electrical properties of an inductor, including the  $i-v$  relationship and energy equation.
- Combine multiple inductors when connected in series or in parallel.

Capacitors (C) and inductors (L) are **energy storage devices**, in contrast with resistors, which are energy dissipation devices. This chapter examines the behavior of RC and RL circuits, to be followed in Chapter 6 with an examination of RLC circuits.

- Analyze the transient responses of RC and RL circuits.
- Design RC op-amp circuits to perform differentiation and integration and related operations.
- Apply Multisim to analyze RC and RL circuits.

Capacitor  $dq = C dv$   
Linear case  $q = C v$

Resistor $dv = R di$	Capacitor $dq = C dv$
Inductor $dv = L di$	Memristor $dq = M di$

**Memristor as 4th fundamental device**

**5-2 Capacitors**

When separated by an insulating medium, any two conducting bodies (regardless of their shapes and sizes) form a capacitor. A capacitor can store electric charge  $q$ .

The **parallel-plate capacitor** shown in Fig. 5-11 represents a simple configuration in which two identical conducting plates (each of area  $A$ ) are separated by a distance  $d$  consisting of an insulating (dielectric) material of electrical permittivity  $\epsilon$ . The insulating (dielectric) material is usually referred to that of free space, namely  $\epsilon_0 = 8.85 \times 10^{-12}$  farads/m (F/m). Hence, the **relative permittivity** of a material is defined as

$$\epsilon_r = \frac{\epsilon}{\epsilon_0} \quad (5.15)$$

When a dielectric material is subjected to an electric field, its atoms become partially polarized; i.e., the atoms are rearranged into positive and negative dipoles. The electric field  $E$  induced by the other between the conducting plates is the result of the voltage  $v$  applied across the plates. The electrical susceptibility  $\chi_e$  of a material is a measure of how susceptible that material is to electrical polarization. The permittivity  $\epsilon$  and susceptibility  $\chi_e$  are related by

$$\epsilon = \epsilon_0(1 + \chi_e) \quad (5.16)$$

In view of Eq. (5.15), the relative permittivity  $\epsilon_r$  is given by

$$\epsilon_r = \frac{\epsilon}{\epsilon_0} = 1 + \chi_e \quad (5.17)$$

**Table 5-2: Relative electrical permittivity of common insulators.**  $\epsilon_r = \epsilon/\epsilon_0$  and  $\epsilon_0 = 8.85 \times 10^{-12}$  F/m.

Material	Relative Permittivity $\epsilon_r$
Air (sea level)	1.0006
Bakelite	2.1
Barium titanate	24
Paper	2.4
Glass	4.5–10
Quartz	3.8–5
Polystyrene	2.6
Alumina	9.6–10
Porcelain	5.7

$\epsilon_0 = 8.854 \times 10^{-12} \text{ [F/m]}$

$\epsilon_r$  of 3.9

$\epsilon = 3.9 \times 8.854 \times 10^{-12} \text{ [F/m]}$

$= 35.4 \times 10^{-12} \text{ [F/m]}$

$= 35.4 \text{ pF/m}$

For the parallel-plate capacitor, combining Eqs. (5.11) and (5.10) (with  $v = q/C$ ), upon inserting the expression for  $E$  in Eq. (5.20), we have

$$C = \frac{\epsilon A}{d} \quad (\text{parallel-plate capacitor}) \quad (5.21)$$

Even though the expression given by Eq. (5.21) is specific to the parallel-plate capacitor, the general form of the expression holds true for other geometrical configurations as well. In general, the capacitance  $C$  of any two-conductor system increases with the area of the conducting surfaces, decreases with the separation between them, and is directly proportional to  $\epsilon$  of the insulating material. For example, the capacitance of a cylindrical capacitor consisting of two concentric conducting cylinders of radii  $a$  and  $b$  (Fig. 5-12(a)) and separated by a dielectric material of permittivity  $\epsilon$  is given by

$$C = \frac{2\pi\epsilon l}{\ln(b/a)} \quad (\text{cylindrical capacitor}) \quad (5.22)$$

where  $l$  is the length of the capacitor and  $\ln(b/a)$  is the natural logarithm of  $b/a$ . The spacing between the cylinders is  $(b-a)$  (conducting this spacing, which holding constant, requires reducing the ratio  $b/a$ ), which reduces the value of  $\ln(b/a)$ , thereby increasing the magnitude of  $C$ .

The **micro capacitor** shown in Fig. 5-12(b) consists of a stack of conducting plates, separated by sheets of mica dielectrics. The **plastic-film capacitor** in Fig. 5-12(c) is constructed by rolling the conducting film capacitor in a plastic layer into a spiral-like configuration. Small capacitors used in microprocessors typically have capacitors in the picofarad ( $10^{-12}$  F) to nanofarad ( $10^{-9}$  F) range. Large capacitors used in power-transmission applications may have capacitors in the range of millifarads ( $10^{-3}$  F). Using thin-film polymers for the dielectric, a new type of capacitor (sometimes called a **polymer capacitor**) was developed in the 1990s with the express goal of significantly increasing the amount of charge that the conductors can hold at a specified voltage level. Such capacitors have capacitance values that are several orders of magnitude greater than conventional capacitors of comparable size. The new fabrication techniques have not only expanded the versatility of capacitors in electronic circuits, but they have also introduced the use of supercapacitors as energy-storage devices in many electronic applications (see Technology First 12: Supercapacitors).

**5-2.1 Electrical Properties of Capacitors**

According to Eq. (5.20),  $q = C \cdot v$ . Application of the standard definition for current (Eq. 1-1) provides the expression for the current through a capacitor as

$$i = \frac{dq}{dt} = C \frac{dv}{dt} \quad (5.23)$$

where the direction of  $i$  and the polarity of  $v$  are defined in accordance with the passive sign convention (Fig. 5-3).

$$C = \frac{q}{v} \quad i = C \frac{dv}{dt}$$

Figure 5-13: Passive sign convention for capacitor: if current  $i$  is entering the (+) voltage terminal across the capacitor, then power is getting transferred into the capacitor. Conversely, if  $i$  is leaving the (+) terminal, then power is getting released from the capacitor.

The  $i$ - $v$  relationship expressed by Eq. (5.23) conveys a very important condition, namely:


► The voltage across a capacitor cannot change instantaneously, but the current can. ◀

This assertion is supported by the observation that if  $v$  were to change values in zero time,  $dv/dt$  would be infinite, as a result of which the current  $i$  would be also infinite. Since  $i$  cannot be infinite,  $v$  cannot change instantaneously.

Another attribute of Eq. (5.23) relates to the behavior of a capacitor under dc conditions (constant voltage across it). Since  $dv/dt = 0$  for a dc voltage, it follows that  $i = 0$ . Such a behavior is characteristic of an open circuit, through which no current flows even when a non-zero voltage exists across it. Thus:

► Under dc conditions, a capacitor behaves like an open circuit. ◀

### Voltage Division

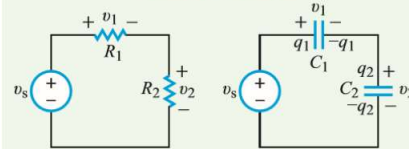

$$(a) \quad v_1 = \left( \frac{R_1}{R_1 + R_2} \right) v_s \quad v_2 = \left( \frac{R_2}{R_1 + R_2} \right) v_s$$

$$(b) \quad v_1 = \left( \frac{C_2}{C_1 + C_2} \right) v_s \quad v_2 = \left( \frac{C_1}{C_1 + C_2} \right) v_s$$

Figure 5-19: Voltage-division rules for (a) in-series resistors and (b) in-series capacitors.

$$i \downarrow \begin{array}{c} + \\ | \\ C \\ | \\ - \end{array} v$$

$$q(t) = \int_{-\infty}^t i(t) dt = \int_{-\infty}^0 i(t) dt + \int_0^t i(t) dt = q(0) + \int_0^t i(t) dt$$

$$\frac{dq(t)}{dt} = \frac{dq(0)}{dt} + i(t)$$

$$\frac{d}{dt}(Cv(t)) = C \frac{dv(t)}{dt} = i(t)$$

$$p(t) = v(t) i(t) = v(t) C \frac{dv(t)}{dt}$$

$$E(t) = \int_{-\infty}^t p(t) dt = C \int_{v(-\infty)}^{v(t)} v \frac{dv}{dt} dt = \frac{1}{2} C v^2(t), \quad v(-\infty) = 0$$

Derive the equivalent voltage-division equation for the series capacitors  $C_1$  and  $C_2$  in Fig. 5-19(b). Assume that the capacitors had no charge on them before they were connected to  $v_s$ .

**Solution:** From the standpoint of the source  $v_s$ , it "sees" an equivalent, single capacitor  $C$  given by the series combination of  $C_1$  and  $C_2$ , namely

$$C = \frac{C_1 C_2}{C_1 + C_2} \quad (5.44)$$

The voltage across  $C$  is  $v_s$ . The law of conservation of energy requires that the energy that would be stored in the equivalent capacitor  $C$  be equal to the sum of the energies stored in  $C_1$  and  $C_2$ . Hence, application of Eq. (5.29) gives

$$\frac{1}{2} C v_s^2 = \frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 v_2^2 \quad (5.45)$$

Upon replacing  $C$  with the expression given by Eq. (5.44) and replacing the source voltage with  $v_s = v_1 + v_2$ , we have

$$\frac{1}{2} \left( \frac{C_1 C_2}{C_1 + C_2} \right) (v_1 + v_2)^2 = \frac{1}{2} C_1 v_1^2 + \frac{1}{2} C_2 v_2^2 \quad (5.46)$$

$$v = v_1 + v_2 = \frac{q}{C_1} + \frac{q}{C_2}$$

$$v = \frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2}$$

$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_1 + C_2}{C_1 C_2}$$

$$\Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

same as conductance ( $G$ ) connection

$$i = i_1 + i_2$$

$$q = q_1 + q_2$$

$$\frac{dq}{dt} = \frac{dq_1}{dt} + \frac{dq_2}{dt}$$

$$\frac{dq}{dt} = \frac{d}{dt}(C_{eq} v)$$

$$= C_{eq} \frac{dv}{dt} = \frac{d}{dt}(C_1 v) + \frac{d}{dt}(C_2 v)$$

$$= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} = (C_1 + C_2) \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2$$

**Exercise 5-9:** Determine  $C_{eq}$  and  $v_{eq}(0)$  at terminals  $(a, b)$  for the circuit in Fig. E5.9 given that  $C_1 = 6 \mu\text{F}$ ,  $C_2 = 4 \mu\text{F}$ ,  $C_3 = 8 \mu\text{F}$ , and the initial voltages on the three capacitors are  $v_1(0) = 5 \text{ V}$  and  $v_2(0) = v_3(0) = 10 \text{ V}$ , respectively.

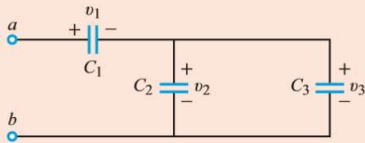



Figure E5.9

Answer:  $C_{eq} = 4 \mu\text{F}$ ,  $v_{eq}(0) = 15 \text{ V}$ . (See CAD)

$q_1(0) = 30 \mu\text{C}$   
 $v_1(0) = 5 \text{ V}$   
 $q_{23}(0) = 120 \mu\text{C}$   
 $4 \mu\text{F} + 8 \mu\text{F} = 12 \mu\text{F}$

$v_{ab}(0) = 5 \text{ V} + 10 \text{ V} = 15 \text{ V}$   
 $C_{ab} = \frac{6 \mu\text{F} (12 \mu\text{F})}{6 \mu\text{F} + 12 \mu\text{F}} = \frac{22 \mu\text{F}}{18 \mu\text{F}} = 4 \mu\text{F}$

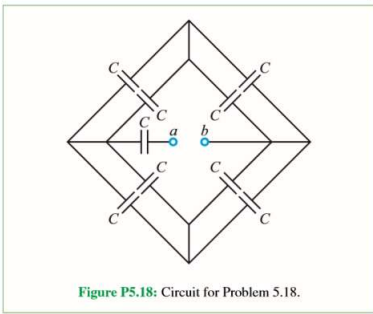
5.18 Reduce the circuit in Fig. P5.18 into a single equivalent capacitor at terminals  $(a, b)$ . Assume that all initial voltages are zero at  $t = 0$ .



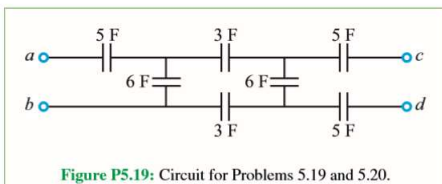5.18 Reduce the circuit in Fig. P5.18 into a single equivalent capacitor at terminals  $(a, b)$ . Assume that all initial voltages are zero at  $t = 0$ .

$C_{ab} = \frac{C \cdot 2C}{C + 2C} = \frac{2}{3} C$

\*5.19 For the circuit in Fig. P5.19, find  $C_{eq}$  at terminals  $(a, b)$ . Assume all initial voltages to be zero.



\*5.19 For the circuit in Fig. P5.19, find  $C_{eq}$  at terminals  $(a, b)$ . Assume all initial voltages to be zero.

$C_{cd} = \frac{1}{5} + \frac{1}{7.2} + \frac{1}{5} = \frac{7.2 \times 2 + 5}{36} = \frac{19.4}{36}$   
 $\frac{1}{C_{ab}} = \frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \frac{2 + 1 + 2}{6} = \frac{5}{6}$   
 $C_{ab} = \frac{6}{5} \text{ F}$

### 5-3 Inductors

Any current-carrying conductor, whether straight or coiled, forms an inductor. A current produces a magnetic field, which stores energy that can be released later in the form of another current. Also, since every wire acts like an inductor, we have small amounts of stray inductance in every circuit. Fortunately, this can be ignored except at extremely high frequencies (microwave band).

Inductors exhibit a number of useful properties, including magnetic coupling and electromagnetic induction. They are employed in microphones and loudspeakers, magnetic relays and sensors, theft detection devices, and motors and generators, and they provide wireless power transmission and data communication (albeit over relatively short distances).

► Capacitors and inductors constitute a canonical pair of devices. Whereas a capacitor can store energy through the electric field induced by the voltage imposed across its terminals, an inductor can store magnetic energy through the magnetic field induced by the current flowing through its wires. ◀

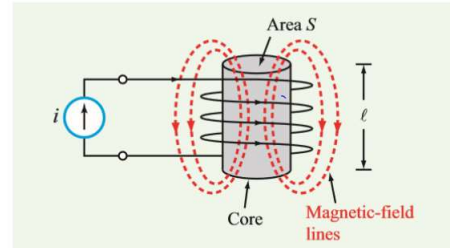


Figure 5-20: The inductance of a solenoid of length  $\ell$  and cross-sectional area  $S$  is  $L = \mu N^2 S / \ell$ , where  $N$  is the number of turns and  $\mu$  is the magnetic permeability of the core material.

$$\phi \leftrightarrow i$$

$$\phi = L i$$

$$\frac{d\phi}{dt} = L \frac{di}{dt}$$

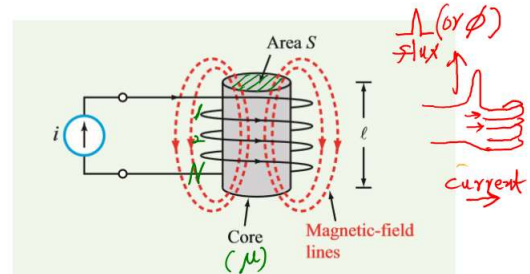


Figure 5-20: The inductance of a solenoid of length  $\ell$  and cross-sectional area  $S$  is  $L = \mu N^2 S / \ell$ , where  $N$  is the number of turns and  $\mu$  is the magnetic permeability of the core material.

#### 5-3.1 Electrical Properties

According to Faraday's law, if the magnetic-flux linkage in an inductor (or circuit) changes with time, it induces a voltage  $v$  across the inductor's terminals given by

$$v = \frac{d\Lambda}{dt} \quad (5.54)$$

*(Handwritten note:  $v = \frac{d\phi}{dt}$ )*

In view of Eq. (5.51),

$$v = \frac{d}{dt} (Li) = L \frac{di}{dt} \quad (5.55)$$

This  $i$ - $v$  relationship adheres to the passive sign convention introduced earlier for resistors and capacitors. If the direction of  $i$  is into the (+) voltage terminal of the inductor (Fig. 5-22), then the inductor is receiving power. Also, the same logic that led us earlier to the conclusion that the voltage across a capacitor cannot change instantaneously leads us now to the conclusion:

► The current through an inductor cannot change instantaneously, but the voltage can. ◀

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v dt' \quad (5.56)$$

where  $t_0$  is an initial reference point in time. The power delivered to the inductor is given by

$$p(t) = vi = Li \frac{di}{dt} \quad (5.57)$$

and as with the resistor and the capacitor, the sign of  $p$  determines whether the inductor is receiving power ( $p > 0$ ) or delivering it ( $p < 0$ ). The accumulation of power over time constitutes the storage of energy. The magnetic energy stored in an inductor is

$$w(t) = \int_{-\infty}^t p dt' = \int_{-\infty}^t \left( Li \frac{di}{dt'} \right) dt' \quad (5.58)$$



*(Handwritten note:  $= L \int i di$ )*

which yields


$$w(t) = \frac{1}{2} L i^2(t) \quad (J) \quad (5.59)$$

*(Handwritten note:  $= \frac{1}{2} Li^2(t)$ )*


same as resistor connection

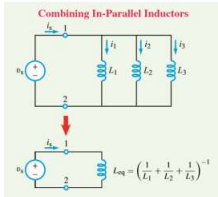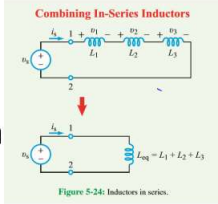

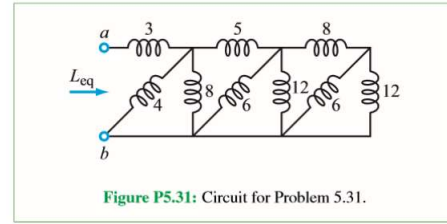
\*5.31 The values of all inductors in the circuit of Fig. P5.31 are in millihenrys. Determine  $L_{eq}$ .



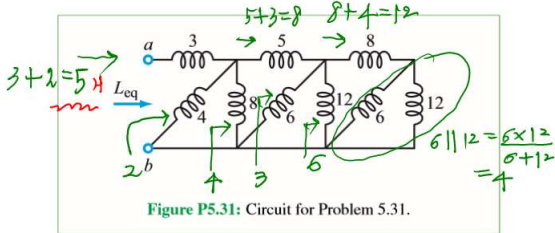
\*5.31 The values of all inductors in the circuit of Fig. P5.31 are in millihenrys. Determine  $L_{eq}$ .



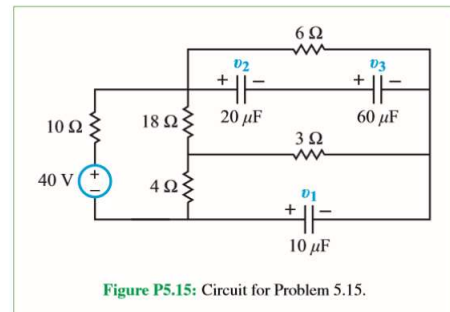
\*5.15 Determine voltages  $v_1$  to  $v_3$  in the circuit of Fig. P5.15 under dc conditions.



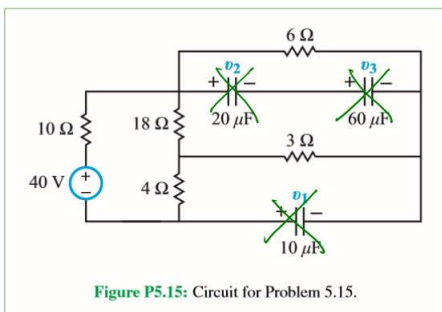\*5.15 Determine voltages  $v_1$  to  $v_3$  in the circuit of Fig. P5.15 under dc conditions.




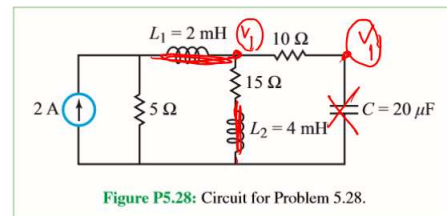5.28 For the circuit in Fig. P5.28, determine the voltage across  $C$  and the currents through  $L_1$  and  $L_2$  under dc conditions.






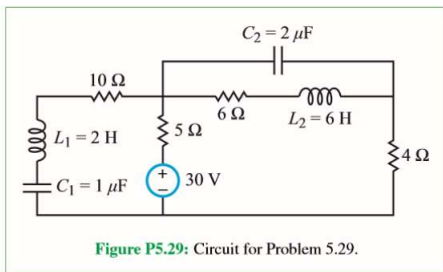\*5.29 For the circuit in Fig. P5.29, determine the voltages across  $C_1$  and  $C_2$  and the currents through  $L_1$  and  $L_2$  under dc conditions.



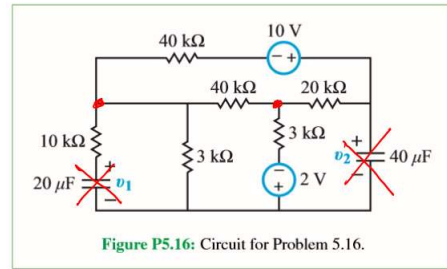5.16 Determine the voltages across the two capacitors in the circuit of Fig. P5.16 under dc conditions.



5.16 Determine the voltages across the two capacitors in the circuit of Fig. P5.16 under dc conditions.

