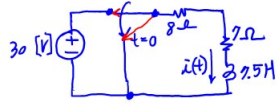



EE 101 Lecture 13, Feb 19, 2019
 Quiz 7 on Feb 26 based on HW 7.

- [1] Prob. 6.1
- [2] 6.2
- [3] 6.3
- [4] 6.4
- [5] 6.5
- [6] 6.7

[7] Find $i(t)$, $t > 0$ for the circuit below



Quiz 5 Average = 7.08, $\alpha = 2.34$

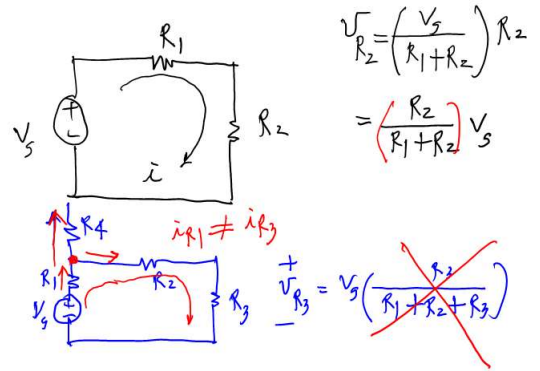

RC and RL First-Order Circuits

Contents

- Overview, 249
- 5-1 Nonperiodic Waveforms, 250
- 5-2 Capacitors, 258
- 5-3 Supercapacitors, 265
- 5-4 Inductors, 269
- 5-5 Response of the RC Circuit, 275
- 5-6 Response of the RL Circuit, 287
- 5-7 RC Op-Amp Circuits, 295
- 5-8 Hard Disk Drives (HDDs), 298
- 5-9 RC Op-Amp Circuits, 295
- 5-10 Capacitive Sensors, 301
- 5-11 Application Note: Parasitic Capacitance and Computer Processing Speed, 305
- 5-12 Analyzing Circuit Response with Multisim, 310
- Summary, 313
- Problems, 314

Objectives

Learn to:


- Use mathematical functions to describe several types of nonperiodic waveforms.
- Define the electrical properties of a capacitor, including its $i-v$ relationship and energy equation.
- Combine multiple capacitors when connected in series or in parallel.
- Define the electrical properties of an inductor, including its $i-v$ relationship and energy equation.
- Combine multiple inductances when connected in series or in parallel.



Capacitors (C) and inductors (L) are energy storage devices, in contrast with resistors, which are energy dissipation devices. This chapter examines the behavior of RC and RL circuits, to be followed in Chapter 6 with an examination of RLC circuits.

- Analyze the transient responses of RC and RL circuits.
- Design RC op-amp circuits to perform differentiation and integration and related operations.
- Apply Multisim to analyze RC and RL circuits.

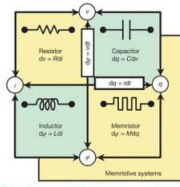Capacitor $dq = C dv$
 Linear case $q = C v$



Memristor as 4th fundamental device

	Resistor	Capacitor
Current	$dv = R di$	$dq = C dv$
Current	$dv = L di$	Memristor
		$dq = M di$
	Voltage	Voltage

Voltage Division

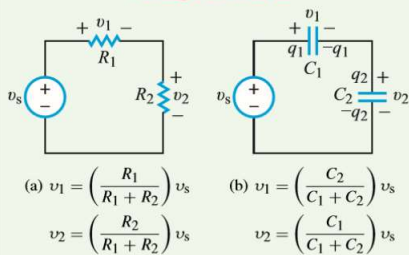


Figure 5-19: Voltage-division rules for (a) in-series resistors and (b) in-series capacitors.

same as resistor connection


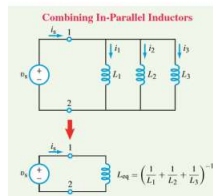
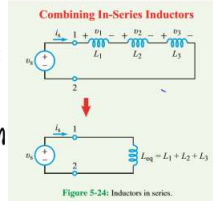
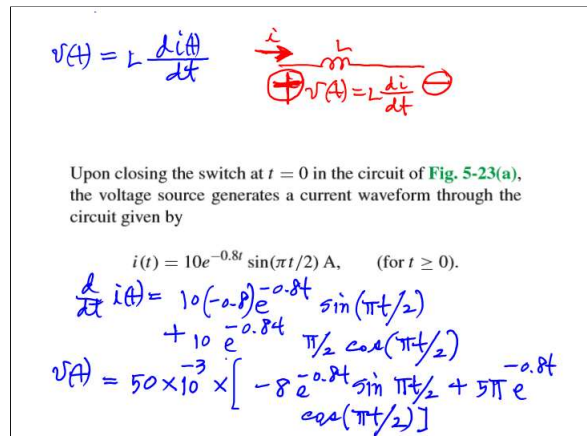
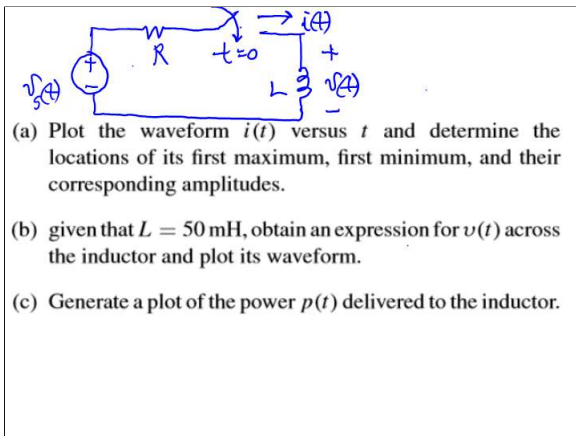
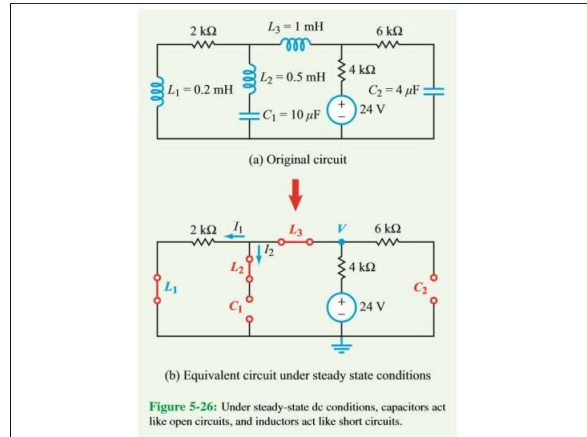
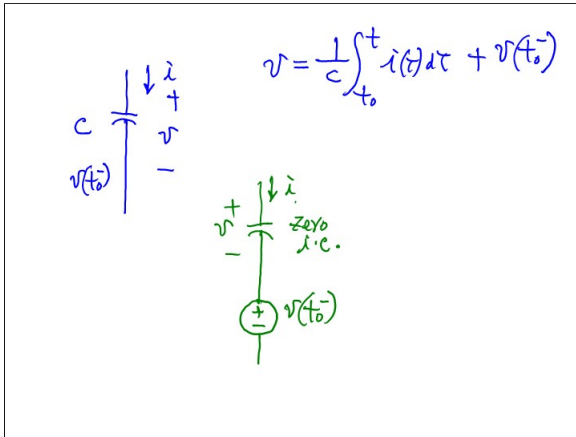





Table 5-4: Basic properties of R, L, and C.

Property	R	L	C
$i-v$ relation	$i = \frac{v}{R}$	$i = \frac{1}{L} \int v dt' + i(t_0)$	$i = C \frac{dv}{dt}$
$v-i$ relation	$v = iR$	$v = L \frac{di}{dt}$	$v = \frac{1}{C} \int i dt' + v(t_0)$
p (power transfer in)	$p = i^2 R$	$p = Li \frac{di}{dt}$	$p = Cv \frac{dv}{dt}$
w (stored energy)	0	$w = \frac{1}{2} Li^2$	$w = \frac{1}{2} Cv^2$
Series combination	$R_{eq} = R_1 + R_2$	$L_{eq} = L_1 + L_2$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$
Parallel combination	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$	$C_{eq} = C_1 + C_2$
dc behavior	no change	short circuit	open circuit
Can v change instantaneously?	yes	yes	no
Can i change instantaneously?	yes	no	yes

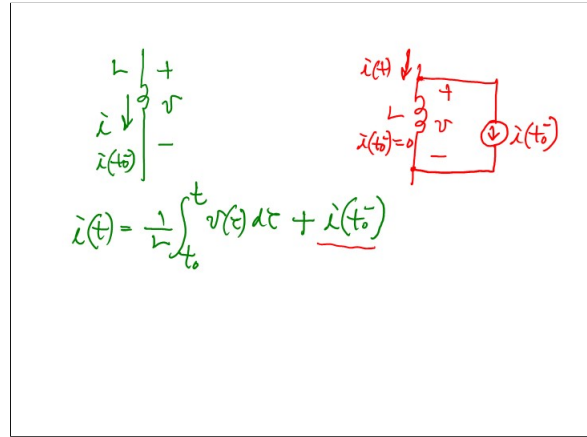

$$\begin{aligned}
 p(t) &= v(t) i(t) \\
 &= 50 \times 10^3 \left[-8 e^{-0.8t} \sin(\pi t/2) + 5 \pi e^{-0.8t} \cos(\pi t/2) \right] \\
 &\quad \times 10 e^{-0.8t} \sin(\pi t/2) \\
 &= -4 e^{-1.6t} \sin^2(\pi t/2) + 2.5 e^{-1.6t} \sin(\pi t/2) \cos(\pi t/2) \\
 &\quad \uparrow \\
 &= -2 e^{-1.6t} (1 - \cos \pi t) + 1.25 e^{-1.6t} \sin(\pi t) \\
 \sin^2 \theta &= \frac{1}{2}(1 - \cos 2\theta) \\
 \sin \theta \cos \theta &= \frac{1}{2} \sin 2\theta \\
 &= -2 e^{-1.6t} + 2 \cos \pi t + 1.25 \sin 2\pi t
 \end{aligned}$$

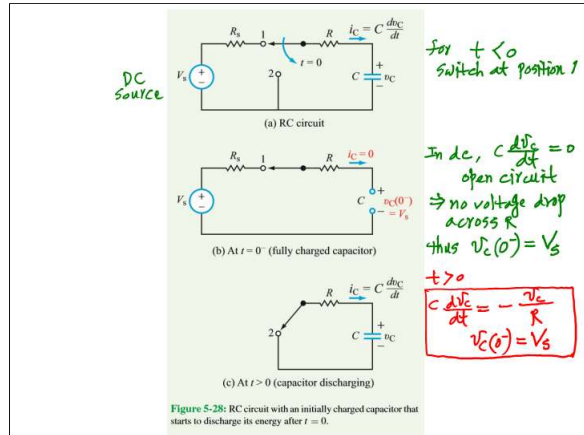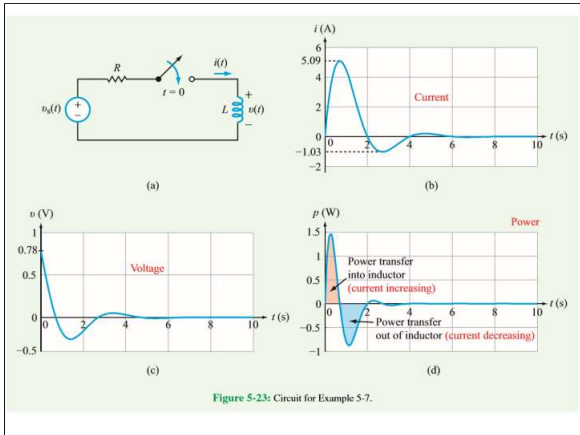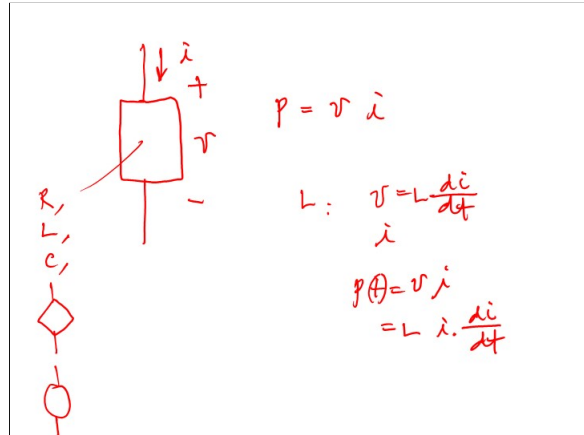at $t=0$ $p(t=0) = -2 + (2 \times 1 + 1.25 \times 0)$
 as $t \rightarrow \infty$ $p(t) \rightarrow 0$ W (makes sense)



$$RC \frac{dv_c}{dt} + v_c = 0. \quad (5.69)$$

Upon dividing both terms by RC, Eq. (5.69) takes the form

$$\frac{dv_c}{dt} + av_c = 0 \quad (\text{source-free}), \quad (5.70)$$

where $a = \frac{1}{RC}$. $v_c(0) = V_s$ (i.c.)

$$\frac{dx}{dt} + ax = 0 \quad (5.71)$$

The solution of the source-free equation is called the **natural response** (discharging condition) of the circuit.

The standard procedure for solving Eq. (5.70) starts by replacing t with dummy variable t' and multiplying both sides by $e^{at'}$.

$$\frac{dv_c}{dt'} e^{at'} + a v_c e^{at'} = 0. \quad (5.72)$$

Next, we recognize that the sum of the two terms on the left-hand side is equal to the expansion of the differential of $(v_c e^{at'})$.

$$\frac{d}{dt'} (v_c e^{at'}) = \frac{dv_c}{dt'} e^{at'} + a v_c e^{at'}. \quad (5.73)$$

Hence, Eq. (5.72) becomes

$$\frac{d}{dt'} (v_c e^{at'}) = 0. \quad (5.74)$$

Integrating both sides, we have

$$\int_0^t \frac{d}{dt'} (v_c e^{at'}) dt' = 0. \quad (5.75)$$

where we have chosen the lower limit to be $t' = 0$ (because we are given specific information on the state of the circuit at that point in time). Performing the integration gives

$$v_c e^{at} \Big|_0^t = 0$$

$$v_C(t) = v_C(0) e^{-t/\tau}, \quad (5.78)$$
 (natural response discharging),

with

$$\tau = RC \quad (\text{s}), \quad (5.79)$$

where τ is called the **time constant** of the circuit, and it is measured in seconds (s).

In view of the initial condition given by Eq. (5.67), namely $v_C(0) = V_s$, the expression for $v_C(t)$ becomes

$$v_C(t) = V_s e^{-t/\tau} u(t), \quad (5.80)$$

where we inserted the unit step function $u(t)$ as a multiplication factor as a substitute for "for $t \geq 0$." The plot shown in Fig. 5-29(a) indicates that in response to the switch action, $v_C(t)$ decays exponentially with time from V_s at $t = 0$ down to its final value of zero as $t \rightarrow \infty$. The decay rate is dictated by the time constant τ . At $t = \tau$,

$$v_C(t = \tau) = V_s e^{-1} = 0.37V_s, \quad (5.81)$$

$$-t/\tau = RC$$

$$e$$

$$t = \tau$$

$$e^{-1} = 0.37$$

$$i_C = C \frac{dv_C}{dt}$$

$$= C \frac{d}{dt} (V_s e^{-t/\tau})$$

$$= V_s e^{-t/\tau} \left(-\frac{1}{\tau}\right)$$

$$= -\frac{V_s}{RC} e^{-t/\tau}$$

Figure 5-29: Response of the RC circuit in Fig. 5-28(a) to moving the SPST switch to terminal 2.

Series RC Circuit Solution

- 1: If switch action is at $t = 0$, analyze circuit at $t = 0^-$ to determine initial conditions $v_C(0^-)$ and $i_C(0^-)$. Use this information to determine $v_C(0)$ and $i_C(0)$, at t immediately after the switch action. Remember that the voltage across a capacitor cannot change instantaneously (between $t = 0^-$ and $t = 0$), but the current can.
- 2: Analyze the circuit to determine $v_C(\infty)$, the voltage across the capacitor long after the switch action.
- 3: Determine the time constant $\tau = RC$.
- 4: Incorporate the information obtained in the previous three steps in Eq. (5.96):

$$v_C(t) = \{v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau}\} u(t).$$
- 5: If the switch action is at $t = T_0$ instead of $t = 0$, replace 0 with T_0 and use Eq. (5.98):

$$v_C(t) = \{v_C(\infty) + [v_C(T_0) - v_C(\infty)] \cdot e^{-(t-T_0)/\tau}\} \cdot u(t - T_0).$$

(a) Original circuit

(b) After replacing circuit with Thévenin equivalent

Figure 5-31: Replacing a resistive circuit with its Thévenin equivalent as seen by capacitor C .

Thévenin Approach to RC Response

Step 1: If the circuit includes a single switch action (open, close, or move between two terminals) at $t = T_0$, analyze the circuit at $t = T_0^-$ (just before the switch action) to determine $v_C(T_0^-)$. When so doing, the capacitor should be replaced with an open circuit. Then set $v_C(T_0) = v_C(T_0^-)$, where $v_C(T_0)$ is the voltage across the capacitor after the switch action.

Step 2: For the circuit configuration at $t \geq T_0$ (after the switch action), obtain the Thévenin equivalent circuit as "seen" by the capacitor. Figure 5-31(b) depicts a general circuit (composed of possibly two subcircuits) connected to a capacitor C . After removing (temporarily) the capacitor and calculating V_{Th} and R_{Th} of the equivalent Thévenin circuit at terminals (a, b) , reinstate the capacitor as in Fig. 5-31(b).

Step 3: The capacitor's voltage response is then given by

$$v_C(t) = \{v_C(\infty) + [v_C(T_0) - v_C(\infty)]e^{-(t-T_0)/\tau}\} \cdot u(t - T_0),$$

with $v_C(\infty) = V_{Th}$, $v_C(T_0)$ as obtained in step 1, and $\tau = R_{Th}C$.

Step 4: If the circuit undergoes multiple switch actions, repeat the procedure for each time segment and use the property that the voltage across a capacitor cannot change instantaneously to match the responses at the boundaries between adjacent time segments.

Table 5-5: Response forms of basic first-order circuits.

Circuit	Diagram	Response
RC		$v_C(t) = \{v_C(\infty) + [v_C(T_0) - v_C(\infty)]e^{-(t-T_0)/\tau}\} u(t - T_0)$ $(\tau = RC)$
RL		$i_L(t) = \{i_L(\infty) + [i_L(T_0) - i_L(\infty)]e^{-(t-T_0)/\tau}\} u(t - T_0)$ $(\tau = L/R)$
Ideal integrator		$v_{out}(t) = -\frac{1}{RC} \int v_i dt' + v_{out}(t_0)$
Ideal differentiator		$v_{out}(t) = -RC \frac{dv_i}{dt}$

Handwritten notes for the integrator and differentiator sections:

$$RC \frac{dv_{out}}{dt} + v_{out} = 0$$

$$\frac{dv_{out}}{dt} = -\frac{1}{RC} v_{in}(t)$$

$$v_{out} = -RC \frac{dv_{in}}{dt}$$

$L \frac{di_L(t)}{dt} = -R i_L(t)$
 $L \frac{di_L(t)}{dt} + R i_L(t) = 0$
 $\frac{di_L(t)}{dt} + \frac{R}{L} i_L(t) = 0$
 $v_C \leftarrow i_L$

Input: dc circuit with switch action @ $t = T_0$



$i_L(t) = [i_L(\infty) + [i_L(T_0) - i_L(\infty)]e^{-(t-T_0)/\tau}] u(t - T_0)$
 $(\tau = L/R)$
 $v_C(t) = \left[\frac{1}{s} + [v_C(T_0) - v_C(\infty)]e^{-(t-T_0)/\tau} \right] u(t - T_0)$

$i_L(t=0) = I_B$
 $i_L(t) = I_{SC}$

(a) Circuit with switch
 (b) Initial condition at $t = 0^-$
 (c) At $t \geq 0$ without the capacitor
 (d) After current to voltage source transformation
 (e) At $t > 0$, after reinserting C in the Thevenin equivalent circuit

$v_C(t) = 6V$
 $R_{TH} = 5k\Omega$
 $C = 100\mu F$
 $i_C(t) = 100\mu F \frac{dv_C}{dt} = -18 \frac{V}{5k\Omega}$
 $\frac{dv_C}{dt} = \frac{-18 - v_C}{100 \times 10^{-6} \times 5 \times 10^3}$
 $= \frac{-18 - v_C}{0.5}$
 $\Rightarrow \frac{dv_C}{dt} + 2v_C = -36$

(f) Plot

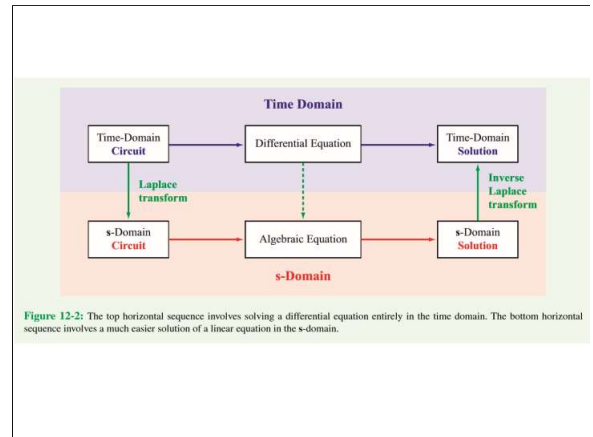 

Solution Procedure: Laplace Transform

Step 1: The circuit is transformed to the Laplace domain—also known as the s-domain.
Step 2: In the s-domain, application of KVL and KCL yields a set of algebraic equations.
Step 3: The equations are solved for the variable of interest.
Step 4: The s-domain solution is transformed back to the time domain.

The uniqueness property can be expressed in symbolic form by

$$f(t) \leftrightarrow \mathbf{F}(s). \quad (12.12a)$$

The two-way arrow is a short-hand notation for the combination of the two statements

$$\mathcal{L}[f(t)] = \mathbf{F}(s), \quad \mathcal{L}^{-1}[\mathbf{F}(s)] = f(t). \quad (12.12b)$$

The first statement asserts that $\mathbf{F}(s)$ is the Laplace transform of $f(t)$, and the second one asserts that the *inverse Laplace transform* ($\mathcal{L}^{-1}[\]$) of $\mathbf{F}(s)$ is $f(t)$.

12-2.1 Definition of the Laplace Transform

The symbol $\mathcal{L}[f(t)]$ is a short-hand notation for "the Laplace transform of function $f(t)$." Usually denoted $F(s)$, the Laplace transform is defined by

$$F(s) = \mathcal{L}[f(t)] = \int_0^{\infty} f(t) e^{-st} dt, \quad (12.10)$$

where s is a complex variable with a real part σ and an imaginary part ω :

$$s = \sigma + j\omega. \quad (12.11)$$



Given that the exponent st has to be dimensionless, s has the unit of inverse second, which is the same as Hz or rad/s. Moreover, since s is a complex quantity, it is often termed **complex frequency**.

$v_s(t) = u(t)$  $\leftrightarrow U(s) = \frac{1}{s}$

$\downarrow \mathcal{L}[u(t)]$

$$\begin{aligned} \mathcal{L}[u(t)] &= \int_0^{\infty} u(t) e^{-st} dt \\ &= \int_0^{\infty} 1 \cdot e^{-st} dt \\ &= \int_0^{\infty} d\left[\frac{e^{-st}}{-s}\right] = -\frac{1}{s} \left[\frac{e^{-s\infty}}{1} - \frac{e^{-s(0)}}{1} \right] \\ &= \frac{1}{s} \end{aligned}$$

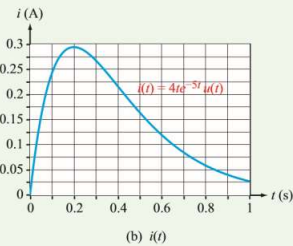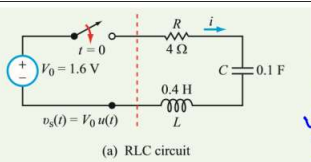$\boxed{\frac{e^{-at}}{s+a}} \leftrightarrow \boxed{\frac{1}{s+a}}$



For $t > 0$

$$\begin{aligned} V_0 &= R i(t) \\ &+ \frac{1}{C} \int_0^t i(\tau) d\tau \\ &+ V_C(0) \\ &+ L \frac{di(t)}{dt} \end{aligned}$$


$t \leftrightarrow s$

$R \leftrightarrow R$

$C \leftrightarrow \frac{1}{Cs}$ (impedance)


$L \leftrightarrow Ls$ (impedance)

$u(t) \leftrightarrow \frac{1}{s}$

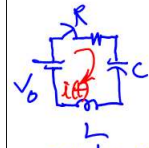

initial condition $v_C(0) = 0$ $i_L(0) = 0$
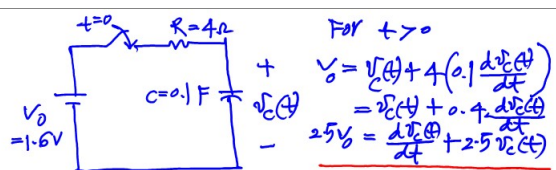
$$\frac{V_0}{s} = R I(s) + \frac{1}{Cs} I(s) + Ls I(s)$$



For $t > 0$

$$\begin{aligned} V_0 &= V_C(t) + 4 \left(0.1 \frac{dV_C(t)}{dt} \right) \\ &= V_C(t) + 0.4 \frac{dV_C(t)}{dt} \\ 2.5 V_0 &= \frac{dV_C(t)}{dt} + 2.5 V_C(t) \end{aligned}$$

$V_C(t) \leftrightarrow V_C(s)$

$\frac{dV_C(t)}{dt} \leftrightarrow s V_C(s) - V_C(0)$

$$\begin{aligned} 2.5 \frac{V_0}{s} &= s V_C(s) + 2.5 V_C(s) \\ &= (s + 2.5) V_C(s) \\ V_C(s) &= \frac{V_0 \times 2.5}{s[s + 2.5]} \\ &= \frac{V_0}{s} + \frac{-V_0}{s + 2.5} \end{aligned}$$

$$\begin{aligned} v_C(t) &= V_0 + (-V_0) e^{-2.5t} \\ &= V_0 [1 - e^{-2.5t}] u(t) \end{aligned}$$

where $i(t)$ is the current flowing through the loop and $v_C(t)$ is the voltage across C. By invoking the i - v relationship for C, Eq. (12.36) becomes

$$Ri + \left[\frac{1}{C} \int_0^t i dt + v_C(0^-) \right] + L \frac{di}{dt} = V_o u(t), \quad (12.37)$$

which now contains a single dependent variable, $i(t)$.

Step 2: Define Laplace transform currents and voltages corresponding to the time-domain currents and voltages and then transform the equation to the s-domain

We designate $\mathbf{I}(s)$ as the s-domain counterpart of $i(t)$,

$$i(t) \longleftrightarrow \mathbf{I}(s). \quad (12.38)$$

To transform Eq. (12.37) to the s-domain, we apply the appropriate property or *Laplace transformation* (LT) from

Tables 12-1 and 12-2, as follows:

$$R i(t) \longleftrightarrow R \mathbf{I}(s) \quad (\text{multiplication by constant}),$$

$$\frac{1}{C} \int_0^t i dt \longleftrightarrow \frac{1}{C} \frac{\mathbf{I}(s)}{s} \quad (\text{time-integral property}),$$

$$v_C(0^-) \longleftrightarrow \frac{v_C(0^-)}{s} \quad (\text{LT of a constant}),$$

$$L \frac{di}{dt} \longleftrightarrow L[s \mathbf{I}(s) - i(0^-)] \quad (\text{time derivative property}),$$

$$V_o u(t) \longleftrightarrow \frac{V_o}{s} \quad (\text{LT of a constant}).$$

The opening paragraph of this section stated that the circuit had no stored energy prior to $t = 0$. Hence, $v_C(0^-) = 0$ and $i(0^-) = 0$. Replacing each of the terms in Eq. (12.37) with its s-domain counterpart leads to

$$R\mathbf{I} + \frac{\mathbf{I}}{Cs} + Ls\mathbf{I} = \frac{V_o}{s} \quad (\text{s-domain}). \quad (12.39)$$

Table 12-1: Properties of the Laplace transform ($f(t) = 0$ for $t < 0^-$).

Property	$f(t)$	$\mathbf{F}(s) = \mathcal{L}\{f(t)\}$
1. Multiplication by constant	$K f(t)$	$K \mathbf{F}(s)$
2. Linearity	$K_1 f_1(t) + K_2 f_2(t)$	$K_1 \mathbf{F}_1(s) + K_2 \mathbf{F}_2(s)$
3. Time scaling	$f(at), \quad a > 0$	$\frac{1}{a} \mathbf{F}\left(\frac{s}{a}\right)$
4. Time shift	$f(t - T) u(t - T)$	$e^{-Ts} \mathbf{F}(s), \quad T \geq 0$
5. Frequency shift	$e^{-at} f(t)$	$\mathbf{F}(s + a)$
6. Time 1st derivative	$f' = \frac{df}{dt}$	$s \mathbf{F}(s) - f(0^-)$
7. Time 2nd derivative	$f'' = \frac{d^2 f}{dt^2}$	$s^2 \mathbf{F}(s) - s f(0^-) - f'(0^-)$
8. Time integral	$\int_0^t f(\tau) d\tau$	$\frac{1}{s} \mathbf{F}(s)$
9. Frequency derivative	$t f(t)$	$-\frac{d}{ds} \mathbf{F}(s)$
10. Frequency integral	$\frac{f(t)}{t}$	$\int_s^\infty \mathbf{F}(s') ds'$