

EE 101 Lecture 14, Feb 21, 2019
 Quiz 7 on Feb 26 based on HW 7.

- [1] Prob. 6.1
- [2] 6.2
- [3] 6.3
- [4] 6.4
- [5] 6.5
- [6] 6.7

[7] Find $i(t)$, $t > 0$ for the circuit below

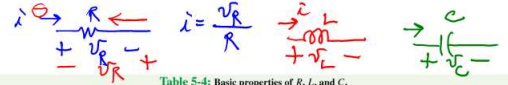
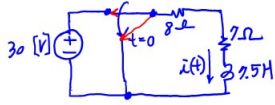


Table 5-4: Basic properties of R, L, and C.

Property	R	L	C
$i-v$ relation	$i = \frac{v}{R}$	$i = \frac{1}{L} \int v dt' + i(t_0)$	$i = C \frac{dv}{dt}$
$v-i$ relation	$v = iR$	$v = L \frac{di}{dt}$	$v = \frac{1}{C} \int i dt' + v(t_0)$
p (power transfer in)	$p = i^2 R$	$p = Li \frac{di}{dt}$	$p = Cv \frac{dv}{dt}$
w (stored energy)	0	$w = \frac{1}{2} Li^2$	$w = \frac{1}{2} Cv^2$
Series combination	$R_{eq} = R_1 + R_2$	$L_{eq} = L_1 + L_2$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$
Parallel combination	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$	$\frac{1}{L_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$ (short circuit)	$C_{eq} = C_1 + C_2$ (open circuit)
dc behavior	no change	short circuit	open circuit
Can v change instantaneously?	yes	yes	no
Can i change instantaneously?	yes	no	yes

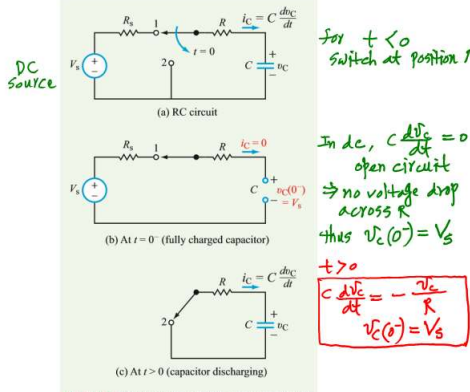


Figure 5-28: RC circuit with an initially charged capacitor that starts to discharge its energy after $t = 0$.

$$RC \frac{dv_c}{dt} + v_c = 0. \quad (5.69)$$

Upon dividing both terms by RC, Eq. (5.69) takes the form

$$\frac{dv_c}{dt} + av_c = 0 \quad (\text{source-free}), \quad (5.70)$$

where

$$\frac{dx}{dt} + ax = 0$$

$$a = \frac{1}{RC}$$

$$v_c(0) = V_s \quad (i.c.)$$

$$(5.71)$$

Table 5-5: Response forms of basic first-order circuits.

Circuit	Diagram	Response
RC	Input: dc circuit with switch action @ $t = T_0$	$v_C(t) = [v_C(\infty) + (v_C(T_0) - v_C(\infty))e^{-(t-T_0)/\tau}] u(t - T_0)$ ($\tau = RC$)
RL	Input: dc circuit with switch action @ $t = T_0$	$i_L(t) = [i_L(\infty) + (i_L(T_0) - i_L(\infty))e^{-(t-T_0)/\tau}] u(t - T_0)$ ($\tau = L/R$)
Ideal integrator		$v_{out}(t) = -\frac{1}{RC} \int v_{in} dt' + v_{out}(t_0)$
Ideal differentiator		$v_{out}(t) = -RC \frac{dv_{in}}{dt}$

Handwritten notes for RC and RL circuits: $RC \frac{dv_c}{dt} + v_c = 0$, $\frac{dv_c}{dt} = -\frac{1}{RC} v_c(t)$, $v_0 = -RC \frac{dv_c}{dt}$.

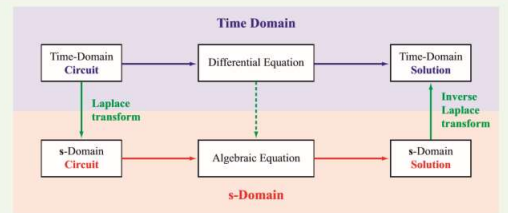


Figure 12-2: The top horizontal sequence involves solving a differential equation entirely in the time domain. The bottom horizontal sequence involves a much easier solution of a linear equation in the s-domain.

$v_s(t) = u(t)$

$\mathcal{L}[u(t)] = \int_0^{\infty} u(t) e^{-st} dt$
 $= \int_0^{\infty} 1 \cdot e^{-st} dt = -\frac{1}{s} \left[e^{-st} \right]_0^{\infty} = \frac{1}{s}$

$\mathcal{L}^{-1}\left[\frac{1}{s+a}\right] = e^{-at} u(t)$

Laplace transform pairs:
 $t \leftrightarrow \frac{1}{s}$
 $R \leftrightarrow R$
 $C \leftrightarrow \frac{1}{Cs}$ (impedance)
 $L \leftrightarrow Ls$ (impedance)
 $u(t) \leftrightarrow \frac{1}{s}$

Initial condition: $v_C(0^-) = 0$, $i_L(0^-) = 0$

$\frac{V_0}{s} = R I(s) + \frac{1}{Cs} I(s) + Ls I(s)$

For $t > 0$
 $V_0 = v_C(t) + 4 \left(0.1 \frac{dv_C(t)}{dt} \right)$
 $2.5 V_0 = \frac{dv_C(t)}{dt} + 2.5 v_C(t)$

$\mathcal{L}\{v_C(t)\} \leftrightarrow V_C(s)$
 $\frac{d}{dt} v_C(t) \leftrightarrow s V_C(s) - v_C(0^-)$

$2.5 \cdot \frac{1.6}{s} = s V_C(s) + 2.5 V_C(s)$
 $= (s + 2.5) V_C(s)$

$V_C(s) = \frac{V_0 \times 2.5}{s(s + 2.5)} = \frac{V_0}{s} + \frac{-V_0}{s + 2.5}$

$v_C(t) = \left(V_0 - V_0 e^{-2.5t} \right) u(t) = V_0 (1 - e^{-2.5t}) u(t)$

where $i(t)$ is the current flowing through the loop and $v_C(t)$ is the voltage across C. By invoking the i - v relationship for C, Eq. (12.36) becomes

Tables 12-1 and 12-2, as follows:
 $R i(t) \leftrightarrow R I(s)$ (multiplication by constant),
 $\frac{1}{C} \int_0^t i dt + v_C(0^-) \leftrightarrow \frac{1}{C} \frac{I(s)}{s} + \frac{v_C(0^-)}{s}$ (time-integral property),
 $v_C(0^-) \leftrightarrow \frac{v_C(0^-)}{s}$ (LT of a constant),
 $L \frac{di}{dt} \leftrightarrow L[s I(s) - i(0^-)]$ (time derivative property),
 $V_0 u(t) \leftrightarrow \frac{V_0}{s}$ (LT of a constant).

Step 2: Define Laplace transform currents and voltages corresponding to the time-domain currents and voltages and then transform the equation to the s -domain. We designate $I(s)$ as the s -domain counterpart of $i(t)$.

$i(t) \leftrightarrow I(s)$ (12.38)

To transform Eq. (12.37) to the s -domain, we apply the appropriate property or Laplace transformation (LT) from

$R I + \frac{1}{Cs} + Ls I = \frac{V_0}{s}$ (s-domain) (12.39)

Table 12-1: Properties of the Laplace transform ($f(t) = 0$ for $t < 0^-$).

Property	$f(t)$	$F(s) = \mathcal{L}\{f(t)\}$
1. Multiplication by constant	$K f(t)$	$K F(s)$
2. Linearity	$K_1 f_1(t) + K_2 f_2(t)$	$K_1 F_1(s) + K_2 F_2(s)$
3. Time scaling	$f(at), a > 0$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
4. Time shift	$f(t - T) u(t - T)$	$e^{-Ts} F(s), T \geq 0$
5. Frequency shift	$e^{-at} f(t)$	$F(s + a)$
6. Time 1st derivative	$f' = \frac{df}{dt}$	$s F(s) - f(0^-)$
7. Time 2nd derivative	$f'' = \frac{d^2 f}{dt^2}$	$s^2 F(s) - s f(0^-) - f'(0^-)$
8. Time integral	$\int_0^t f(\tau) d\tau$	$\frac{1}{s} F(s)$
9. Frequency derivative	$t f(t)$	$-\frac{d}{ds} F(s)$
10. Frequency integral	$\frac{f(t)}{t}$	$\int_s^{\infty} F(s') ds'$

In general, for

$\frac{dx}{dt} + ax = y(t)$

$\mathcal{L}\left\{ \frac{dx}{dt} + ax \right\} = \mathcal{L}\{y(t)\}$

$sX(s) - x(0^-) + aX(s) = Y(s)$

$X(s)(s + a) = Y(s) + x(0^-)$

$X(s) = \frac{Y(s)}{s + a} + \frac{x(0^-)}{s + a}$

Example: $\Rightarrow y(t) = u(t), Y(s) = \frac{1}{s}$

$x(t) = \mathcal{L}^{-1}\left\{ \frac{Y(s)}{s + a} \right\} + x(0^-) e^{-at}$
 Force response + Natural response

\mathcal{L}^{-1} (Inverse Laplace transform)

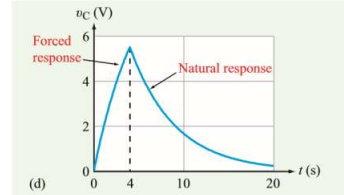
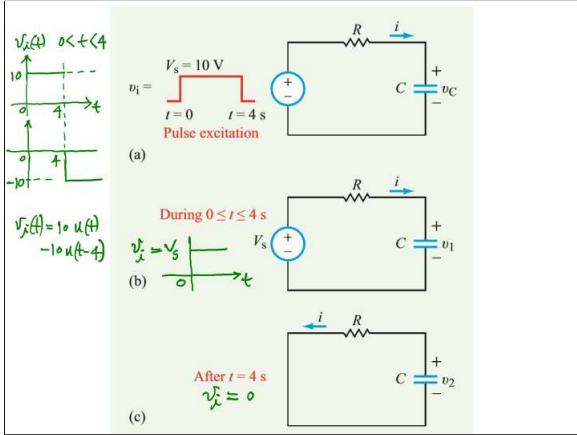


Figure 5-35: RC-circuit response to a 4 s long rectangular pulse.

Solution: According to Example 5-2, a rectangular pulse is equivalent to the sum of two step functions. Thus

$$v_1(t) = V_s[u(t - T_1) - u(t - T_2)],$$

where $u(t - T_1)$ accounts for the rise in level from 0 to 1 at $t = T_1$ and the second term (with negative amplitude) serves to counteract (cancel) the first term after $t = T_2$. For the present problem, $T_1 = 0$, and $T_2 = 4\text{ s}$. Hence, the input pulse can be written as

$$v_1(t) = V_s u(t) - V_s u(t - 4).$$

Response to $V_s u(t)$ alone

The response $v_1(t)$ is given by Eq. (5.96) with $v_1(0) = 0$, $v_1(\infty) = V_s$, and $\tau = RC$. Hence,

$$v_1(t) = v_1(\infty) + [v_1(0) - v_1(\infty)]e^{-t/\tau} = V_s(1 - e^{-t/\tau}) \quad (\text{for } t \geq 0).$$

For $V_s = 10\text{ V}$ and $\tau = RC = 25 \times 10^3 \times 0.2 \times 10^{-3} = 5\text{ s}$,

$$v_1(t) = 10(1 - e^{-0.2t}) \text{ V} \quad (\text{for } t \geq 0).$$

Response to $-V_s u(t - 4)$ alone


The second step function has an amplitude of $-V_s$ and is delayed in time by 4 s. Upon reversing the polarity of V_s and replacing t with $(t - 4)$, we have

$$v_2(t) = -10[1 - e^{-0.2(t-4)}] \text{ V} \quad (\text{for } t \geq 4\text{ s}).$$


Total response

The total response for $t \geq 0$ therefore is given by

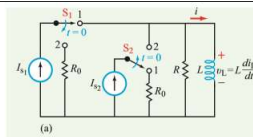
$$v_C(t) = v_1(t) + v_2(t) = 10[1 - e^{-0.2t}] - 10[1 - e^{-0.2(t-4)}] u(t - 4) \text{ V},$$



(a)

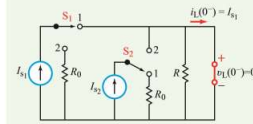


(b) Initial condition at $t = 0^-$

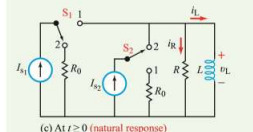


(c) At $t \geq 0$ (natural response)


$$I = I_L + \frac{v_L}{R} = I_L + \frac{1}{R} L \frac{di_L}{dt}$$

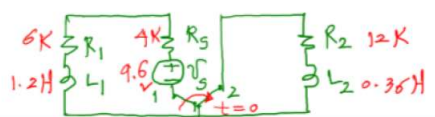

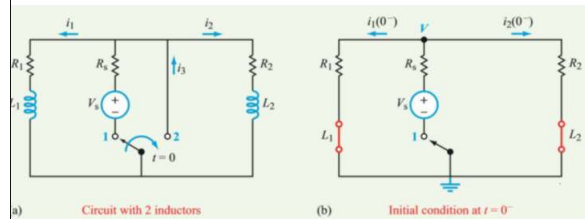Example 5-13: Circuit with Two RL Branches

After having been in position 1 for a long time, the SPDT switch in Fig. 5-38(a) was moved to position 2 at $t = 0$. Determine i_1 , i_2 , and i_3 for $t \geq 0$, given that $V_s = 9.6\text{ V}$, $R_s = 4\text{ k}\Omega$, $R_1 = 6\text{ k}\Omega$, $R_2 = 12\text{ k}\Omega$, $L_1 = 1.2\text{ H}$, and $L_2 = 0.36\text{ H}$.



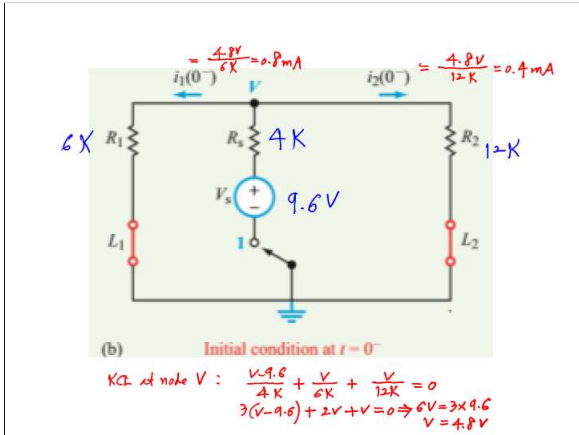

to the expression given by Eq. (5.96). Thus, the general form for the current through an inductor in an RL circuit is given by

$$i_L(t) = [i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau}] u(t), \quad (5.107)$$

(switch action at $t = 0$)




with time constant $\tau = L/R$. For the specific circuit in Fig. 5-37(a), $i_L(0) = I_{s1}$ and $i_L(\infty) = I_{s2}$.



If the sudden change in the circuit configuration happens at $t = T_0$ instead of at $t = 0$, the general expression for $i_L(t)$ becomes

$$i_L(t) = \{i_L(\infty) + [i_L(T_0) - i_L(\infty)]e^{-(t-T_0)/\tau}\} \cdot u(t - T_0), \quad (5.108)$$

(switch action at $t = T_0$)

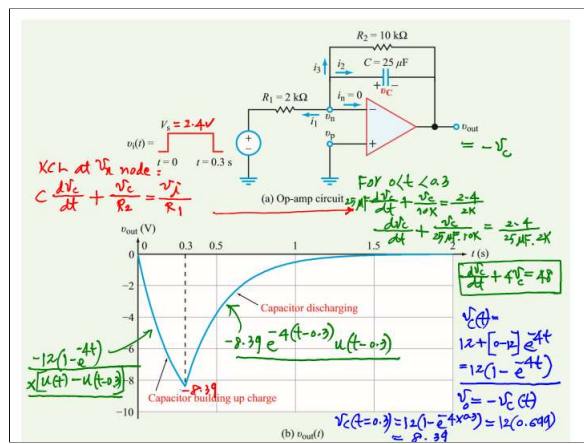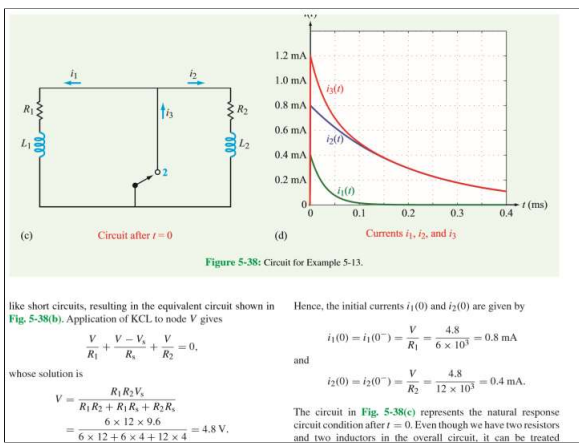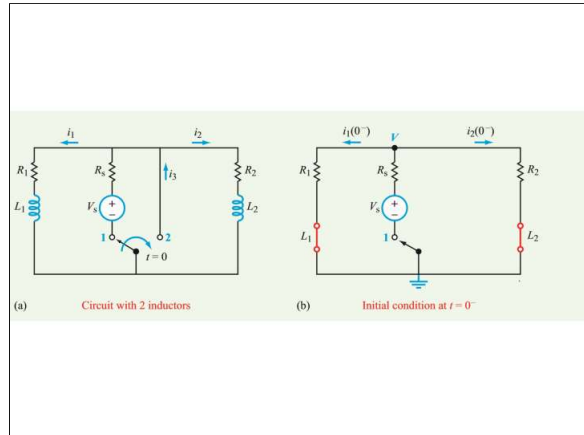where $i_L(T_0)$ is the current at T_0 . This expression is the analogue of Eq. (5.98) for the voltage across the capacitor.



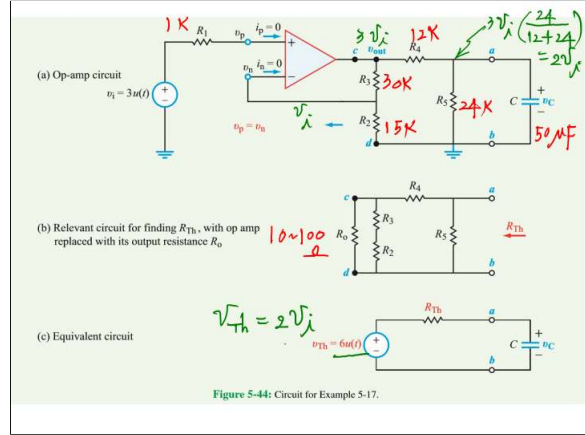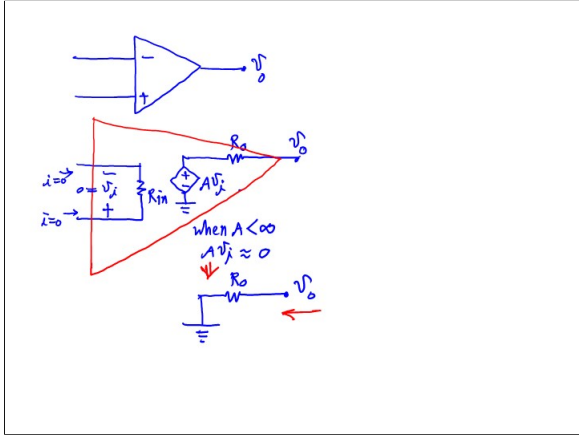

$$R_{Th} = \left[\underbrace{\left\{ R_o \parallel (R_2 + R_3) \right\}}_{\text{small}} + R_4 \right] \parallel R_5$$

$$\approx R_4 \parallel R_5 = \frac{12K \times 24K}{12K + 24K} = 8K\Omega$$

$$6 \mu A + \frac{dV_C(t)}{dt} + \frac{V_C(t)}{8K \times 50 \mu} = 0, t > 0$$

$$V_C(t) = 6 + (0 - 6)e^{-2.5t}$$

$$= 6(1 - e^{-2.5t}) \mu(t)$$