

EE101 W19 Lecture 17, May 5, 2019
 HW #9 for Quiz 9 on May 12

[1] 6.29 [6] 7.1
 [2] 6.35 [7] 7.10 (a), (b), (c)
 [3] 6.38 [8] 7.22
 [4] 6.50 [9] 7.36
 [5] 6.54 [10] 7.86

Quiz 7 Average = 7.08
 20 = 2.33

chap 7 AC Analysis

Figure 7-1: The function $v(t) = V_m \cos(\omega t)$ plotted as a function of (a) ωt and (b) t .

Table 7-1: Useful trigonometric identities (additional relations are given in Appendix D):

- $\sin \omega t = +\cos(\omega t - 90^\circ)$ (7.7a)
- $\sin x = \pm \cos(x \pm 90^\circ)$ (7.7b)
- $\cos x = \pm \sin(x \pm 90^\circ)$ (7.7b)
- $\sin x = -\sin(x \pm 180^\circ)$ (7.7c)
- $\cos x = -\cos(x \pm 180^\circ)$ (7.7d)
- $\sin(-x) = -\sin x$ (7.7e)
- $\cos(-x) = \cos x$ (7.7f)
- $\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$ (7.7g)
- $\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$ (7.7h)
- $2 \sin x \sin y = \cos(x - y) - \cos(x + y)$ (7.7i)
- $2 \sin x \cos y = \sin(x + y) + \sin(x - y)$ (7.7j)
- $2 \cos x \cos y = \cos(x + y) + \cos(x - y)$ (7.7k)

In addition to ωt , the argument of the cosine function contains a constant angle of -60° . A cosine-referenced sinusoidal function generally takes the form

$$v(t) = V_m \cos(\omega t + \phi), \quad (7.8)$$


where ϕ is called its **phase angle**. For $i(t)$ of Eq. (7.8), $\phi = -60^\circ$.

The angle ϕ may assume any positive or negative value, but we usually add or subtract multiples of 2π radians (or equivalently, multiples of 360°) so that the remainder is between -180° and $+180^\circ$. The magnitude and sign (+ or -) of ϕ determine, respectively, by how much and in what direction the waveform of $v(t)$ is shifted along the time axis, relative to the reference waveform corresponding to $v(t)$ with $\phi = 0$. Figure 7-2 displays three waveforms:

Sinusoidal waveforms can be expressed in terms of either sine or cosine functions.

► To avoid confusion, we adopt the cosine form as our reference standard throughout this and followup chapters. ◀

This means that we will always express voltages and currents in terms of cosine functions, so if a voltage (or current) waveform is given in terms of a sine function, we should first convert it to a cosine form with a positive amplitude before proceeding with our circuit analysis. Conversion from sine to cosine form is realized through the application of Eq. (7.7a) of Table 7-1.

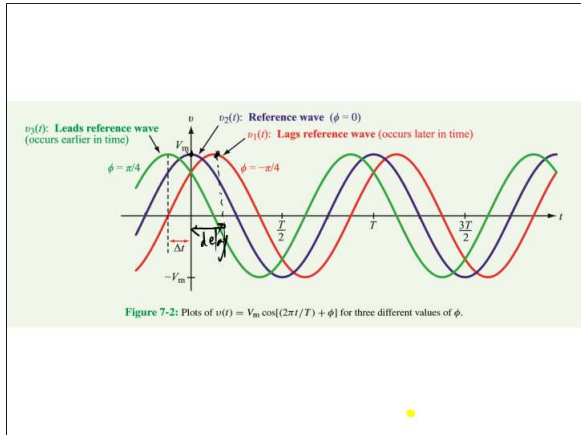

Example 7-2: Phase Lead / Lag

Given the current waveforms

$$i_1(t) = -8 \cos(\omega t - 30^\circ) \text{ A}$$

and

$$i_2(t) = 12 \sin(\omega t + 45^\circ) \text{ A}$$

does $i_1(t)$ lead $i_2(t)$, or the other way around, and by how much?

Solution: Standard cosine format requires that the sinusoidal functions be cosines and that the amplitudes have positive values. Application of Eq. (7.7d) of Table 7-1 allows us to remove the negative sign preceding the amplitude of $i_1(t)$.

$$i_1(t) = 8 \cos(\omega t - 30^\circ) = 8 \cos(\omega t - 30^\circ + 180^\circ) = 8 \cos(\omega t + 150^\circ) \text{ A}$$

Application of Eq. (7.7a) to $i_2(t)$ leads to

$$i_2(t) = 12 \sin(\omega t + 45^\circ) = 12 \cos(\omega t + 45^\circ - 90^\circ) = 12 \cos(\omega t - 45^\circ) \text{ A}$$

Hence, $\phi_1 = 150^\circ$, $\phi_2 = -45^\circ$, and

Exercise 7-2: Given two current waveforms:

$$i_1(t) = 3 \cos \omega t$$

and


$$i_2(t) = 3 \sin(\omega t + 36^\circ),$$

does $i_2(t)$ lead or lag $i_1(t)$, and by what phase angle?

Answer: $i_2(t)$ lags $i_1(t)$ by 54° . (See CAD)

$$i_2(t) = 3 \cos(\omega t + 36^\circ - 90^\circ) = 3 \cos(\omega t - 54^\circ)$$

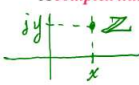A complex number z may be written in the **rectangular form**




$$z = x + jy, \quad (7.12)$$

where x and y are the **real** ($\Re(z)$) and **imaginary** ($\Im(z)$) parts of z , respectively, and $j = \sqrt{-1}$. That is,

$$x = \Re(z), \quad y = \Im(z). \quad (7.13)$$

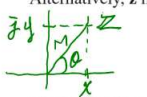
Alternatively, z may be written in **polar form** as



$$z = |z|e^{j\theta} = |z|\angle\theta \quad (7.14)$$

$$M = |z| = \sqrt{x^2 + y^2}, \quad \theta = \tan^{-1} \frac{y}{x}$$

where $|z|$ is the magnitude of z , θ is its phase angle, and the form $\angle\theta$ is a useful shorthand representation commonly used in numerical calculations. A phase angle may be expressed in degrees, as in $\theta = 30^\circ$, or in radians, as in $\theta = 0.52$ rad.

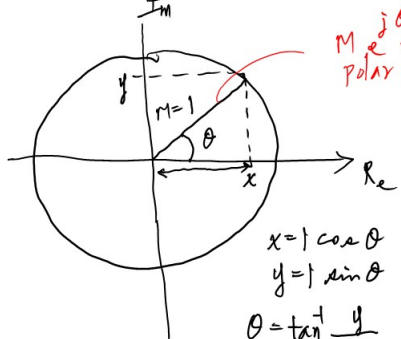

$M e^{j\theta} = M \angle \theta$
POLAR notation


$$x = |z| \cos \theta$$

$$y = |z| \sin \theta$$

$$\theta = \tan^{-1} \frac{y}{x}$$

$$\sqrt{x^2 + y^2} = m$$

By applying **Euler's identity**,

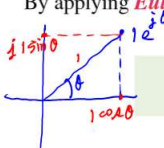

$$e^{j\theta} = \cos \theta + j \sin \theta, \quad (7.15)$$

we can convert z from polar form, as in Eq. (7.14), into rectangular form, as in Eq. (7.12),

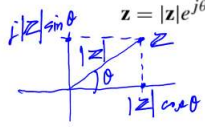
$$z = |z|e^{j\theta} = |z| \cos \theta + j|z| \sin \theta, \quad (7.16)$$


Table 7-2: Properties of complex numbers.

Euler's Identity: $e^{j\theta} = \cos \theta + j \sin \theta$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$e^{-j\theta} = \cos(\theta) - j \sin(\theta) = \cos \theta - j \sin \theta$

$z = x + jy = |z|e^{j\theta}$ $z^* = x - jy = |z|e^{-j\theta}$ **complex conjugate**

Real part $x = \Re(z) = |z| \cos \theta$ $|z| = \sqrt{z z^*} = \sqrt{x^2 + y^2}$

Imaginary part $y = \Im(z) = |z| \sin \theta$ $\theta = \begin{cases} \tan^{-1}(y/x) & \text{if } x > 0, \\ \tan^{-1}(y/x) \pm \pi & \text{if } x < 0, \\ \pi/2 & \text{if } x = 0 \text{ and } y > 0, \\ -\pi/2 & \text{if } x = 0 \text{ and } y < 0. \end{cases}$

$z^n = |z|^n e^{jn\theta}$ $z^{1/2} = \pm |z|^{1/2} e^{j\theta/2}$



$z_1 = x_1 + jy_1$ $z_2 = x_2 + jy_2$

$z_1 = z_2$ iff $x_1 = x_2$ and $y_1 = y_2$ $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

$z_1 z_2 = |z_1| |z_2| e^{j(\theta_1 + \theta_2)}$ $\frac{z_1}{z_2} = \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)}$

$-1 = e^{j\pi} = e^{-j\pi} = 1 \angle \pm 180^\circ$ $-j = e^{-j\pi/2} = 1 \angle -90^\circ$

$j = e^{j\pi/2} = 1 \angle 90^\circ$ $\sqrt{j} = \pm e^{j\pi/4} = \pm \frac{(1 + j)}{\sqrt{2}}$ $\sqrt{-j} = \pm e^{-j\pi/4} = \pm \frac{(1 - j)}{\sqrt{2}}$
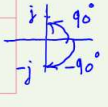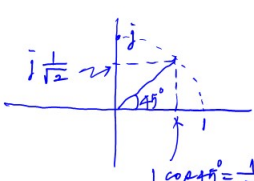
$$j = 1 e^{j90^\circ}$$

$$\sqrt{j} = \pm \sqrt{1} e^{j\frac{90^\circ}{2}} = \pm 1 e^{j45^\circ} = \pm \left(\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right) = \pm \frac{1}{\sqrt{2}} (1 + j)$$

$$1 \angle 45^\circ = \frac{1}{\sqrt{2}}$$

the desired variable—such as a particular voltage or current—in the phasor domain, conversion back to the time domain provides the same solution that we would have obtained had we solved the integro-differential equations entirely in the time domain. The procedure involves multiple steps, but it avoids the complexity of solving differential equations containing sinusoidal functions.

7-3.1 Time-Domain/Phasor-Domain Correspondence

Transformation from the time domain to the phasor domain entails transforming all time-dependent quantities in the circuit, which in effect transforms the entire circuit from the time domain to an equivalent circuit in the phasor domain. The quantities involved in the transformation include all currents and voltages, all sources, and all capacitors and inductors. The values of capacitors and inductors do not change per se, but their i - v relationships undergo a transformation because they involve differentiation or integration with respect to t .

Any cosinusoidally **time-varying function** $x(t)$, representing a voltage or a current, can be expressed in the form

$$x(t) = \Re\{X e^{j\omega t}\} \quad (7.28)$$

where X is a **time-independent function** called the **phasor counterpart** of $x(t)$. Thus, $x(t)$ is defined in the time domain, while its counterpart X is defined in the phasor domain.

Time Domain **Phasor Domain**

$v(t) = V_0 \cos \omega t$ \leftrightarrow $V = V_0$ (7.31a)

$v(t) = V_0 \cos(\omega t + \phi)$ \leftrightarrow $V = V_0 e^{j\phi}$ (7.31b)

If $\phi = -\pi/2$,

$v(t) = V_0 \cos(\omega t - \pi/2) \leftrightarrow V = V_0 e^{-j\pi/2} = -j$ (7.32)

Since $\cos(\omega t - \pi/2) = \cos(\pi/2 - \omega t) = \sin \omega t$ and $e^{-j\pi/2} = \cos(\pi/2) - j \sin(\pi/2) = -j$,

Eq. (7.32) reduces to $V_0 \cos(\omega t - 90^\circ) = V_0 e^{-j\pi/2}$

$v(t) = V_0 \sin \omega t \leftrightarrow V = -j V_0$ (7.33)

which can be generalized to

$v(t) = V_0 \sin(\omega t + \phi) \leftrightarrow V = V_0 e^{j(\phi - \pi/2)}$ (7.34)

Occasionally, voltage and current time functions may encounter differentiation or integration. For example, consider a current $i(t)$ with a corresponding phasor I ,

$$i(t) = \Re\{I e^{j\omega t}\} \quad (7.35)$$

where I may be complex but, by definition, not a function of time. The derivative di/dt is given by

$$\frac{d}{dt} \Re\{I e^{j\omega t}\} = \Re\left\{ \frac{d}{dt} (I e^{j\omega t}) \right\} = \Re\{j\omega I e^{j\omega t}\}$$

where $X = X \cos(\omega t + \phi)$ $X = X e^{j\theta}$

$$X = X e^{j\phi}$$

$$X e^{j\omega t} = X e^{j\omega t} e^{j\phi}$$

$$= X e^{j(\omega t + \phi)}$$

$$\text{Re } X e^{j\omega t} = X \cos(\omega t + \phi)$$

$$\text{Im } X e^{j\omega t} = X \sin(\omega t + \phi)$$

$\frac{d}{dt} \leftrightarrow j\omega$ (7.37)

time derivative, and vice versa. We surmise from Eq. (7.36) that

or

Differentiation of a time function $i(t)$ in the time domain is equivalent to multiplication of its phasor counterpart \mathbf{I} by $j\omega$ in the phasor domain.

Similarly,

$$\int i dt = \int \Re\{I e^{j\omega t}\} dt = \Re\left\{I \int e^{j\omega t} dt\right\} = \Re\left\{I \left[\frac{1}{j\omega} e^{j\omega t}\right]\right\} \quad (7.38)$$

phasor of $\int i dt$

or

$$\int i dt \leftrightarrow \frac{\mathbf{I}}{j\omega} \quad (7.39)$$

Table 7-3: Time-domain sinusoidal functions $x(t)$ and their cosine-reference phasor-domain counterparts \mathbf{X} , where $x(t) = \Re\{X e^{j\omega t}\}$.

$x(t)$	\mathbf{X}
$A \cos \omega t$	A
$A \cos(\omega t + \phi)$	$A e^{j\phi}$
$-A \cos(\omega t + \phi)$	$A e^{j(\phi+\pi)}$
$A \sin \omega t$	$A e^{-j\pi/2} = -jA$
$A \sin(\omega t + \phi)$	$A e^{j(\phi-\pi/2)}$
$-A \sin(\omega t + \phi)$	$A e^{j(\phi+\pi/2)}$
$\frac{d}{dt} x(t)$	$j\omega \mathbf{X}$
$\frac{d}{dt} [A \cos(\omega t + \phi)]$	$j\omega A e^{j\phi}$
$\int x(t) dt$	$\frac{1}{j\omega} \mathbf{X}$
$\int A \cos(\omega t + \phi) dt$	$\frac{1}{j\omega} A e^{j\phi}$

$i_{\text{R}} = \Re\{I_{\text{R}} e^{j\omega t}\} \quad (7.41b)$

Table 7-4: Summary of v - i properties for R , L , and C .

Property	R	L	C
v - i	$v = Ri$	$v = L \frac{di}{dt}$	$i = C \frac{dv}{dt}$
\mathbf{V} - \mathbf{I}	$\mathbf{V} = R\mathbf{I}$	$\mathbf{V} = j\omega L\mathbf{I}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$
\mathbf{Z}	R	$j\omega L$	$\frac{1}{j\omega C}$
dc equivalent	R	Short circuit	Open circuit
High-frequency equivalent	R	Open circuit	Short circuit
Frequency response	$ Z_R $	$ Z_L $	$ Z_C $

Exercise 7-5: Determine the phasor counterparts of the following waveforms:

(a) $i_1(t) = 2 \sin(6 \times 10^3 t - 30^\circ)$ A. $\rightarrow 2 \cos(6 \times 10^3 t - 30^\circ - 90^\circ) = 2 \cos(6 \times 10^3 t - 120^\circ)$

(b) $i_2(t) = 4 \sin(1000t + 136^\circ)$ A. $\rightarrow 4 \cos(1000t + 136^\circ - 90^\circ) = 4 \cos(1000t + 46^\circ)$

Answer: (a) $\mathbf{I}_1 = 2 \angle -120^\circ$ A. (b) $\mathbf{I}_2 = 4 \angle -134^\circ$ A. (See CAD)

Exercise 7-6: Obtain the time-domain waveforms (in standard cosine format) corresponding to the following phasors at angular frequency $\omega = 3 \times 10^4$ rad/s:

(a) $\mathbf{V}_1 = (-3 + j4)$ V. $\rightarrow 5 \angle 126.87^\circ$

(b) $\mathbf{V}_2 = (3 - j4)$ V. $\rightarrow 5 \angle -53.13^\circ$

Answer: (a) $v_1(t) = 5 \cos(3 \times 10^4 t + 126.87^\circ)$ V. (b) $v_2(t) = 5 \cos(3 \times 10^4 t - 53.13^\circ)$ V. (See CAD)

Exercise 7-7: At $\omega = 10^6$ rad/s, the phasor voltage across and current through a certain element are given by $\mathbf{V} = 4 \angle -20^\circ$ V and $\mathbf{I} = 2 \angle 70^\circ$ A. What type of element is it?

Answer: Capacitor with $C = 0.5 \mu\text{F}$. (See CAD)

$$\cos(\theta_1 - 90^\circ)$$

$$= \cos \theta_1 \cos 90^\circ + \sin \theta_1 \sin 90^\circ$$

$$= \sin \theta_1$$

phasor domain circuit analysis

Step 1: Adopt Cosine Reference (Time Domain). $v_s(t) = 12 \sin(\omega t - 45^\circ)$ (V). $= 12 \cos(\omega t - 45^\circ - 90^\circ) = 12 \cos(\omega t - 135^\circ)$

Step 2: Transfer to Phasor Domain. $\mathbf{V}_s = 12 \angle -135^\circ$ (V). $\mathbf{Z}_R = R$, $\mathbf{Z}_L = j\omega L$, $\mathbf{Z}_C = \frac{1}{j\omega C}$.

Step 3: Cast Equations in Phasor Form. Mesh analysis KVL: $\mathbf{I} \left(R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$.

Step 4: Solve for Unknown Variable (Phasor Domain). $\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$. $\mathbf{I} = \frac{\mathbf{V}_s}{Z}$, $Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$, $e^{j \tan^{-1} \left(\frac{1/\omega C}{R} \right)}$.

Step 5: Transform Solution Back to Time Domain. $i(t) = 8 \cos(\omega t - 105^\circ)$ (mA).

Figure 7-7: Five-step procedure for analyzing ac circuits using the phasor-domain technique.

Using the specified values, namely $R = \sqrt{3} \text{ k}\Omega$, $C = 1 \mu\text{F}$, and $\omega = 10^3 \text{ rad/s}$, Eq. (7.67) becomes

$$\mathbf{I} = \frac{j12 \times 10^3 \times 10^{-6} e^{-j135^\circ}}{1 + j10^3 \times \sqrt{3} \times 10^3 \times 10^{-6}} = \frac{j12e^{-j135^\circ}}{1 + j\sqrt{3}} \text{ mA}$$

$$= \frac{j\omega C V_s}{1 + j\omega C R}$$

$$= \frac{j \cdot 10^3 \cdot 10^{-6} \cdot 12e^{-j135^\circ}}{1 + j \cdot 10^3 \cdot (\sqrt{3} \times 10^3) \cdot 10^{-6}}$$

In preparation for the next step, we should convert the expression for \mathbf{I} into polar form ($Ae^{j\phi}$, where A is a positive real number) because it is easier to multiply or divide two complex numbers using the polar form. To that end, we should replace j in the numerator with $e^{j\pi/2}$ and convert the denominator into polar form:

$$1 + j\sqrt{3} = \sqrt{1+3} e^{j\phi} = 2e^{j\phi}$$

where

$$\phi = \tan^{-1}\left(\frac{\sqrt{3}}{1}\right) = 60^\circ$$

Hence,


$$\mathbf{I} = \frac{12e^{-j135^\circ} \cdot e^{j90^\circ}}{2e^{j60^\circ}} = 6e^{j(-135^\circ+90^\circ-60^\circ)} = 6e^{-j105^\circ} \text{ mA}$$

Step 5: Transform solution back to time domain


To return to the time domain, we apply the fundamental relation between a sinusoidal function and its phasor counterpart, namely

$$i(t) = \Re\{Ie^{j\omega t}\} = \Re\{6e^{-j105^\circ} e^{j\omega t}\} = 6\cos(\omega t - 105^\circ) \text{ mA}$$

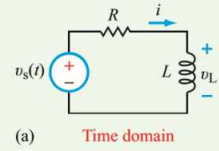This concludes our demonstration of the five-step procedure of the phasor-domain analysis technique. The procedure is equally applicable for solving any linear ac circuit.



(a) Time domain

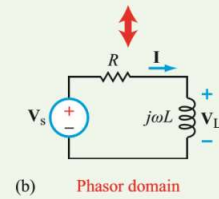

(b) Phasor domain

Figure 7-8: RL circuit of Example 7-5.

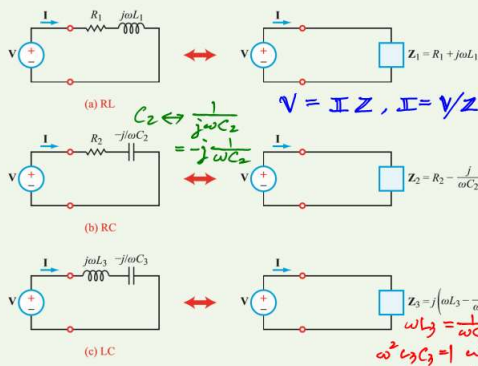


Figure 7-9: Three different, two-element, series combinations.

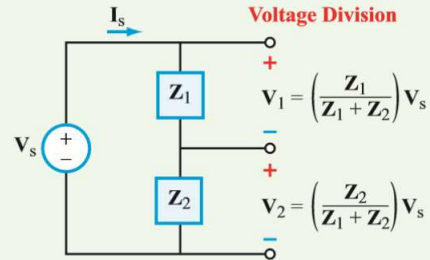


Figure 7-10: Voltage division among two impedances in series.



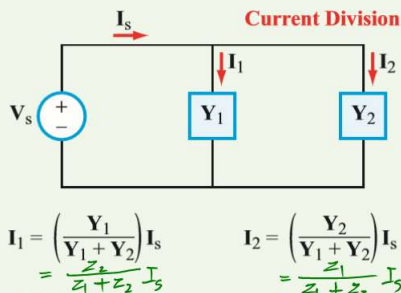
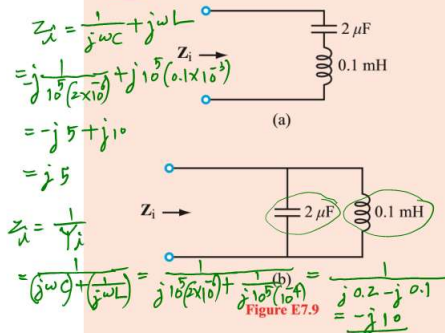


Figure 7-11: Current division among two admittances in parallel.

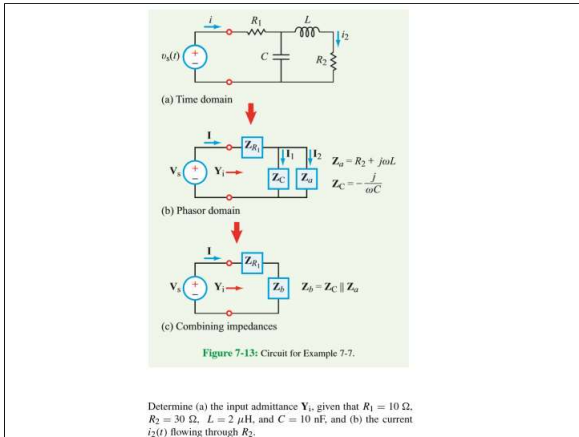Exercise 7-9: Determine the input impedance at $\omega = 10^5 \text{ rad/s}$ for each of the circuits in Fig. E7.9.



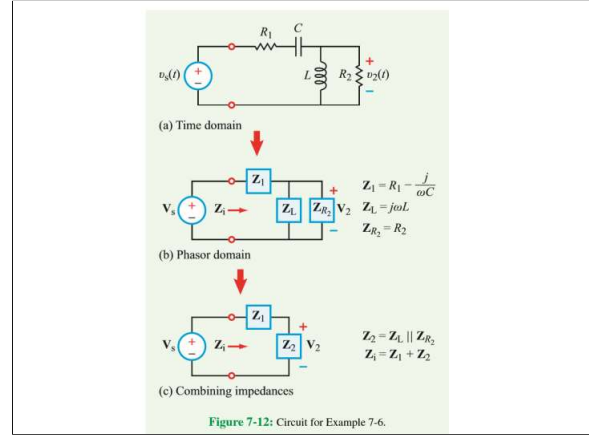Answer: (a) $Z_a = j5 \Omega$, (b) $Z_b = -j10 \Omega$. (See CAD)



Solution: (a) We start by converting $v_s(t)$ to cosine format:

$$v_s(t) = 4 \sin(10^7 t + 15^\circ) = 4 \cos(10^7 t + 15^\circ - 90^\circ) = 4 \cos(10^7 t - 75^\circ) \text{ V.}$$

The corresponding phasor voltage is

$$\mathbf{V}_s = 4e^{-j75^\circ} \text{ V,}$$

and the impedances shown in **Fig. 7-13(b)** are given by

$$\mathbf{Z}_{R1} = R_1 = 10 \Omega,$$

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{10^7 \times 10^{-8}} = -j10 \Omega,$$

$\mathbf{Z}_L = j\omega L = 30 + j10^7 \times 2 \times 10^{-6} = (30 + j20) \Omega$.
 In **Fig. 7-13(c)**, \mathbf{Z}_a represents the parallel combination of \mathbf{Z}_C and \mathbf{Z}_L .

$$\mathbf{Z}_a = \mathbf{Z}_C \parallel \mathbf{Z}_L = \frac{(-j10)(30 + j20)}{-j10 + 30 + j20} = \frac{20 - j30}{3 + j1} = \frac{(20 - j30)(3 - j1)}{(3 + j1)(3 - j1)} = \frac{3 - j11}{169 + 121} = (4.5 + j3.8) \times 10^{-2} = 5.89 \times 10^{-2} e^{j40.2^\circ} \text{ S.}$$


(b) The current \mathbf{I} is given by

$$\mathbf{I} = \mathbf{V}_i \mathbf{Y}_i = (4e^{-j75^\circ})(5.89 \times 10^{-2} e^{j40.2^\circ}) = 0.235e^{-j34.8^\circ} \text{ A.}$$

By current division in **Fig. 7-13(b)**:

$$\mathbf{I}_2 = \frac{\mathbf{Z}_C}{\mathbf{Z}_a + \mathbf{Z}_C} \mathbf{I} = \frac{-j10}{30 + j20 - j10} (0.235e^{-j34.8^\circ}) = \frac{2.35e^{-j34.8^\circ} e^{-j90^\circ}}{31.6e^{j36.9^\circ}} = 7.4 \times 10^{-2} e^{-j143.2^\circ} \text{ A.}$$

The corresponding current in the time domain is
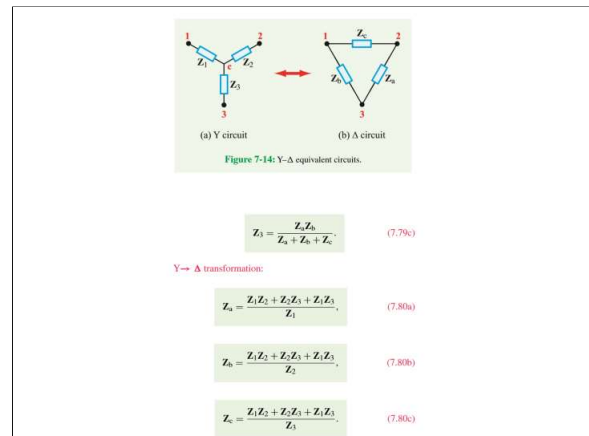
$$i_2(t) = 98 \text{ mA} e^{j143.2^\circ} = 98(7.4 \times 10^{-2} e^{-j143.2^\circ} e^{j107t}) = 7.4 \times 10^{-2} \cos(10^7 t - 143.2^\circ) \text{ A.}$$


$\Delta \rightarrow Y$ transformation:

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}, \quad (7.79a)$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}, \quad (7.79b)$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}. \quad (7.79c)$$

$\Delta \rightarrow Y$ transformation:

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \quad (7.79c)$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}, \quad (7.79b)$$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c} = \frac{-j6 \times 12}{24 - j12 - j6 + 12} = \frac{-j72}{36 - j18} = (0.8 - j1.6) \Omega,$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c} = \frac{(24 - j12) \times 12}{36 - j18} = 8 \Omega,$$

and

$$Z_3 = \frac{Z_b Z_a}{Z_a + Z_b + Z_c} = \frac{-j6(24 - j12)}{36 - j18} = -j4 \Omega.$$

In Fig. 7-15(c), Z_f represents the series combination of Z_3 and Z_d ,

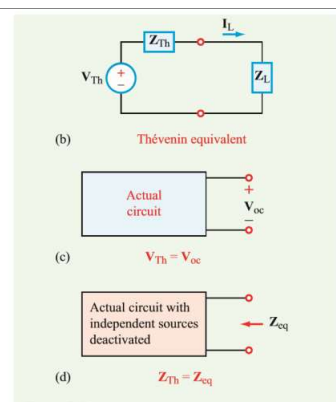
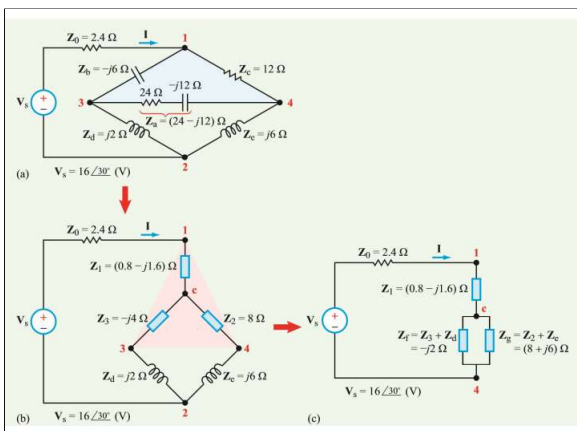


Figure 7-17: Thévenin-equivalent method for a circuit with no dependent sources.

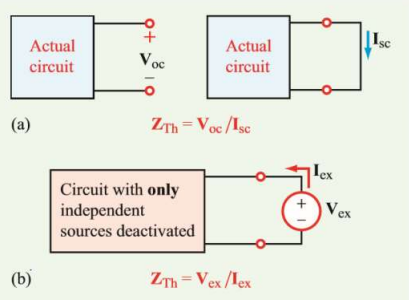


Figure 7-18: The (a) open-circuit/short-circuit method and (b) the external-source method are both suitable for determining Z_{Th} , whether or not the circuit contains dependent sources.

Open-circuit / short-circuit method

$$Z_{Th} = \frac{V_{oc}}{I_{sc}}, \quad (7.83)$$

where I_{sc} is the short-circuit current at the circuit's output terminals (**Fig. 7-18(a)**).

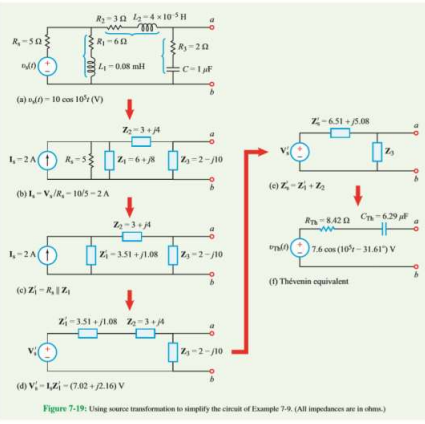


Figure 7-19: Using source transformation to simplify the circuit of Example 7-9. (All impedances are in ohms.)

Exercise 7-15: Write down the node-voltage matrix equation for the circuit in **Fig. E7.15**.

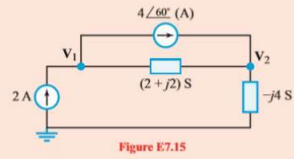


Figure E7.15

Answer:

$$\begin{bmatrix} (2+j2) & -(2+j2) \\ -(2+j2) & (2-j2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2-4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix}$$

(See **CAD**)

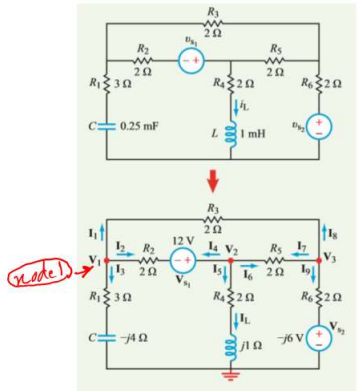


Figure 7-25: Circuit for Example 7-12 in (a) the time domain and (b) the phasor domain.

Example 7-12: Nodal Analysis

Apply the nodal-analysis method to determine $i_L(t)$ in the circuit of **Fig. 7-25(a)**. The sources are given by:

$$v_{s1}(t) = 12 \cos 10^3 t \text{ V,}$$

$$v_{s2}(t) = 6 \sin 10^3 t \text{ V.}$$

Solution: We first demonstrate how to solve this problem using the standard nodal-analysis method (Section 3-2), and then we solve it again by applying the by-inspection method (Section 3-4).

Nodal-analysis method

Our first step is to transform the given circuit to the phasor domain. Accordingly,

$$\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{-j}{10^3 \times 0.25 \times 10^{-3}} = -j4 \, \Omega,$$

$$\mathbf{Z}_L = j\omega L = j10^3 \times 10^{-3} = j1 \, \Omega,$$

$$v_{s1} = 12 \cos 10^3 t \quad \longleftrightarrow \quad \mathbf{V}_{s1} = 12 \, \text{V},$$

and

$$v_{s2} = 6 \sin 10^3 t \quad \longleftrightarrow \quad \mathbf{V}_{s2} = -j6 \, \text{V},$$

where for \mathbf{V}_{s2} we used the property given in **Table 7-2**, namely that the phasor counterpart of $\sin \omega t$ is $-j$. Using these values, we generate the phasor-domain circuit given in **Fig. 7-25(b)** in

which we selected one of the extraordinary nodes as a ground node and assigned phasor voltages \mathbf{V}_1 to \mathbf{V}_3 to the other three. Our plan is to write the voltage-node equations at nodes 1 to 3 to solve them simultaneously for \mathbf{V}_1 , \mathbf{V}_2 , and \mathbf{V}_3 , and then use the value of \mathbf{V}_1 to obtain \mathbf{i} . The final step will involve transforming \mathbf{i} to the time domain to obtain $i(t)$.

At node 1, KCL requires that

$$\mathbf{i}_1 + \mathbf{i}_2 + \mathbf{i}_3 = 0 \quad (7.105)$$

In terms of node voltages \mathbf{V}_1 to \mathbf{V}_3 ,

$$\mathbf{i}_1 = \frac{\mathbf{V}_1 - \mathbf{V}_2}{R_1} = \frac{\mathbf{V}_1 - \mathbf{V}_2}{2}$$

$$\mathbf{i}_2 = \frac{\mathbf{V}_1 - \mathbf{V}_2 + \mathbf{V}_3}{R_2} = \frac{\mathbf{V}_1 - \mathbf{V}_2 + \mathbf{V}_3 + 12}{2}$$

and

$$\mathbf{i}_3 = \frac{\mathbf{V}_1}{R_3 + j\omega L} = \frac{\mathbf{V}_1}{1 + j}$$

Inserting the expressions for \mathbf{i}_1 to \mathbf{i}_3 in Eq. (7.105) and then rearranging the terms leads to

$$\left(\frac{1}{2} + \frac{1}{2} + \frac{1}{1+j} \right) \mathbf{V}_1 - \frac{1}{2} \mathbf{V}_2 - \frac{1}{2} \mathbf{V}_3 = -6 \quad (7.106)$$

The coefficient of \mathbf{V}_1 can be simplified as follows:

$$\frac{1}{2} + \frac{1}{2} + \frac{1}{1+j} = \frac{1}{2} + \frac{1}{2} + \frac{1-j}{(1+j)(1-j)} = \frac{1}{2} + \frac{1}{2} + \frac{1-j}{2} = \frac{3-j}{2}$$

and

$$\frac{1}{1+j} = \frac{1-j}{(1+j)(1-j)} = \frac{1-j}{2}$$

Therefore, Eq. (7.106) can be written as

$$(2.5 - j) \mathbf{V}_1 - 0.5 \mathbf{V}_2 - 0.5 \mathbf{V}_3 = -6 \quad (7.107)$$

Inserting Eq. (7.107) in Eq. (7.104) and multiplying all terms by 2 leads to the following simplified algebraic equation for node 1:

$$(2.5 - j) \mathbf{V}_1 - 0.5 \mathbf{V}_2 - 0.5 \mathbf{V}_3 = -6 \quad (7.108)$$

Similarly, at node 2,

$$\frac{\mathbf{V}_2 - \mathbf{V}_1}{2} - \frac{\mathbf{V}_2 - \mathbf{V}_1 + \mathbf{V}_3}{2} + \frac{\mathbf{V}_2}{2} = 0$$

which can be simplified to

$$-\mathbf{V}_1 + (2.5 - j) \mathbf{V}_2 - \mathbf{V}_3 = 12 \quad (7.109)$$

and at node 3,

$$\frac{\mathbf{V}_3 - \mathbf{V}_2}{2} - \frac{\mathbf{V}_3 - \mathbf{V}_1 + \mathbf{V}_3}{2} + \frac{\mathbf{V}_3 + j6}{2} = 0$$

or

$$-\mathbf{V}_1 - \mathbf{V}_2 + 3\mathbf{V}_3 = -j6 \quad (7.110)$$

Equations (7.108) to (7.110) now are ready to be cast in matrix form:

$$\begin{bmatrix} 2.5 - j & -0.5 & -0.5 \\ -1 & 2.5 - j & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 12 \\ -j6 \end{bmatrix} \quad (7.111)$$

Matrix inversion either manually or by MATLAB or Mathcad provides the solution:

$$\mathbf{V}_1 = (-4.72 + j0.88) \, \text{V} \quad (7.112a)$$

$$\mathbf{V}_2 = (2.46 - j0.89) \, \text{V} \quad (7.112b)$$

and

$$\mathbf{V}_3 = (-0.36 + j2.39) \, \text{V} \quad (7.112c)$$

Hence,

$$\mathbf{i} = \frac{\mathbf{V}_1}{2 + j} = \frac{-4.72 + j0.88}{2 + j} = 0.81 - j0.85 = 1.17 \angle -46.7^\circ \, \text{A}$$

and its corresponding time-domain counterpart is

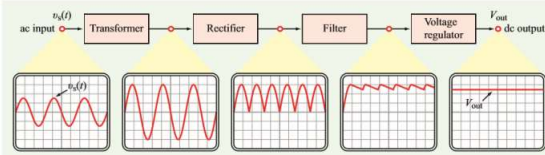
$$i(t) = 1.17 e^{j\omega t - 46.7^\circ} = 1.17 \cos(1000t - 46.7^\circ) \, \text{A}$$


Figure 7-35: Block diagram of a basic dc power supply.

11-2 Transformers

11-2.1 Coupling Coefficient

To couple magnetic flux between two coils, the coils may be wound around a common core (Fig. 11-7(a)), on two separate arms of a rectangular core (Fig. 11-7(b)), or in any other arrangement conducive to having a significant fraction of the magnetic flux generated by each coil shared with the other. The coupling coefficient k defines the degree of magnetic coupling between the coils, with $0 \leq k \leq 1$. For a *loosely coupled* pair of coils, $k < 0.5$; for *tightly coupled* coils, $k > 0.5$; and for *perfectly coupled* coils, $k = 1$. The magnitude of k depends on the physical geometry of the two-coil configuration and the magnetic permeability μ of the core material.

► A transformer is said to be *linear* if μ of its core material is a constant, independent of the magnitude of the currents flowing through the coils (and hence, the strength of the induced magnetic field).

Most core materials, including air, wood, and ceramics, are nonferromagnetic, and their μ is approximately equal to μ_0 , the permeability of free space. When nonferromagnetic materials are used for the common core around which the coils are wound, the magnitude of k depends entirely on how tightly coupled the two windings are. Such transformers are indeed linear, but the magnitude of k is seldom greater than 0.4. Increasing k requires the use of ferromagnetic cores, but the transformer becomes heavier in weight and its behavior becomes nonlinear. The degree of nonlinearity depends on the choice of materials. With certain types of purified iron, transformers can be designed to exhibit coupling coefficients approaching unity.

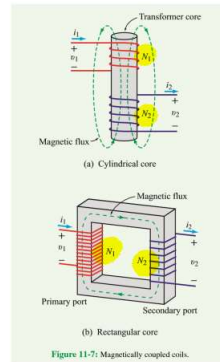


Figure 11-7: Magnetically coupled coils.

which can be cast in matrix form as

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \quad (11.27c)$$

(transformer)

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_x + L_y) & j\omega L_z \\ j\omega L_z & j\omega(L_x + L_y) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \quad (11.28)$$

(T-equivalent circuit)

The transformer and its T-equivalent circuit exhibit the same I-V relationships if the four terms in the matrix of Eq. (11.27)

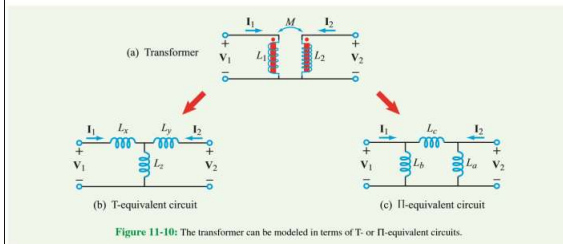


Figure 11-10: The transformer can be modeled in terms of T- or Pi-equivalent circuits.

Transformer dots on same ends

$$L_x = L_1 - M, \quad (11.29a)$$

$$L_y = L_2 - M, \quad (11.29b)$$

and

$$L_z = M. \quad (11.29c)$$

Had the transformer dots been located on opposite ends, the two terms involving M in Eq. (11.27) would have been preceded by minus signs. Consequently, the element values of inductors L_x , L_y , and L_z would be

Transformer dots on opposite ends


$$L_x = L_1 + M, \quad (11.30a)$$

$$L_y = L_2 + M, \quad (11.30b)$$

and

$$L_z = -M. \quad (11.30c)$$

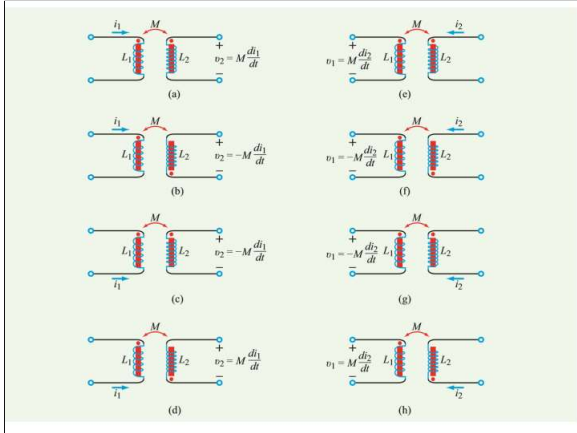Even though a negative value for inductance L_z is not physically realizable, the mathematical equivalency holds nonetheless and the equivalent circuit is perfectly applicable.




7-12.1 Ideal Transformers

A transformer consists of two inductors called **windings**, that are in close proximity to each other but not connected electrically. The two windings are called the **primary** and the **secondary**, as shown in Fig. 7-36. Even though the two windings are isolated electrically—meaning that no current flows between them—when an ac voltage is applied to the primary, it creates a magnetic flux that permeates both windings through a common **core**, inducing an ac voltage in the secondary.

► The **transformer** gets its name from the fact that it is used to **transform** currents, voltages, and impedances between its primary and secondary circuits. ◀

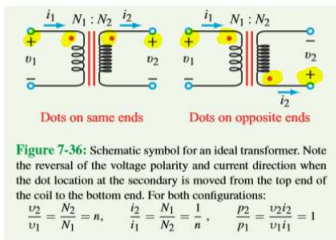The key parameter that determines the relationships between the primary and the secondary is the **turns ratio** $n = N_2/N_1$.





where N_1 is the number of turns in the primary coil and N_2 is the number of turns in the secondary. An additionally important attribute is the direction of the primary winding, relative to that of the secondary, around the common magnetic core. The relative directions determine the voltage polarity and current direction at the secondary, relative to those at the primary. To distinguish between the two cases, a dot usually is placed at one or the other end of each winding, as shown in Fig. 7-36. For the **ideal transformer**, voltage v_2 at the secondary side is related to voltage v_1 at the primary side by

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n. \quad (7.142)$$

where the polarities of v_1 and v_2 are defined such that their (+) terminals are at the ends with the dots. In an ideal transformer, no power is lost in the core, so all of the power supplied by a source to its primary coil is transferred to the load connected at its secondary side. Thus, $p_1 = p_2$, and since $p_1 = i_1 v_1$ and $p_2 = i_2 v_2$, it follows that

$$\frac{i_2}{i_1} = \frac{N_1}{N_2}. \quad (7.143)$$

with i_1 always defined in the direction towards the dot on the primary side and i_2 defined in the direction away from the dot on the secondary side. The purpose of the dot designation is to indicate whether the windings in the primary and secondary coils curl in the same (clockwise or counterclockwise) direction or in opposite directions. The coil directions determine the

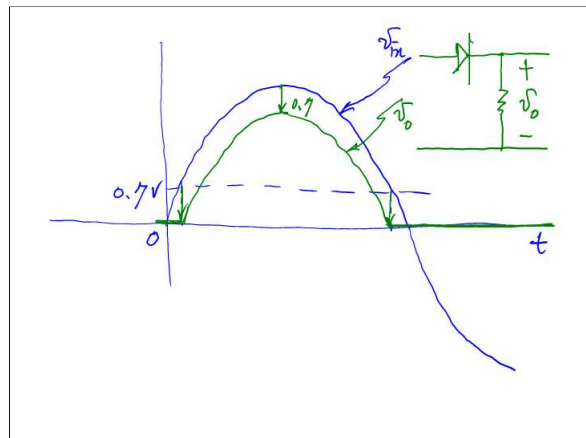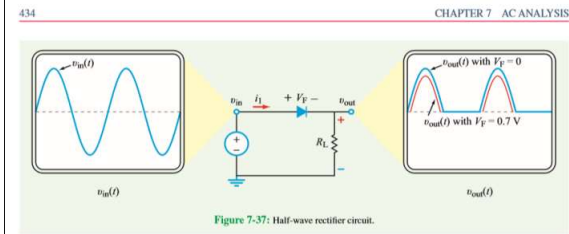

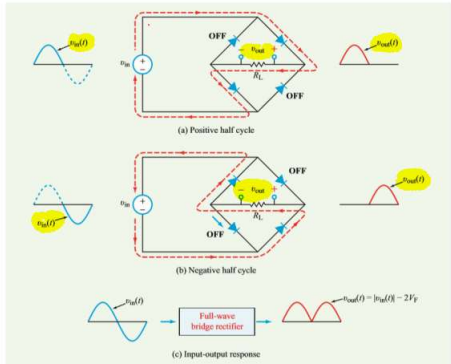


Figure 7-38: Full-wave bridge rectifier. Current flows in the same direction through the load resistor for both half cycles.


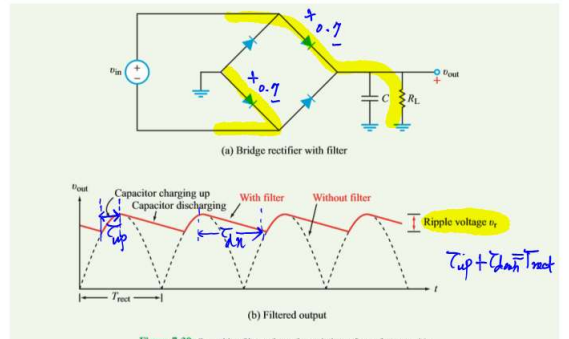


Figure 7-39: Smoothing filter reduces the variations of waveform $v_{out}(t)$.

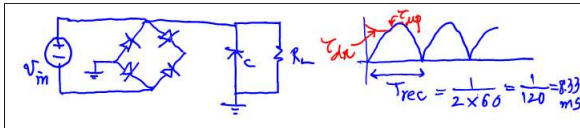

Example 7-19: Filter Design

If the bridge rectifier circuit of Fig. 7-39(a) has a 60 Hz ac input signal, determine the values of R_L and C that would result in $\tau_{up} = \tau_{down}/12$ and $\tau_{up} = 12T_{rect}$, where T_{rect} is the period of the rectified waveform. Assume $R_D = 5 \Omega$.

Solution: If the frequency of the original ac signal is 60 Hz, the frequency of the rectified waveform is 120 Hz. Hence, the period of the rectified waveform is

$$T_{rect} = \frac{1}{120} = 8.33 \text{ ms}$$

and the corresponding design specifications are

$$\tau_{up} = \frac{T_{rect}}{12} = 0.69 \text{ ms, and } \tau_{dn} = 12T_{rect} = 100 \text{ ms.}$$

Application of Eq. (7.145) leads to

$$\tau_{up} \approx 2R_L C$$

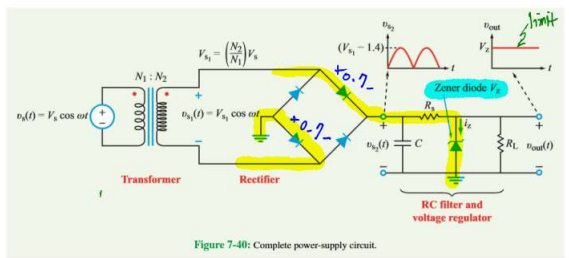


Figure 7-40: Complete power-supply circuit.

or

$$C = \frac{\tau_{up}}{2R_L} = \frac{0.69 \times 10^{-3}}{2 \times 5} = 69 \mu\text{F}$$

With the value of C known, application of Eq. (7.146) gives

$$R_L = \frac{\tau_{dn}}{C} = \frac{100 \times 10^{-3}}{69 \times 10^{-6}} = 1.45 \text{ k}\Omega$$

7-12.4 Voltage Regulator

The circuit shown in Fig. 7-40 includes all of the power-supply subcircuits we have discussed thus far, plus two additional elements, namely a series resistance R_s and a zener diode. When operated in reverse breakdown, the zener diode maintains the voltage across it at a constant level V_z —so long as the current passing through it remains between certain limits. Since the diode is connected in parallel with R_L , the output voltage becomes equal to the zener voltage V_z , and the effective time constant of the smoothing filter becomes $\tau = R_s C$. It is worth noting that the addition of the zener diode reduces the peak-to-peak ripple voltage V_r (Fig. 7-39(b)) at the output of

the RC filter by about an order of magnitude. An approximate expression for the peak-to-peak ripple voltage with the zener diode in place is given by

$$V_r = \frac{[(V_{s2} - 1.4) - V_z]T_{rect}}{R_s C} \times \frac{(R_s \parallel R_L)}{R_s + (R_s \parallel R_L)} \quad (7.147)$$

where V_{s2} is the amplitude of the ac signal at the output of the transformer (Fig. 7-40), the factor 1.4 V accounts for the voltage drop across a pair of diodes in the rectifier, V_z is the manufacturer-rated zener voltage for the specific model used in the circuit, T_{rect} is the period of the rectified waveform, and R_L is the manufacturer specified value of the zener-diode resistance.

Example 7-20: Power-Supply Design

A power supply with the circuit configuration shown in Fig. 7-40 has the following specifications: the input voltage is 60 Hz with an rms amplitude $V_{ms} = 110 \text{ V}$ where $V_{rms} = V_m/\sqrt{2}$ (the rms value of a sinusoidal function is

Time constant of the smoothing filter

$$\tau = R_s C = 50 \times 69 \times 10^{-6} = 3.45 \text{ ms}$$

$\tau \approx 50 \mu\text{s}$

discussed in Chapter 8), $N_1/N_2 = 5$, $C = 2 \text{ mF}$, $R_s = 50 \Omega$, $R_L = 1 \text{ k}\Omega$, $V_z = 24 \text{ V}$, and $R_D = 20 \Omega$. Determine v_{out} , the ripple voltage, and the ripple fraction relative to v_{out} .

Solution: At the secondary side of the transformer,

$$v_{s2}(t) = \left(\frac{N_2}{N_1}\right) (V_s \cos 377t) = \frac{1}{5} \times 110\sqrt{2} \cos 377t = 31.11 \cos 377t \text{ V.}$$

Hence, $V_{s2} = 31.11 \text{ V}$, which is greater than the zener voltage $V_z = 24 \text{ V}$.

Consequently, the zener diode will limit the output voltage at

$$v_{out} = V_z = 24 \text{ V.}$$

In Example 7-19, we established that $T_{rect} = 8.33 \text{ ms}$. Also,

$$R_s \parallel R_L = \frac{20 \times 1000}{20 + 1000} = 19.6 \Omega.$$

Application of Eq. (7.147) gives

$$V_r = \frac{[(V_{s2} - 1.4) - V_z]T_{rect}}{R_s C} \times \frac{(R_s \parallel R_L)}{R_s + (R_s \parallel R_L)} = \frac{[(31.11 - 1.4) - 24] \times 8.33 \times 10^{-3}}{50 \times 2 \times 10^{-3}} \times \frac{19.6}{50 + 19.6} = 0.13 \text{ V (peak-to-peak).}$$

Hence,

$$\text{ripple fraction} = \frac{(V_r/2)}{V_o} = \frac{0.13/2}{24} = 0.0027,$$

which represents a relative variation of less than ± 0.3 percent.

