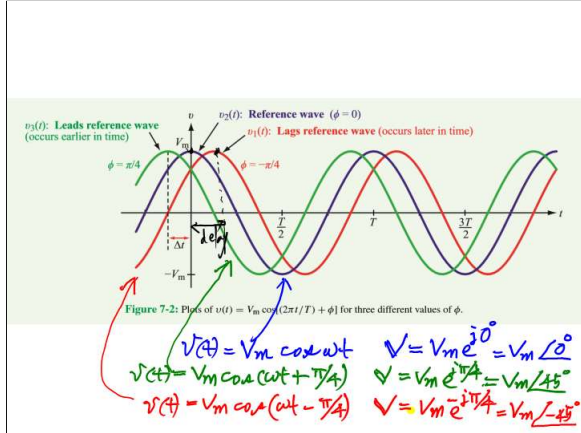


EE101 W19 Lecture 18, May 7, 2019
 HW #9 for Quiz 9 on May 12

[1] 6.29 [6] 7.1
 [2] 6.35 [7] 7.10 (a), (b), (c)
 [3] 6.38 [8] 7.22
 [4] 6.50 [9] 7.36
 [5] 6.54 [10] 7.86

Quiz 8 Average = 9.00
 20 = 1.59



$\frac{d}{dt} \leftrightarrow j\omega$ (7.37)

time derivative, and vice versa. We surmise from Eq. (7.36) that

or

Differentiation of a time function $i(t)$ in the time domain is equivalent to multiplication of its phasor counterpart I by $j\omega$ in the phasor domain.

Similarly,

$$\int i dt = \int \Re\{Ie^{j\omega t}\} dt = \Re\left\{ \int Ie^{j\omega t} dt \right\} = \Re\left\{ \frac{1}{j\omega} Ie^{j\omega t} \right\}$$

phasor of $\int i dt$

or

$$\int i dt \leftrightarrow \frac{1}{j\omega} I$$

(7.39)

$i_R = \Re\{I_R e^{j\omega t}\}$ (7.41b)

$x(t)$	X
$A \cos \omega t$	A
$A \cos(\omega t + \phi)$	$Ae^{j\phi}$
$-A \cos(\omega t + \phi)$	$Ae^{j(\phi \pm \pi)}$
$A \sin \omega t$	$Ae^{-j\pi/2} = -jA$
$A \sin(\omega t + \phi)$	$Ae^{j(\phi - \pi/2)}$
$-A \sin(\omega t + \phi)$	$Ae^{j(\phi + \pi/2)}$
$\frac{d}{dt} x(t)$	$j\omega X$
$\frac{d}{dt} [A \cos(\omega t + \phi)]$	$j\omega Ae^{j\phi}$
$\int x(t) dt$	$\frac{1}{j\omega} X$
$\int A \cos(\omega t + \phi) dt$	$\frac{1}{j\omega} Ae^{j\phi}$

$x(t)$	X
$A \cos \omega t$	A
$A \cos(\omega t + \phi)$	$Ae^{j\phi}$
$-A \cos(\omega t + \phi)$	$Ae^{j(\phi \pm \pi)}$
$A \sin \omega t$	$Ae^{-j\pi/2} = -jA$
$A \sin(\omega t + \phi)$	$Ae^{j(\phi - \pi/2)}$
$-A \sin(\omega t + \phi)$	$Ae^{j(\phi + \pi/2)}$
$\frac{d}{dt} x(t)$	$j\omega X$
$\frac{d}{dt} [A \cos(\omega t + \phi)]$	$j\omega Ae^{j\phi}$
$\int x(t) dt$	$\frac{1}{j\omega} X$
$\int A \cos(\omega t + \phi) dt$	$\frac{1}{j\omega} Ae^{j\phi}$

Property	R	L	C
v - i	$v = Ri$	$v = L \frac{di}{dt}$	$i = C \frac{dv}{dt}$
V - I	$V = RI$	$V = j\omega LI$	$V = \frac{1}{j\omega C} I$
Z	R	$j\omega L$	$\frac{1}{j\omega C}$
dc equivalent	Short circuit	Open circuit	Open circuit
High-frequency equivalent	Open circuit	Short circuit	Short circuit
Frequency response	$ Z_R = R$	$ Z_L = \omega L$	$ Z_C = 1/\omega C$

phasor domain circuit analysis

Step 1: Adopt Cosine Reference (Time Domain)
 $v_s(t) = 12 \sin(\omega t - 45^\circ)$ (V)



Step 2: Transfer to Phasor Domain
 $v_s = 12 \angle -45^\circ$ (V)
 $R = 12 \angle 0^\circ$ (Ω)
 $Z_C = \frac{1}{j\omega C} = -6 \angle -90^\circ$ (Ω)
 $Z = 12 \angle -45^\circ - 6 \angle -90^\circ = 12 \cos(\omega t - 45^\circ - 90^\circ) = 12 \cos(\omega t - 135^\circ)$

Step 3: Cast Equations in Phasor Form
 $I(R + \frac{1}{j\omega C}) = V_s$ Mesh analysis KVL

Step 4: Solve for Unknown Variable (Phasor Domain)
 $I = \frac{V_s}{R + \frac{1}{j\omega C}}$
 $I = \frac{12 \angle -45^\circ}{12 \angle 0^\circ - 6 \angle -90^\circ} = \frac{12 \angle -45^\circ}{12 \angle -45^\circ} = 1 \angle 0^\circ$ (mA)


Step 5: Transform Solution Back to Time Domain
 $i(t) = \Re\{Ie^{j\omega t}\} = 1 \cos(\omega t - 105^\circ)$ (mA)

Figure 7-7: Five-step procedure for analyzing ac circuits using the phasor-domain technique.

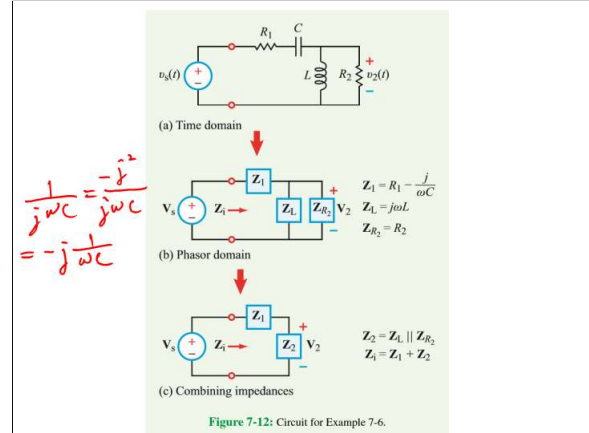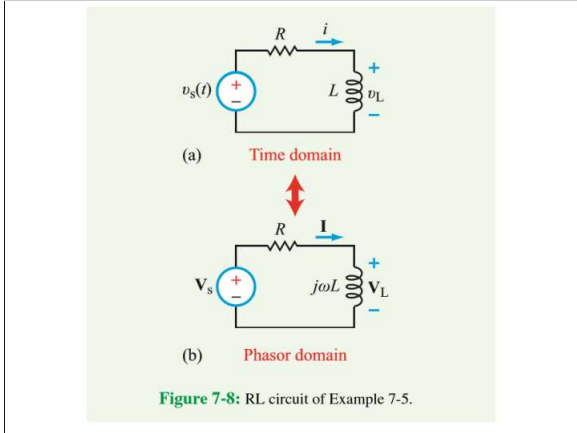

$$\frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$= -j\frac{1}{\omega C}$$

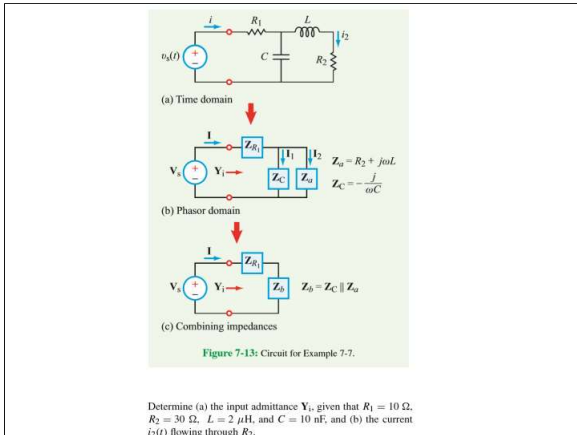

Determine (a) the input admittance Y_i , given that $R_1 = 10 \Omega$, $R_2 = 30 \Omega$, $L = 2 \mu\text{H}$, and $C = 10 \text{ nF}$; and (b) the current $i_2(t)$ flowing through R_2 .

Solution: (a) We start by converting $v_s(t)$ to cosine format:

$$v_s(t) = 4 \sin(10^7 t + 15^\circ)$$

$$= 4 \cos(10^7 t + 15^\circ - 90^\circ) = 4 \cos(10^7 t - 75^\circ) \text{ V.}$$

The corresponding phasor voltage is

$$V_s = 4e^{-j75^\circ} \text{ V,}$$

and the impedances shown in **Fig. 7-13(b)** are given by

$$Z_{R1} = R_1 = 10 \Omega,$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{10^7 \times 10^{-8}} = -j10 \Omega,$$

$Z_a = R_2 + j\omega L = 30 + j10^7 \times 2 \times 10^{-6} = (30 + j20) \Omega$.

In **Fig. 7-13(c)**, Z_a represents the parallel combination of Z_C and Z_a .

$$Z_a = Z_C \parallel Z_a = \frac{(-j10)(30 + j20)}{-j10 + 30 + j20} = \frac{20 - j30}{3 + j1} = \frac{(20 - j30)(3 - j1)}{(3 + j1)(3 - j1)} = \frac{3 - j11}{5} = (0.6 - j2.2) \Omega.$$

The input impedance is

$$Z_i = Z_{R1} + Z_a = 10 + 0.6 - j2.2 = (10.6 - j2.2) \Omega,$$

and its reciprocal is

$$Y_i = \frac{1}{Z_i} = \frac{1}{10.6 - j2.2} = \frac{10.6 + j2.2}{(10.6)^2 + (2.2)^2} = \frac{10.6 + j2.2}{116.44} = (0.091 + j0.019) \text{ S} = 9.1 \times 10^{-2} + j1.9 \times 10^{-2} \text{ S}.$$

(b) The current I is given by

$$I = V_s Y_i = (4e^{-j75^\circ})(9.1 \times 10^{-2} + j1.9 \times 10^{-2}) = 0.235e^{-j14.8^\circ} \text{ A}.$$

By current division in **Fig. 7-13(b)**,

$$I_2 = \frac{Z_C}{Z_a + Z_C} I = \frac{-j10}{30 + j20 - j10} (0.235e^{-j14.8^\circ}) = \frac{2.35e^{-j14.8^\circ} e^{-j90^\circ}}{31.62 \angle 33.7^\circ} = 7.4 \times 10^{-2} e^{-j104.2^\circ} \text{ A}.$$

The corresponding current in the time domain is

$$i_2(t) = \Re\{I_2 e^{j\omega t}\} = \Re\{7.4 \times 10^{-2} e^{-j104.2^\circ} e^{j10^7 t}\} = 7.4 \times 10^{-2} \cos(10^7 t - 143.2^\circ) \text{ A}.$$

$$Z_C \parallel Z_a = \frac{Z_C Z_a}{Z_C + Z_a}$$

$$R_C \parallel R_a = \frac{R_C \cdot R_a}{R_C + R_C}$$

$$\cos(\theta - 90^\circ) = \cos \theta \cos 90^\circ + \sin \theta \sin 90^\circ = \sin \theta$$

$$\cos(\theta + 90^\circ) = \cos \theta \cos 90^\circ - \sin \theta \sin 90^\circ = -\sin \theta$$

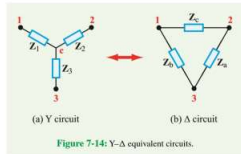


Figure 7-14: Y-Δ equivalent circuits.

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c} \quad (7.79c)$$

Y → Δ transformation:

$$z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1} \quad (7.80a)$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2} \quad (7.80b)$$

$$z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3} \quad (7.80c)$$

Δ → Y transformation:

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}, \quad (7.79a)$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}, \quad (7.79b)$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \quad (7.79c)$$

Δ → Y transformation:

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \quad (7.79c)$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}, \quad (7.79b)$$


$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c} = \frac{-j6 \times 12}{24 - j12 - j6 + 12} = \frac{-j72}{36 - j18} = (0.8 - j1.6) \Omega,$$



$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c} = \frac{(24 - j12) \times 12}{36 - j18} = 8 \Omega,$$

and

$$Z_3 = \frac{Z_b Z_a}{Z_a + Z_b + Z_c} = \frac{-j6(24 - j12)}{36 - j18} = -j4 \Omega.$$

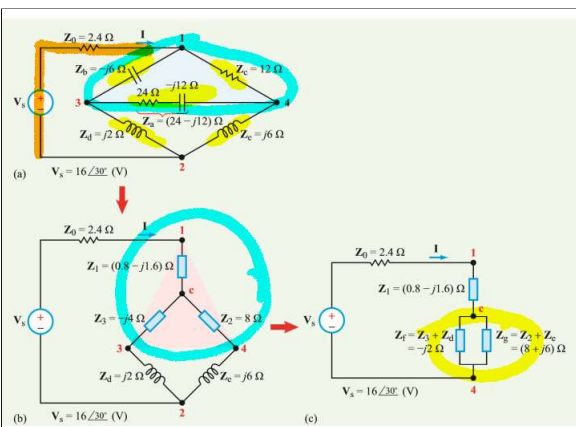In Fig. 7-15(c), Z_f represents the series combination of Z_3 and Z_d .





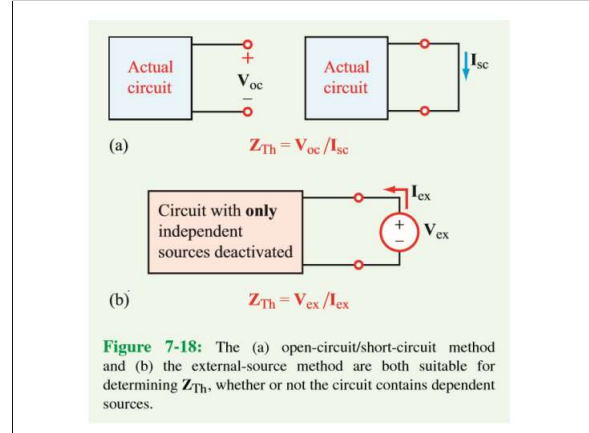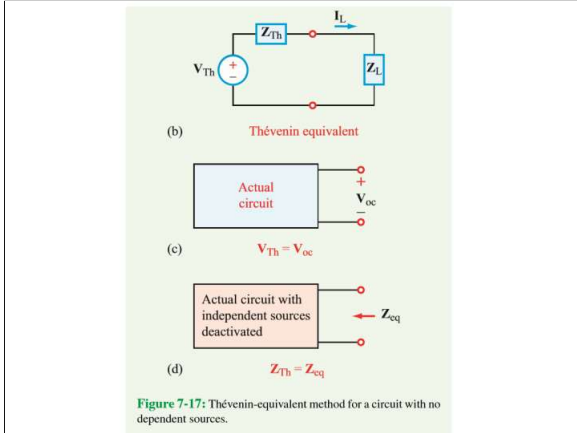

Open-circuit / short-circuit method

$$Z_{Th} = \frac{V_{oc}}{I_{sc}} \quad (7.83)$$

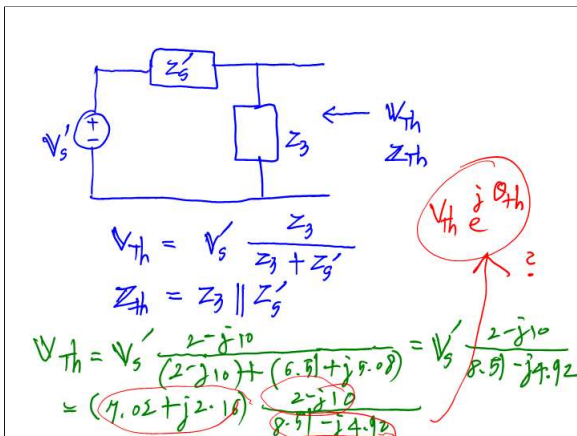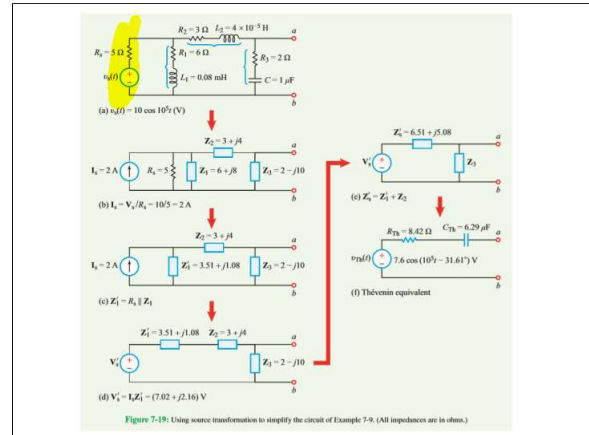where I_{sc} is the short-circuit current at the circuit's output terminals (**Fig. 7-18(a)**).



complex number coordinate

$$\frac{(a+jb)(c+jd)}{(e+jf)(e-jf)} = \frac{(a+jb)(c+jd)(e-jf)}{(e+jf)(e-jf)} = \frac{\dots}{(e^2+f^2)}$$

$$= \alpha + j\beta \Rightarrow \sqrt{\alpha^2 + \beta^2} \angle \tan^{-1}\left(\frac{\beta}{\alpha}\right)$$


$$r + jb = \sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a} = M_1 e^{j\theta_1}$$

$$c + jd = \sqrt{c^2 + d^2} \angle \tan^{-1} \frac{d}{c} = M_2 e^{j\theta_2}$$

$$e + jf = \sqrt{e^2 + f^2} \angle \tan^{-1} \frac{f}{e} = M_3 e^{j\theta_3}$$

$$\Rightarrow \frac{M_1 \cdot M_2}{M_3} e^{j(\theta_1 + \theta_2 - \theta_3)}$$

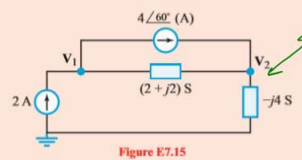Exercise 7-15: Write down the node-voltage matrix equation for the circuit in Fig. E7.15.



Answer:

$$\begin{bmatrix} (2+j2) & -(2+j2) \\ -(2+j2) & (2-j2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 - 4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix}$$
 (See CAD)

$$KCL \uparrow / 60^\circ$$

$$= V_2(-j4)$$

$$+ (V_1 - V_2)(2+j2)$$

$$= -V_1(2+j2)$$

$$+ V_2(2+j2-j4)$$

$$2-j2$$

$$A = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \quad A^{-1} = \frac{1}{|A|} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$B = \begin{bmatrix} 2 & 4 \\ 1 & 3 \end{bmatrix} \quad B^{-1} = \frac{1}{2} \begin{bmatrix} 3 & -4 \\ -1 & 2 \end{bmatrix}$$

$$|B| = (2)(3) - (4)(1) = 6 - 4 = 2$$

$$|B| = 6 - 4 = 2$$

$$B^{-1} = \frac{1}{2} \begin{bmatrix} 3 & -4 \\ -1 & 2 \end{bmatrix} = \begin{bmatrix} 1.5 & -2 \\ -0.5 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 2+j2 & -(2+j2) \\ -(2+j2) & (2-j2) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 - 4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2+j2 & -(2+j2) \\ -(2+j2) & (2-j2) \end{bmatrix}^{-1} \begin{bmatrix} 2 - 4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix}$$

$$\det A = (2+j2)(2-j2) - (-(2+j2)(2+j2))$$

$$= 2(2) + j(-j)2(2) - (-(2+j2)(2+j2))$$

$$= 4 - (-4)4 - (4 + j4 + j4 + j^24) = 8 - (0 + j8) = 8 - j8$$

$$A^{-1} = \frac{1}{8-j8} \begin{bmatrix} (2-j2) & (2+j2) \\ (2+j2) & (2+j2) \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = A^{-1} \begin{bmatrix} 2 - 4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix} = \frac{1}{8-j8} \begin{bmatrix} (2-j2)(2+j2) & (2-j2)(2+j2) \\ (2+j2)(2+j2) & (2+j2)(2+j2) \end{bmatrix} \begin{bmatrix} 2 - 4e^{j60^\circ} \\ 4e^{j60^\circ} \end{bmatrix}$$

$$= \frac{1}{8-j8} \begin{bmatrix} (2-j2)(-j2\sqrt{3}) + (2+j2)(2+j2\sqrt{3}) \\ (2+j2)(-j2\sqrt{3}) + (2+j2)(2+j2\sqrt{3}) \end{bmatrix}$$

$$= \frac{1}{8-j8} \begin{bmatrix} -j4\sqrt{3} - 4\sqrt{3} + 4 + j4\sqrt{3} + j4 - 4\sqrt{3} \\ -j4\sqrt{3} + 4\sqrt{3} + 4 + j4\sqrt{3} + j4 - 4\sqrt{3} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{(4-8\sqrt{3}) + j4}{8-j8} \\ \frac{4+j4}{8-j8} \end{bmatrix} = \frac{1}{2} \begin{bmatrix} \frac{(1-2\sqrt{3}) + j1}{2-j2} \\ \frac{1+j1}{1-j1} \end{bmatrix}$$

$$= \frac{1}{2} \begin{bmatrix} \frac{(1-2\sqrt{3} + j)(2+j2)}{(\sqrt{2}e^{j45^\circ})^2 - 2e^{j90^\circ}} \\ \frac{(1+j)(1+j1)}{(1-j)(1+j1)} \end{bmatrix}$$

$$z = 2$$

$$= \frac{1}{2} \begin{bmatrix} \frac{((1-2\sqrt{3}) + j)(2+j2)}{8-j4} \\ j \end{bmatrix} = \frac{1}{2} \begin{bmatrix} \frac{-\sqrt{3} + j(1-\sqrt{3})}{2-j} \\ j \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{2} \frac{-\sqrt{3} - j(\sqrt{3}-1)}{2-j} \\ \frac{1}{2} j \end{bmatrix} = \begin{bmatrix} \frac{1}{2} (1.88) e^{j(-159.1^\circ)} \\ \frac{1}{2} e^{j90^\circ} \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\theta_x = \tan^{-1} \frac{\sqrt{3}-1}{\sqrt{3}} = \tan^{-1} 0.423 = 0.4 \text{ rad} = 22.9^\circ$$

$$\begin{bmatrix} 1 & 5 & -4 \\ -1 & -3 & 6 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 5 \end{bmatrix}. \quad (\text{B.4})$$

Note that $a_{11} = 1$, $a_{21} = -1$, and $a_{33} = 0$. The regularized set of three linear, simultaneous equations given by Eq. (B.4) is a system of order 3.

Step 2: General Solution

According to Cramer's rule, the solutions for i_1 to i_3 are given by

$$i_1 = \frac{\Delta_1}{\Delta}, \quad (\text{B.5a})$$

$$i_2 = \frac{\Delta_2}{\Delta}, \quad (\text{B.5b})$$

$$i_3 = \frac{\Delta_3}{\Delta}, \quad (\text{B.5c})$$

$$\mathbf{I} = \mathbf{A}^{-1}\mathbf{B}, \quad (\text{B.22})$$

where \mathbf{A}^{-1} is the *inverse* of matrix \mathbf{A} . The inverse of a square matrix is given by

$$\mathbf{A}^{-1} = \frac{\text{adj } \mathbf{A}}{\Delta}, \quad (\text{B.23})$$

where $\text{adj } \mathbf{A}$ is the *adjoint* of \mathbf{A} and Δ is the determinant of \mathbf{A} . The adjoint of \mathbf{A} is obtained from \mathbf{A} by replacing each element a_{jk} with its cofactor C_{jk} , and then *transposing* the resultant matrix, wherein the rows and columns are interchanged. Thus,

$$\text{adj } \mathbf{A} = [C_{jk}]^T. \quad (\text{B.24})$$

To illustrate the matrix solution method, let us return to the three simultaneous equations given by Eq. (B.3). Matrices \mathbf{A} and \mathbf{B} are given by

$$\mathbf{A} = \begin{bmatrix} 1 & 5 & -4 \\ -1 & -3 & 6 \\ 1 & -1 & 0 \end{bmatrix}, \quad (\text{B.25a})$$

$$\mathbf{B} = \begin{bmatrix} 10 \\ 0 \\ 5 \end{bmatrix}. \quad (\text{B.25b})$$

According to Eq. (B.24), $\text{adj } \mathbf{A}$ is given by

$$\text{adj } \mathbf{A} = \begin{bmatrix} C_{11} & C_{12} & C_{13} \\ C_{21} & C_{22} & C_{23} \\ C_{31} & C_{32} & C_{33} \end{bmatrix}^T = \begin{bmatrix} C_{11} & C_{21} & C_{31} \\ C_{12} & C_{22} & C_{32} \\ C_{13} & C_{23} & C_{33} \end{bmatrix}. \quad (\text{B.26})$$

Each cofactor is a 2×2 determinant. Application of the definition given by Eq. (B.9) leads to

$$\text{adj } \mathbf{A} = \begin{bmatrix} 6 & 4 & 18 \\ 6 & 4 & -2 \\ 4 & 6 & 2 \end{bmatrix}. \quad (\text{B.27})$$

Upon incorporating Eqs. (B.22) and (B.23) and using the value of Δ obtained in Eq. (B.13), we have

$$\mathbf{I} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \frac{1}{20} \begin{bmatrix} 6 & 4 & 18 \\ 6 & 4 & -2 \\ 4 & 6 & 2 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 5 \end{bmatrix}. \quad (\text{B.28})$$

Standard matrix multiplication leads to

$$i_1 = \frac{1}{20} [6 \ 4 \ 18] \begin{bmatrix} 10 \\ 0 \\ 5 \end{bmatrix} = \frac{1}{20} (6 \times 10 + 4 \times 0 + 18 \times 5) = 7.5. \quad (\text{B.29})$$

Similarly, multiplication using the second and third rows of $\text{adj } \mathbf{A}$ leads to $i_2 = i_3 = 2.5$.

Method 1: Creating the Adjugate Matrix to Find the Inverse Matrix

$$M = \begin{bmatrix} 1 & 2 & 3 \\ 0 & 1 & 4 \\ 5 & 6 & 0 \end{bmatrix}$$

$$\begin{aligned} \det(M) &= 1(0-24) - 2(0-20) \\ &\quad + 3(0-5) \\ &= 1 \end{aligned}$$

$$M = \begin{bmatrix} 1 & 2 & 3 \\ 0 & 1 & 4 \\ 5 & 6 & 0 \end{bmatrix}$$

$$M^T = \begin{bmatrix} 1 & 0 & 5 \\ 2 & 1 & 6 \\ 3 & 4 & 0 \end{bmatrix}$$

$$M^T = \begin{bmatrix} 1 & 0 & 5 \\ 2 & 1 & 6 \\ 3 & 4 & 0 \end{bmatrix}$$


$$\begin{vmatrix} 1 & 6 \\ 4 & 0 \end{vmatrix} = -24 \quad \begin{vmatrix} 2 & 6 \\ 3 & 0 \end{vmatrix} = -18 \quad \begin{vmatrix} 2 & 1 \\ 3 & 4 \end{vmatrix} = 5$$

$$\begin{vmatrix} 0 & 5 \\ 4 & 0 \end{vmatrix} = -20 \quad \begin{vmatrix} 1 & 5 \\ 3 & 0 \end{vmatrix} = -15 \quad \begin{vmatrix} 1 & 0 \\ 3 & 4 \end{vmatrix} = 4$$

$$\begin{vmatrix} 0 & 5 \\ 1 & 6 \end{vmatrix} = -5 \quad \begin{vmatrix} 1 & 5 \\ 2 & 6 \end{vmatrix} = -4 \quad \begin{vmatrix} 1 & 0 \\ 2 & 1 \end{vmatrix} = 1$$

$$\text{Adj}(M) = \begin{bmatrix} -24 & -18 & 5 \\ -20 & -15 & 4 \\ -5 & -4 & 1 \end{bmatrix} \times \begin{bmatrix} + & - & + \\ - & + & - \\ + & - & + \end{bmatrix}$$

$$\text{Adj}(M) = \begin{bmatrix} -24 & 18 & 5 \\ 20 & -15 & -4 \\ -5 & 4 & 1 \end{bmatrix}$$

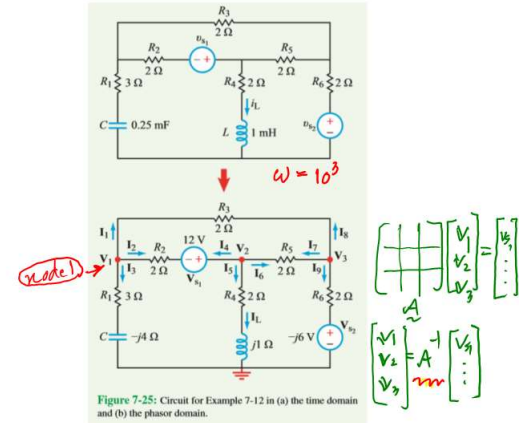

Example 7-12: Nodal Analysis

Apply the nodal-analysis method to determine $i_1(t)$ in the circuit of Fig. 7-25(a). The sources are given by:

$$v_{s1}(t) = 12 \cos 10^3 t \text{ V},$$

$$v_{s2}(t) = 6 \sin 10^3 t \text{ V}.$$

Handwritten:
 $v_{s1} = 12 \angle 0^\circ$
 $v_{s2} = 6 \angle -90^\circ$

Solution: We first demonstrate how to solve this problem using the standard nodal-analysis method (Section 3-2), and then we solve it again by applying the by-inspection method (Section 3-4).

Nodal-analysis method

Our first step is to transform the given circuit to the phasor domain. Accordingly,

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{10^3 \times 0.25 \times 10^{-3}} = -j4 \Omega,$$

$$Z_L = j\omega L = j10^3 \times 10^{-3} = j1 \Omega,$$

$$v_{s1} = 12 \cos 10^3 t \iff \mathbf{V}_{s1} = 12 \text{ V},$$

and

$$v_{s2} = 6 \sin 10^3 t \iff \mathbf{V}_{s2} = -j6 \text{ V},$$

where for \mathbf{V}_{s2} we used the property given in Table 7-2, namely that the phasor counterpart of $\sin \omega t$ is $-j$. Using these values, we generate the phasor-domain circuit given in Fig. 7-25(b) in

which we selected one of the extraordinary nodes as a ground node and assigned phasor voltages \mathbf{V}_1 to \mathbf{V}_3 to the other three. Our plan is to write the voltage-node equations at nodes 1 to 3, solve them simultaneously to find \mathbf{V}_1 , \mathbf{V}_2 , and then use the value of \mathbf{V}_1 to obtain i_1 . The final step will involve transforming i_1 to the time domain to obtain $i_1(t)$.

At node 1, KCL requires that

$$i_1 + i_2 + i_3 = 0 \quad (7.105)$$

In terms of node voltages \mathbf{V}_1 to \mathbf{V}_3 ,

$$i_1 = \frac{\mathbf{V}_1 - \mathbf{V}_2}{R_1} = \frac{\mathbf{V}_1 - \mathbf{V}_2}{3}$$

$$i_2 = \frac{\mathbf{V}_1 - \mathbf{V}_2 + \mathbf{V}_{s1}}{R_2} = \frac{\mathbf{V}_1 - \mathbf{V}_2 + 12}{2}$$

and

$$i_3 = \frac{\mathbf{V}_1 - \mathbf{V}_3}{R_3} = \frac{\mathbf{V}_1 - \mathbf{V}_3}{2}$$

Inserting the expressions for i_1 to i_3 in Eq. (7.105) and then rearranging the terms leads to

$$\left(\frac{1}{3} + \frac{1}{2} + \frac{1}{2}\right)\mathbf{V}_1 - \frac{1}{2}\mathbf{V}_2 - \frac{1}{2}\mathbf{V}_3 = -6 \quad (7.106)$$

The coefficient of \mathbf{V}_1 can be simplified as follows:

$$\frac{1}{3} + \frac{1}{2} + \frac{1}{2} = \frac{1}{3} + \frac{1}{1} = \frac{1}{3} + \frac{3}{3} = \frac{4}{3}$$

$$\frac{4}{3}\mathbf{V}_1 - \frac{1}{2}\mathbf{V}_2 - \frac{1}{2}\mathbf{V}_3 = -6 \quad (7.106)$$

Inserting Eq. (7.105) in Eq. (7.106) and multiplying all terms by 2 leads to the following simplified algebraic equation for node 1:

$$2(2.67 + j0.33)\mathbf{V}_1 - \mathbf{V}_2 - \mathbf{V}_3 = -12 \quad (7.107)$$

Node 2:

$$\mathbf{V}_2 - \mathbf{V}_1 - 12 = \frac{\mathbf{V}_2 - \mathbf{V}_1 + 12}{2} \implies \mathbf{V}_2 - \mathbf{V}_1 - 12 = \frac{\mathbf{V}_2 - \mathbf{V}_1}{2} + 6$$

which can be simplified to

$$-\mathbf{V}_1 + (2.5 - j0.49)\mathbf{V}_2 - \mathbf{V}_3 = 12 \quad (7.108)$$

and at node 3:

$$-\mathbf{V}_1 - \mathbf{V}_2 + 3\mathbf{V}_3 = -j6 \quad (7.109)$$

Equations (7.107) to (7.109) now are ready to be cast in matrix form:

$$\begin{bmatrix} 2.67 + j0.33 & -1 & -1 \\ -1 & 2.5 - j0.49 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \\ \mathbf{V}_3 \end{bmatrix} = \begin{bmatrix} -12 \\ 12 \\ -j6 \end{bmatrix}$$

Matrix inversion, either manually or by MATLAB or Mathcad, provides the solution:

$$\mathbf{V}_1 = (-4.72 + j0.88) \text{ V} \quad (7.110)$$

$$\mathbf{V}_2 = (2.46 - j0.89) \text{ V} \quad (7.110a)$$


$$\mathbf{V}_3 = (-0.26 + j2.96) \text{ V} \quad (7.110b)$$

Hence,

$$i_1 = \frac{\mathbf{V}_1 - \mathbf{V}_2}{3} = \frac{2.46 - j0.89 - (-4.72 + j0.88)}{3} = \frac{7.18 - j1.77}{3} = 2.39 - j0.59 \text{ A}$$

and its corresponding time-domain counterpart is
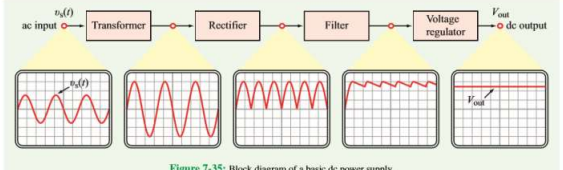
$$i_1(t) = 766.8 e^{j(1000t - 10.7^\circ)} = 766.8 \cos(1000t - 10.7^\circ) \text{ A}$$



11-2 Transformers

11-2.1 Coupling Coefficient

To couple magnetic flux between two coils, the coils may be wound around a common core (Fig. 11-7(a)), on two separate arms of a rectangular core (Fig. 11-7(b)), or in any other arrangement conducive to having a significant fraction of the magnetic flux generated by each coil shared with the other. The *coupling coefficient* k defines the degree of magnetic coupling between the coils, with $0 \leq k \leq 1$. For a *tightly coupled* pair of coils, $k < 0.5$; for *loosely coupled* coils, $k > 0.5$; and for *perfectly coupled* coils, $k = 1$. The magnitude of k depends on the physical geometry of the two-coil configuration and the magnetic permeability μ of the core material.

► A transformer is said to be *linear* if μ of its core material is a constant, independent of the magnitude of the currents flowing through the coils (and hence, the strength of the induced magnetic field). ◀

Most core materials, including air, wood, and ceramics, are nonferromagnetic, and their μ is approximately equal to μ_0 , the *permeability of free space*. When nonferromagnetic materials are used for the common core around which the coils are wound, the magnitude of k depends entirely on how tightly coupled the two windings are. Such transformers are indeed linear, but the magnitude of k is seldom greater than 0.4. Increasing k requires the use of ferromagnetic cores, but the transformer becomes heavier in weight and its behavior becomes nonlinear. The degree of nonlinearity depends on the choice of materials. With certain types of powdered-iron transformers can be designed to exhibit coupling coefficients approaching unity.

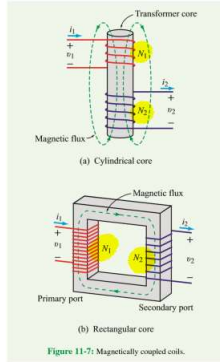


Figure 11-7: Magnetically coupled coils.

which can be cast in matrix form as

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad (11.27c)$$

(transformer)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_1 + L_2) & j\omega L_2 \\ j\omega L_2 & j\omega(L_1 + L_2) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad (11.28)$$

(T-equivalent circuit)

The transformer and its T-equivalent circuit exhibit the same I-V relationships if the four terms in the matrix of Eq. (11.27)

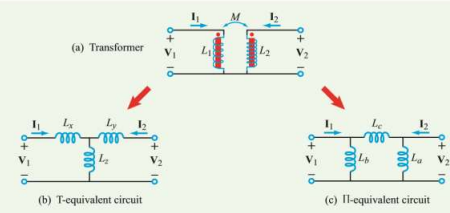


Figure 11-10: The transformer can be modeled in terms of T- or Pi-equivalent circuits.

Transformer dots on same ends

$$L_x = L_1 - M, \quad (11.29a)$$

$$L_y = L_2 - M, \quad (11.29b)$$

and

$$L_z = M. \quad (11.29c)$$

Had the transformer dots been located on opposite ends, the two terms involving M in Eq. (11.27) would have been preceded by minus signs. Consequently, the element values of inductors L_x , L_y , and L_z would be

Transformer dots on opposite ends


$$L_x = L_1 + M, \quad (11.30a)$$

$$L_y = L_2 + M, \quad (11.30b)$$

and

$$L_z = -M. \quad (11.30c)$$

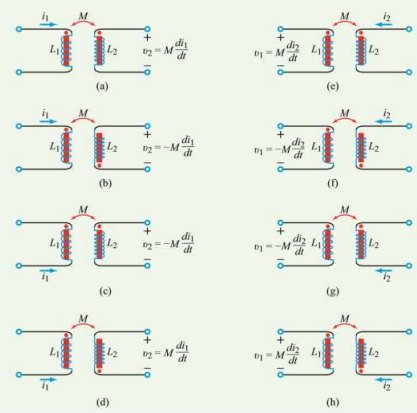Even though a negative value for inductance L_z is not physically realizable, the mathematical equivalency holds nonetheless and the equivalent circuit is perfectly applicable.



7-12.1 Ideal Transformers

A transformer consists of two inductors called *windings*, that are in close proximity to each other but not connected electrically. The two windings are called the *primary* and the *secondary*, as shown in Fig. 7-36. Even though the two windings are isolated electrically—meaning that no current flows between them—when an ac voltage is applied to the primary, it creates a magnetic flux that permeates both windings through a common *core*, inducing an ac voltage in the secondary.

► The *transformer* gets its name from the fact that it is used to transform currents, voltages, and impedances between its primary and secondary circuits. ◀

The key parameter that determines the relationships between the primary and the secondary is the *turns ratio* $n = N_2/N_1$.

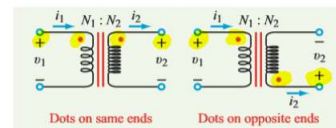


Figure 7-36: Schematic symbol for an ideal transformer. Note the reversal of the voltage polarity and current direction when the dot location at the secondary is moved from the top end of the coil to the bottom end. For both configurations:

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n, \quad \frac{i_2}{i_1} = \frac{N_1}{N_2} = \frac{1}{n}, \quad \frac{p_2}{p_1} = \frac{v_2 i_2}{v_1 i_1} = 1$$

where N_1 is the number of turns in the primary coil and N_2 is the number of turns in the secondary. An additional important attribute is the direction of the primary winding, relative to that of the secondary, around the common magnetic core. The relative directions determine the voltage polarity and current direction at the secondary, relative to those at the primary. To distinguish between the two cases, a dot usually is placed at one or the other end of each winding, as shown in Fig. 7-36. For the *ideal transformer*, voltage v_2 at the secondary side is related to voltage v_1 at the primary side by

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n. \quad (7.142)$$

where the polarities of v_1 and v_2 are defined such that their (+) terminals are at the ends with the dots. In an ideal transformer, no power is lost in the core, so all of the power supplied by a source to its primary coil is transferred to the load connected at its secondary side. Thus, $p_1 = p_2$, and since $p_1 = i_1 v_1$ and $p_2 = i_2 v_2$, it follows that

$$\frac{i_2}{i_1} = \frac{N_1}{N_2}. \quad (7.143)$$

with i_1 always defined in the direction towards the dot on the primary side and i_2 defined in the direction away from the dot on the secondary side. The purpose of the dot designation is to indicate whether the windings in the primary and secondary coils curl in the same (clockwise or counterclockwise) direction or in opposite directions. The coil directions determine the

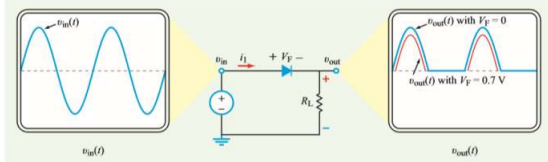


Figure 7-37: Half-wave rectifier circuit.

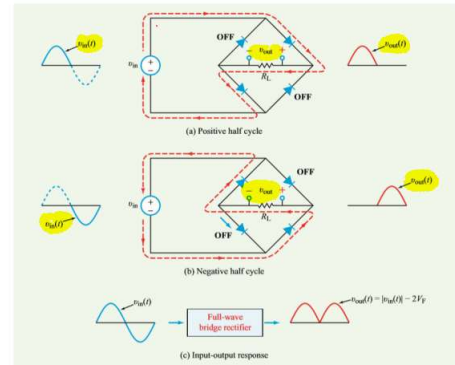
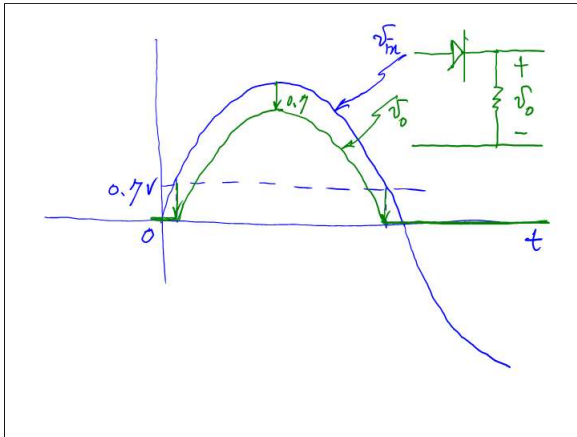


Figure 7-38: Full-wave bridge rectifier. Current flows in the same direction through the load resistor for both half cycles.


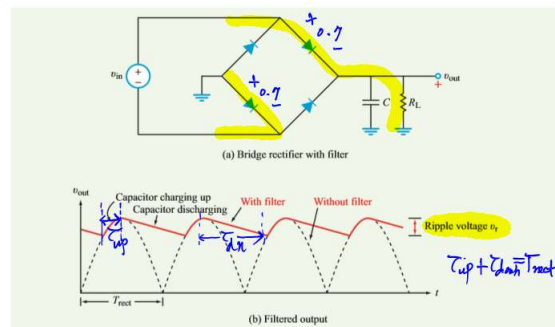


Figure 7-39: Smoothing filter reduces the variations of waveform $v_{out}(t)$.

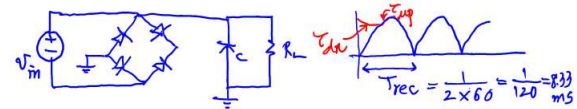

Example 7-19: Filter Design

If the bridge rectifier circuit of Fig. 7-39(a) has a 60 Hz ac input signal, determine the values of R_L and C that would result in $\tau_{cap} = T_{rect}/12$ and $\tau_{dis} = 12T_{rect}$, where T_{rect} is the period of the rectified waveform. Assume $R_D = 5 \Omega$.

Solution: If the frequency of the original ac signal is 60 Hz, the frequency of the rectified waveform is 120 Hz. Hence, the period of the rectified waveform is

$$T_{rect} = \frac{1}{120} = 8.33 \text{ ms,}$$

and the corresponding design specifications are

$$\tau_{cap} = \frac{T_{rect}}{12} = 0.69 \text{ ms, and } \tau_{dis} = 12T_{rect} = 100 \text{ ms.}$$

Application of Eq. (7.145) leads to

$$\tau_{cap} \approx 2R_L C.$$

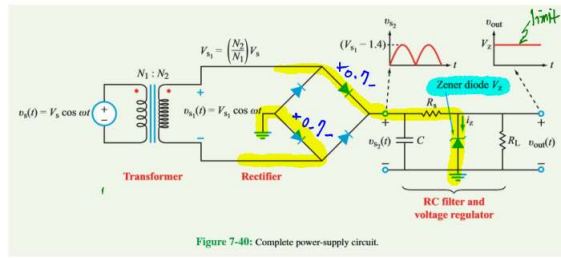


Figure 7-40: Complete power-supply circuit.

or

$$C = \frac{T_{rec}}{2R_1} = \frac{0.69 \times 10^{-3}}{2 \times 5} = 69 \mu\text{F}$$

With the value of C known, application of Eq. (7.146) gives

$$R_1 = \frac{T_{rec}}{C} = \frac{100 \times 10^{-3}}{69 \times 10^{-6}} = 1.45 \text{ k}\Omega$$

7-12.4 Voltage Regulator

The circuit shown in Fig. 7-40 includes all of the power-supply subcircuits we have discussed thus far, plus two additional elements, namely a series resistance R_1 and a zener diode. When operated in reverse breakdown, the zener diode maintains the voltage across it at a constant level V_z —so long as the current i_z passing through it remains between certain limits. Since the diode is connected in parallel with R_1 , the output voltage becomes equal to the zener voltage V_z , and the effective time constant of the smoothing filter becomes $\tau = R_1 C$. It is worth noting that the addition of the zener diode reduces the peak-to-peak ripple voltage V_r (Fig. 7-39(b)) at the output of

the RC filter by about an order of magnitude. An approximate expression for the peak-to-peak ripple voltage with the zener diode in place is given by

$$V_r = \frac{[(V_1 - 1.4) - V_z] T_{rec}}{R_1 C} \times \frac{(R_2 \parallel R_L)}{R_1 + (R_2 \parallel R_L)} \quad (7.147)$$

where V_1 is the amplitude of the ac signal at the output of the transformer (Fig. 7-40), the factor 1.4 V accounts for the voltage drop across a pair of diodes in the rectifier, V_z is the manufacturer-rated zener voltage for the specific model used in the circuit, T_{rec} is the period of the rectified waveform, and R_1 is the manufacturer specified value of the zener-diode resistance.

Example 7-20: Power-Supply Design

A power supply with the circuit configuration shown in Fig. 7-40 has the following specifications: the input voltage is 60 Hz with an rms amplitude $V_{rms} = 110$ V where $V_{rms} = V_1/\sqrt{2}$ (the rms value of a sinusoidal function is

Time constant of the smoothing filter
 $\tau = R_1 C = 50 \times 69 \times 10^{-6} = 3.45 \times 10^{-3} = 3.45 \text{ ms}$
 $\tau \approx R_1 = 50 \Omega$

discussed in Chapter 6), $N_1/N_2 = 5$, $C = 2 \text{ mF}$, $R_1 = 50 \Omega$, $R_2 = 1 \text{ k}\Omega$, $V_z = 24 \text{ V}$, and $R_L = 20 \Omega$. Determine v_{out} , the ripple voltage, and the ripple fraction relative to v_{out} .

Solution: At the secondary side of the transformer,

$$v_2(t) = \left(\frac{N_2}{N_1}\right) (V_s \cos 377t) = \frac{1}{5} \times 110\sqrt{2} \cos 377t = 31.11 \cos 377t \text{ V}$$

Hence, $V_1 = 31.11$ V, which is greater than the zener voltage $V_z = 24$ V.

Consequently, the zener diode will limit the output voltage at

$$v_{out} = V_z = 24 \text{ V}$$

In Example 7-19, we established that $T_{rec} = 8.33 \text{ ms}$. Also,

$$R_2 \parallel R_L = \frac{20 \times 1000}{20 + 1000} = 19.6 \Omega$$

Application of Eq. (7.147) gives

$$V_r = \frac{[(V_1 - 1.4) - V_z] T_{rec}}{R_1 C} \times \frac{(R_2 \parallel R_L)}{R_1 + (R_2 \parallel R_L)} = \frac{[(31.11 - 1.4) - 24] (8.33 \times 10^{-3})}{50 \times 2 \times 10^{-3}} \times \frac{19.6}{50 + 19.6} = 0.13 \text{ V (peak-to-peak)}$$

Hence,

$$\text{ripple fraction} = \frac{(V_r/2)}{V_z} = \frac{0.13/2}{24} = 0.0027,$$

which represents a relative variation of less than ± 0.3 percent.

