

ECE 101 Lecture #2 Jan 10, 2019

In Lect #1,

we covered

- circuit elements R, L, C
sources, dependent sources
- Kirchhoff Current Law (KCL)
Kirchhoff Voltage Law (KVL)
- Power generation $V \cdot I < 0$
consumption $V \cdot I > 0$
conservation of power $\sum P_K = 0$

2-1.2 $i-v$ Characteristics of Ideal Resistor

Based on the results of his experiments on the nature of conduction in circuits, German physicist Georg Simon Ohm (1789–1854) formulated in 1826 the $i-v$ relationship for a resistor, which has become known as **Ohm's law**. He discovered that the voltage v across a resistor is directly proportional to the current i flowing through it, namely

$$v = iR, \quad (2.3)$$


with the resistance R being the proportionality factor.

In compliance with the passive sign convention, current enters a resistor at the "+" side of the voltage across it.

$$\begin{aligned} v_{ab} &= v_a - v_b \\ + &\quad R \quad - \\ v_a & \quad i \quad v_b \end{aligned}$$

$$i = \frac{v_a - v_b}{R}$$

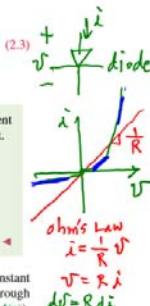An ideal **linear resistor** is one whose resistance R is constant and independent of the magnitude of the current flowing through it, in which case its $i-v$ response is a straight line (Fig. 2-4(a)).



Prof. Ohm's
Statue
at
Tech U
München
(2018)

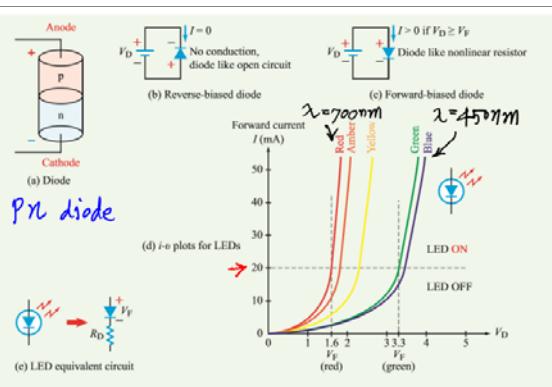


Figure 2-8: p-n junction diode (a) configuration, (b) reverse biased, (c) forward biased, (d) typical $i-v$ plots for LEDs, and (e) LED equivalent circuit.


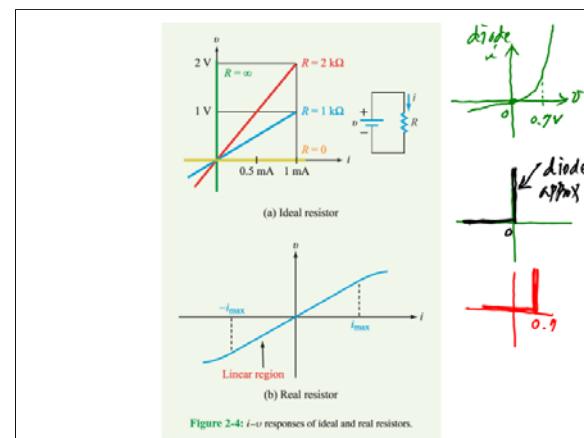


Figure 2-4: $i-v$ responses of ideal and real resistors.

2.2 KIRCHHOFF'S LAW

KCL

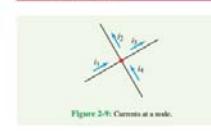

Mathematically, KCL can be expressed by the compact form:

$$\sum_{k=1}^N i_k = 0 \quad (\text{KCL}), \quad (2.8)$$

where N is the total number of branches connected to the node, and i_k is the k th current.

A common convention is to assign a positive "+" sign to a current if it is entering the node and a negative "-" sign if it is leaving it.

For the node in Fig. 2-9, the sum of currents entering the node is

$$i_1 - i_2 - i_3 + i_4 = 0, \quad (2.9)$$

where currents i_1 and i_4 were assigned positive signs because they are labeled as entering the node, and i_2 and i_3 were assigned negative signs because they are leaving the node.

$$\sum_i i_j = \sum_k i_k$$

$$i_1 + i_4 - i_2 - i_3 = 0$$

$$-i_1 - i_4 + i_2 + i_3 = 0$$

$$\sum_i i_j = \sum_k i_k$$

entering leaving

► A common convention is to assign a positive "+" sign to a current if it is entering the node and a negative "-" sign if it is leaving it. ◀


For the node in Fig. 2-9, the sum of currents entering the node is

$$i_1 - i_2 - i_3 + i_4 = 0, \quad (2.9)$$



where currents i_1 and i_4 were assigned positive signs because they are labeled in the figure as entering the node, and i_2 and i_3 were assigned negative signs because they are leaving the node.

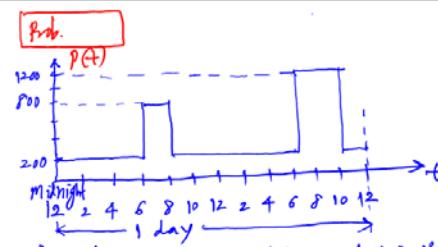► Alternatively, the sum of currents leaving a node is zero, in which case we assign a "+" to a current leaving the node and a "-" to a current entering it. ◀






a) Total energy consumed in one day in kWh?

$$200 \times 6 + 800 \times 2 + 200 \times 10 + 1200 \times 4 + 200 \times 2 \\ = 1200 + 1600 + 2000 + 4800 + 400 = 10,000 \text{ Wh} = 10 \text{ kWh}$$

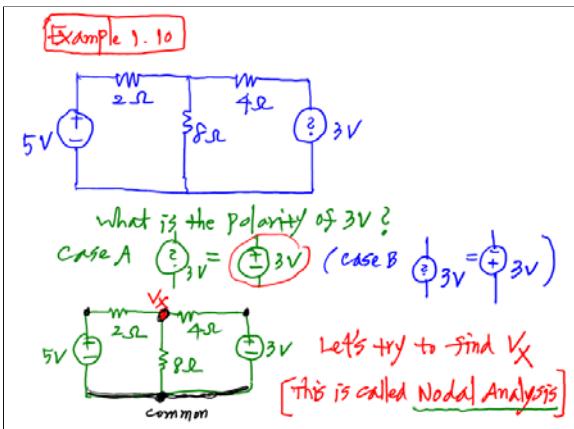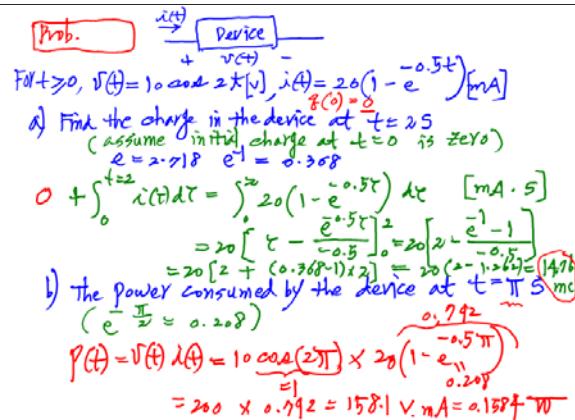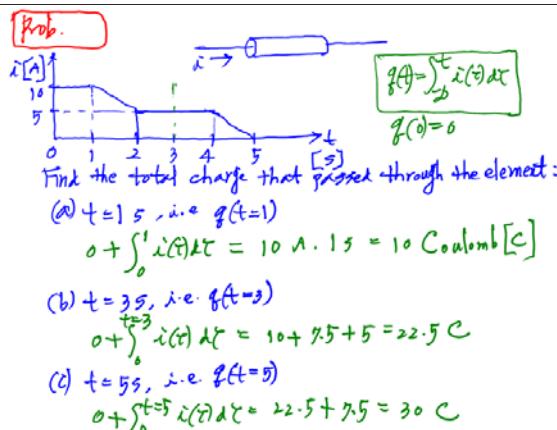b) Average power over the 24-hour period (day)?

$$P_{avg} = \frac{1}{T} \int_0^T P(t) dt = \frac{10 \text{ kWh}}{24 \text{ h}} \approx 0.416 \text{ kW}$$



KCL at $\textcircled{1}$

$$i_{2,1} + i_{4,1} = i_{8,1}$$

$$\frac{5-V_X}{2} + \frac{3-V_X}{4} = \frac{V_X}{8}$$

$$\times 8 \quad 20 - 4V_X + 6 - 2V_X = V_X$$


$$20 + 6 = V_X + 4V_X + 2V_X$$

$$26 = 7V_X$$

$$V_X = \frac{26}{7} \text{ V}$$

$$i_{4,1} = \frac{3-V_X}{4} = \frac{3 - \frac{26}{7}}{4} = \frac{21 - 26}{4 \times 7} = -\frac{5}{28} \text{ A}$$
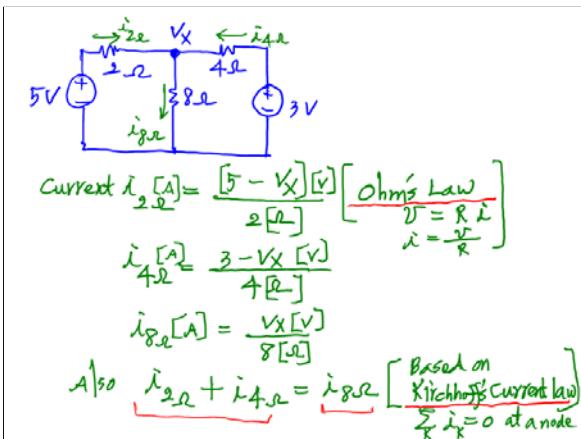
$$V_X = 4(\frac{5}{28}) + 3 - \frac{5}{7} + 3 - \frac{26}{7} \quad \checkmark$$



$$\frac{5 - V_x}{2} + \frac{3 - V_x}{4} = \frac{V_x}{8}$$

$$+ (5 - V_x) + 2(3 - V_x) = V_x$$

$$20 + 6 - 4V_x - 2V_x = V_x$$

$$26 = 7V_x \Rightarrow V_x = \frac{26}{7} [V]$$

$i_{2\Omega} = \frac{5 - \frac{26}{7}}{2} = \frac{9}{14} [A]$

$i_{4\Omega} = \frac{3 - \frac{26}{7}}{4} = \frac{-5}{14} [A]$ means in opposite direction

$i_{8\Omega} = i_{2\Omega} + i_{4\Omega}$ (KCL) $i_{8\Omega} = \frac{(-5)}{8} = \frac{12}{28} [A]$

Also, power absorbed in $2\Omega, 4\Omega, 8\Omega$ resistors are:

2Ω case $P_{2\Omega} = \frac{9}{14} A \times 5V = \left(\frac{5}{7} \right) [V] \left[\frac{9}{14} A \right] = \frac{45}{98} [W]$

4Ω case $P_{4\Omega} = \frac{5}{28} A \times 3V = \left(\frac{25}{7} \right) [V] \times \frac{5}{28} [A] = \frac{25}{196} [W]$

8Ω case $P_{8\Omega} = \frac{25}{196} A \times 5V = \frac{25}{7} [V] \times \frac{12}{28} [A] = \frac{169}{98} [W]$

Total consumption


$$P_{\text{total}} = \frac{P_1}{98} + \frac{25}{196} + \frac{169}{98} = \frac{162 + 25 + 338}{196} = \frac{525}{196} = \frac{75}{28} [W]$$

Power generated by two voltage sources:

$P_{5V} = -5[V] \times \frac{9}{14} A = \frac{-45}{14} W$ negative sign since this is supplied/generated

$P_{3V} = +3[V] \times \frac{5}{28} [A] = +\frac{15}{28} [W]$

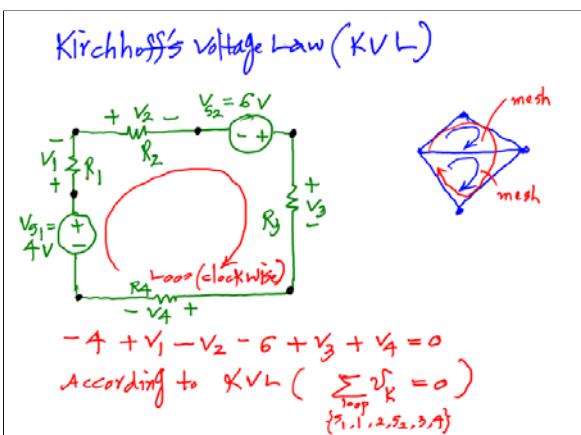Total $P_{5V} + P_{3V} = -\frac{45}{14} + \frac{15}{28} = -\frac{75}{28} [W]$




If we denote the current in the loop (loop current) as I , then (by Ohm's law $V_k = R_k I$)

$$-4 + R_1 I + R_2 I - 6 + R_3 I + R_4 I = 0$$

$$-(4 + 6) + (R_1 + R_2 + R_3 + R_4) I = 0$$


$$I = \frac{4 + 6}{R_1 + R_2 + R_3 + R_4}$$

[Problem] from Fig. 2-15 (a) on page 65

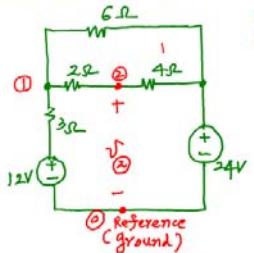

[Q] what is the voltage at ②?

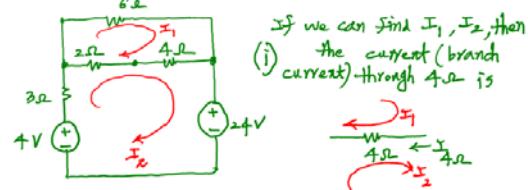[Method 1] solving by Loop Analysis - Loop Currents are unknown variables



If we can find I_1, I_2 , then
(i) the current (branch current) through 4Ω is


$$I_{4\Omega} = I_1 - I_2$$

$$\frac{-V_{4\Omega}}{4\Omega} = I_{4\Omega}$$

$$(ii) V_{4\Omega} = 4 I_{4\Omega} = 4(I_1 - I_2)$$

$$\text{and (iii)} \quad V_2 = -V_{4\Omega} + 24$$

Loop 1

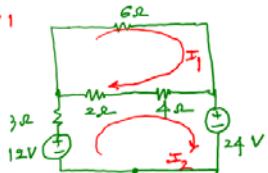

By KVL in Loop 1

$$+6I_1 + 4(I_1 - I_2) + 2(I_1 - I_2) = 0$$

By KVL in Loop 2

$$-12 + 3I_2 + 2(I_2 - I_1) + 4(I_2 - I_1) + 24 = 0$$

$$\begin{bmatrix} 12 & -6 \\ -6 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -12 \end{bmatrix}$$

$$\text{Row 1} \times 3 + \text{Row 2} \times 2 \Rightarrow$$

$$\begin{array}{l} 36I_1 - 18I_2 = 0 \\ -12I_1 + 18I_2 = -24 \\ \hline 24I_1 + 0 = -24 \end{array} \Rightarrow I_1 = -1A$$

$$\text{Row 1} + \text{Row 2} \times 2 \Rightarrow$$

$$\begin{array}{l} 12I_1 - 6I_2 = 0 \\ -12I_1 + 18I_2 = -24 \\ \hline 0 + 12I_2 = -24 \end{array} \Rightarrow I_2 = -2A$$

Matrix solution

$$A \underset{\sim}{\underset{\sim}{X}} = b$$

$$\underset{\sim}{X} = \underset{\sim}{A}^{-1} \underset{\sim}{b}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 & -6 \\ -6 & 9 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ -12 \end{bmatrix}$$

$$= \frac{1}{12(9) - (-6)(-6)} \begin{bmatrix} 9 & 6 \\ 6 & 12 \end{bmatrix} \begin{bmatrix} 0 \\ -12 \end{bmatrix} = \frac{[-72]}{72} = \begin{bmatrix} -1 \\ -2 \end{bmatrix}$$


thus with $I_1 = -1A$, $I_2 = -2A$

$$V_2 = 4\Omega(I_2 - I_1) + 24 = 4(-2 - (-1)) + 24 = 20V$$

Revisit the circuit

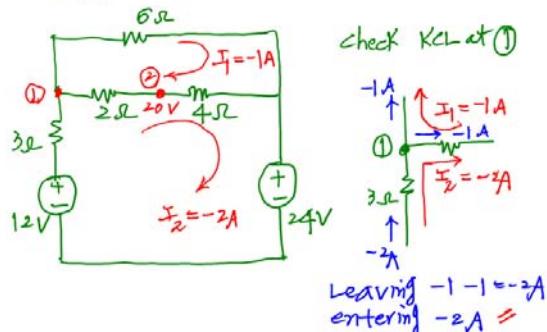

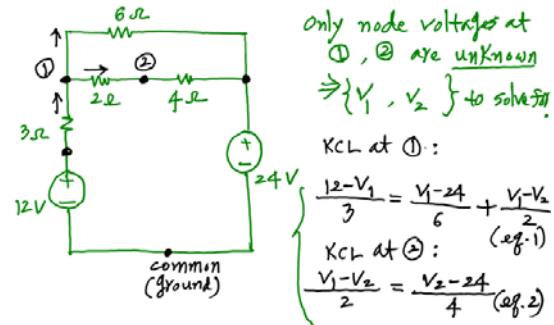Method 2: Nodal Analysis - node voltages are unknown variables



$$6 \times \text{eq.1} \Rightarrow 24 - 2V_1 = V_1 - 24 + 3V_1 - 3V_2 \\ \text{or } 48 = 6V_1 - 3V_2 \quad (\text{eq.1}')$$

$$4 \times \text{eq.2} \Rightarrow 2V_1 - 2V_2 = V_2 - 24 \\ \text{or } 2V_1 - 3V_2 = -24 \quad (\text{eq.2}')$$

In matrix form

$$\begin{bmatrix} 6 & -3 \\ 2 & -3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 48 \\ -24 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = 24 \begin{bmatrix} 6 & -3 \\ 2 & -3 \end{bmatrix}^{-1} \begin{bmatrix} 2 \\ -1 \end{bmatrix} = 24 \frac{\begin{bmatrix} -3 & 3 \\ -2 & 6 \end{bmatrix}}{\begin{vmatrix} 6 & -3 \\ 2 & -3 \end{vmatrix}} \begin{bmatrix} 2 \\ -1 \end{bmatrix} = \frac{24}{-12} \begin{bmatrix} -9 \\ -10 \end{bmatrix} \\ = \begin{bmatrix} 18 \\ 20 \end{bmatrix}$$