

## EE101 Lecture #3 Jan 15, 2019

So far we have discussed

- Elements of electronic circuits  
R, L, C, independent sources, dependent sources
- Electrical variables  
voltage (V), current (I), power ( $P = VI$ )  
Energy ( $E = \int_0^t P(t) dt$ ), Average power  
 $P_{avg} = \frac{1}{T} \int_0^T P(t) dt$
- Loop/Mesh currents, Node voltages
- KCL, KVL, Ohm's Law

## HW #2 for Quiz on Jan 22

[1] Prob. 2-11

[2] Prob. 2-19

[3] Prob. 2-25

[4] Prob. 2-28

[5] Prob. 2-33

[6] Prob. 2-40

[7] Prob. 2-43




[8] Prob. 2-47



DRC Quiz is in E2-215, 234 at 2:40-3:10

Group Tutor Hours in E2-516

Tu, Th 3:30 - 6 pm

W 3 - 4 pm

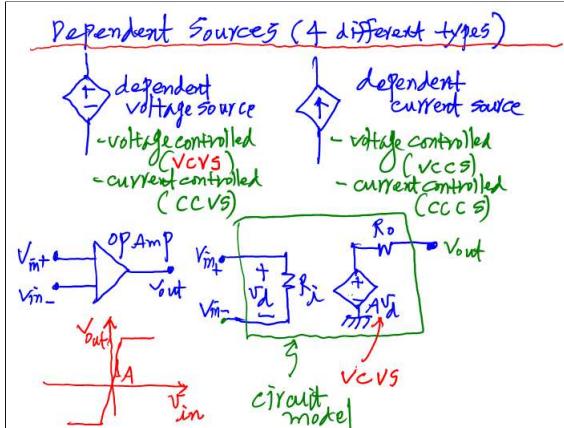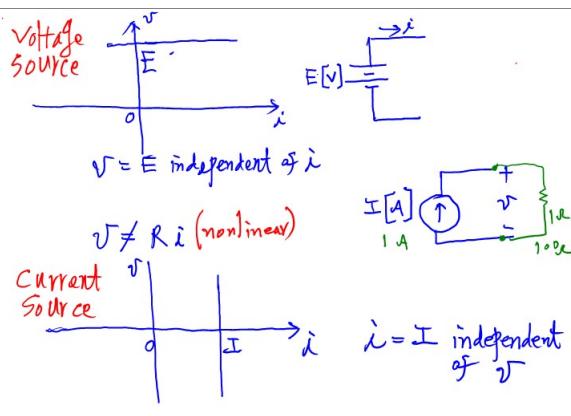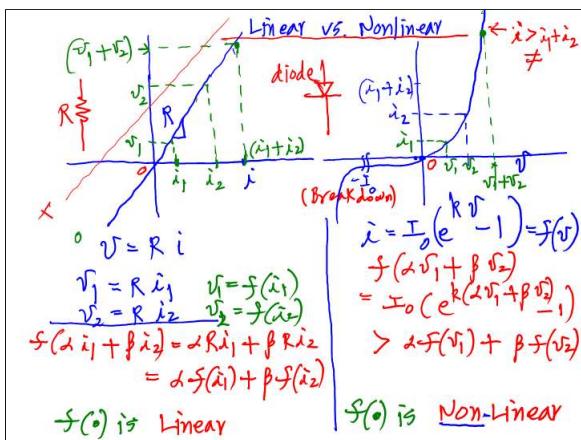

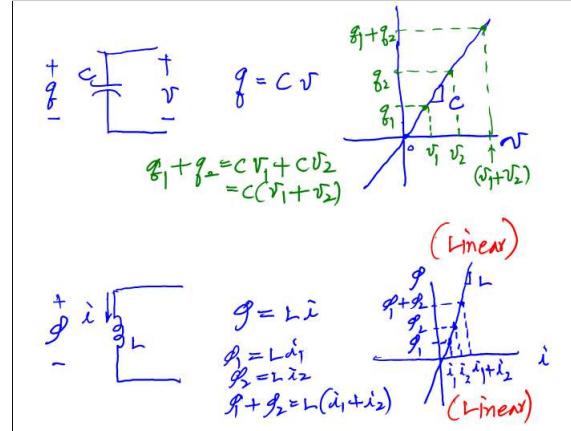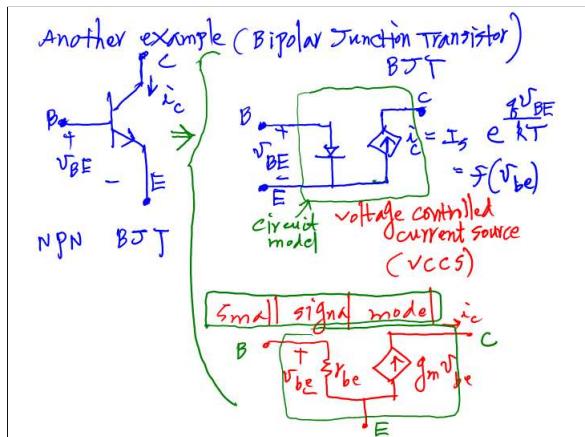

In general

$$y = f(x) \quad f \text{ linear function}$$

$$y_1 = f(x_1), y_2 = f(x_2)$$


For  $x = ax_1 + bx_2$

$$y = f(ax_1 + bx_2)$$

$$\uparrow \quad \uparrow$$

$$= a \cdot f(x_1) + b \cdot f(x_2) = ay_1 + by_2$$

( $f$  linear)

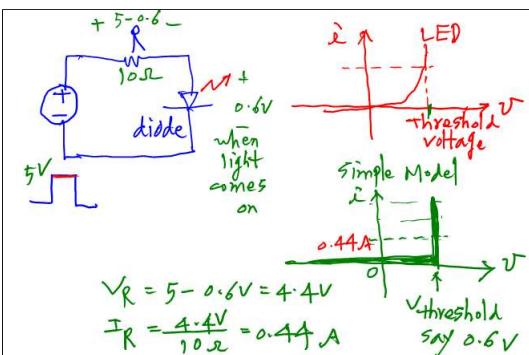

Complex number

$$z = x + jy$$

magnitude phase angle

$$z = z_m \angle \phi_z$$

$$= \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x} = \phi_z$$

$$= z_m \cos \phi_z + j z_m \sin \phi_z$$

$$\sqrt{3^2 + 4^2} = \sqrt{25} = 5$$

$$\tan^{-1} \frac{4}{3} = 53.1^\circ$$

$$z_1 = x_1 + jy_1 = z_{1m} \angle \phi_{z1}$$

$$z_2 = x_2 + jy_2 = z_{2m} \angle \phi_{z2}$$

$$z_t = z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$


$$= \sqrt{(x_1 + x_2)^2 + (y_1 + y_2)^2} \angle \tan^{-1} \frac{y_1 + y_2}{x_1 + x_2} = z_{tm} \angle \phi_{zt}$$

$$\begin{aligned}
 V &= V_m \cos(\omega t + \phi_v) \\
 &= \operatorname{Re}[V_m e^{j(\omega t + \phi_v)}] \\
 &\stackrel{j\theta}{=} \operatorname{Re}[V_m (\cos(\omega t + \phi_v) + j \sin(\omega t + \phi_v))] \\
 &\stackrel{\text{def}}{=} \operatorname{Re}[V_m e^{j\phi_v} e^{j\omega t}] = \operatorname{Re}[V e^{j\omega t}] \\
 \boxed{V = V_m e^{j\phi_v} = V_m \angle \phi_v \text{ phasor}}
 \end{aligned}$$

Likewise


$$\begin{aligned}
 I &= I_m \cos(\omega t + \phi_i) \\
 &= \operatorname{Re}[I_m e^{j(\omega t + \phi_i)}] \\
 &= \operatorname{Re}[I_m e^{j\phi_i} e^{j\omega t}] \\
 &= \operatorname{Re}[I e^{j\omega t}] \\
 \boxed{I = I_m e^{j\phi_i} = I_m \angle \phi_i \text{ phasor}}
 \end{aligned}$$
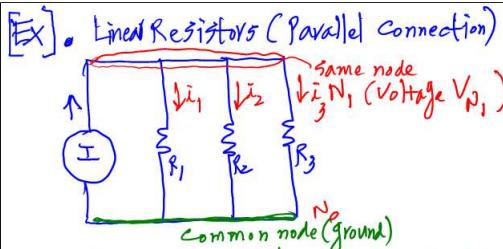
$$V \cdot I = V_m e^{j\phi_v} \cdot I_m e^{j\phi_i} = V_m I_m e^{j(\phi_v + \phi_i)}$$



In this case Nodal Analysis is better than Loop Analysis.
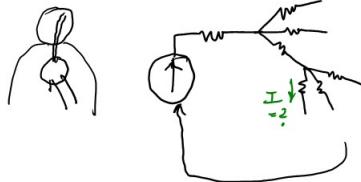
$$\begin{aligned}
 I &= i_1 + i_2 + i_3 \stackrel{\text{Ohm's law}}{=} \frac{V_{N1}}{R_1} + \frac{V_{N1}}{R_2} + \frac{V_{N1}}{R_3} \\
 &= V_{N1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \\
 \underline{V_{N1}} &= \underline{I} / \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)
 \end{aligned}$$




In Ohm's Law  $V = R \cdot I$ ,  $R$  = Resistance [ $\Omega$ ]  
or  $I = \frac{V}{R} = \frac{1}{R} V$

$$\begin{aligned}
 &= G \cdot V \\
 \text{so } V_{N1} &= I / \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \\
 &= I / (G_1 + G_2 + G_3) \\
 \underline{i_1} &= \underline{V_{N1}} / R_1 = G_1 V_{N1} = I \left[ \frac{G_1}{G_1 + G_2 + G_3} \right]
 \end{aligned}$$


Revisit of the Example

$$\begin{aligned}
 6A &= \frac{V_{N1}}{R_1} = \frac{V_{N1}}{\frac{1}{G_1}} = G_1 V_{N1} \\
 G_1 &= 1 \Omega \quad G_2 = 2 \Omega \quad G_3 = 3 \Omega \\
 i_1 &= \frac{V_{N1}}{R_1} = \frac{V_{N1}}{\frac{1}{G_1 + G_2 + G_3}} = 6 \cdot \frac{1}{1+2+3} = 1 [A] \\
 i_2 &= \frac{V_{N1}}{R_2} = 6 \cdot \frac{2}{1+2+3} = 2 [A] \\
 i_3 &= \frac{V_{N1}}{R_3} = 6 \cdot \frac{3}{1+2+3} = 3 [A] \\
 I &= i_1 + i_2 + i_3 (\checkmark) (KCL)
 \end{aligned}$$

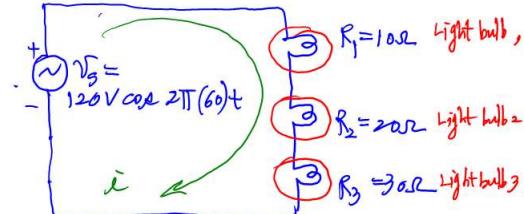

Loop (Mesh) current  $i = ?$
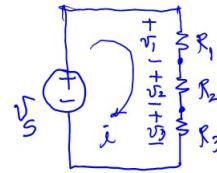
$$\text{By Ohm's Law } i = \frac{V_s}{R_1 + R_2 + R_3} = \frac{120 \cos 120\pi t}{60} = 2 \cos 120\pi t [A]$$



$$\begin{aligned} \text{KVL} \\ -v_3 + v_1 + v_2 + v_3 &= 0 \\ \Rightarrow v_1 + v_2 &= 0 \\ &= i R_1 + i R_2 + i R_3 \\ &= i (R_1 + R_2 + R_3) \end{aligned}$$

$$\left. \begin{aligned} i &= \frac{V_s}{R_1 + R_2 + R_3} \\ v_1 &= i R_1 = V_s \frac{R_1}{R_1 + R_2 + R_3} \\ v_3 &= i R_3 = V_s \frac{R_3}{R_1 + R_2 + R_3} \end{aligned} \right\} \begin{aligned} V &= V_s \frac{R_K}{\sum R_i} \\ &\text{Voltage division} \end{aligned}$$

Average power in light bulb 1

$$\begin{aligned} P_1 &= \frac{1}{T} \int_0^T V_s(t) i(t) dt \\ &= \frac{1}{T} \int_0^T R_1 i^2(t) dt \\ V_s = R_1 i &= \frac{10}{T} \int_0^T [2 \cos 120\pi t]^2 dt \\ R_1 = 10\Omega &= \frac{10 \times 4}{T} \int_0^T \cos^2 120\pi t dt \\ \cos^2 \theta &= \frac{1}{2}(1 + \cos 2\theta) = \frac{40}{T} \left[ \frac{1}{2} T + \frac{1}{2} \int_0^T \cos 240\pi t dt \right] \\ &= 20 \text{ W} \end{aligned}$$


For Light Bulb 2 ( $R_2 = 20\Omega$ )

$$P_2 = \frac{20}{T} [20 \text{ W}] = 40 \text{ W}$$

$$P_3 = \frac{20}{T} [20 \text{ W}] = 60 \text{ W}$$



$$\text{Total Wattage } P_1 + P_2 + P_3 = 120 \text{ W}$$

If bulbs are connected in Parallel

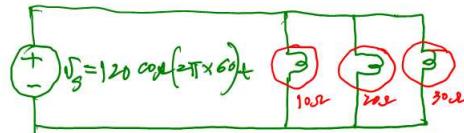

Avg Power in bulb 1

$$\begin{aligned} P_1 &= \frac{1}{T} \int_0^T V_s^2(t) / R_1 dt = \frac{1}{T} \int_0^T \frac{V_s^2(t)}{R_1} dt \\ &= \frac{1}{10} \int_0^T [120 \cos 120\pi t]^2 dt \\ &= \frac{14400}{10} \left[ \frac{1}{2} \int_0^T (1 + \cos 240\pi t) dt \right] \\ &= \frac{144}{10} \left[ \frac{1}{2} T + \frac{1}{2} \int_0^T \cos 240\pi t dt \right] \\ &= 72 \text{ W} \\ P_2 &= 72 \text{ W} \left( \frac{20}{20} \right) = 36 \text{ W} \quad (P(t) = \frac{V_s^2(t)}{R}) \\ P_3 &= 72 \text{ W} \left( \frac{30}{30} \right) = 24 \text{ W} \\ P_1 + P_2 + P_3 &= 72 + 36 + 24 = 132 \text{ W} \end{aligned}$$

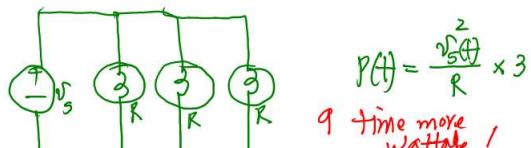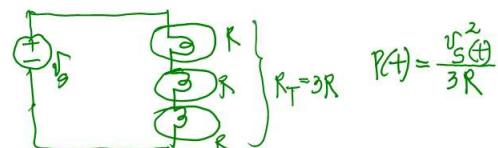

$$P(t) = \frac{V_s^2(t)}{R}$$

9 time more wattage!

(Light Bulb at home are connected this way)  
But if too many in parallel, then overload (shut off)