

EE101 Lect 4 Jan 17, 2019  
Equivalent Circuits (textbook pp 70-86)

we denote serial connection by + and parallel connection by ||, then

$$R_{eq} = \left\{ \left[ \left( R_4 + R_5 \right) \parallel R_3 \right] + R_2 \right\} \parallel R_1$$

should start from the far end

again,  $I$  [A] Ampere  
 $V$  [V] volt  
 $R$  [ $\Omega$ ] ohm

Ohm's Law  
 $V = R I$   
[V] [A] [A]

$$I [A] = \frac{V [V]}{R [\Omega]}$$

$$R [\Omega] = \frac{V [V]}{I [A]}$$

Conductance Unit [ $S$ ] siemens

For a conducting element, electrical resistance  $R$  and electrical conductance  $G$  are defined as

$$G = \frac{1}{R} = \frac{I [A]}{V [V]} [S]$$

where  $I$  is the electric current through the object and  $V$  is the voltage (electrical potential difference) across the object.

The unit **siemens** for the conductance  $G$  is defined by

$$[S] = [\Omega]^{-1}$$

where  $\Omega$  is the ohm, A is the ampere, and V is the volt.

For a device with a conductance of one siemens, the electric current through the device will increase by one ampere for every increase of one volt of electric potential difference across the device.

The conductance of a resistor with a resistance of five ohms, for example, is  $(5 \Omega)^{-1}$ , which is equal to 200 mS.

$$G = \frac{1}{R} = \frac{1}{5 [\Omega]} = 0.2 S = 200 mS$$

ohm mho

Mho [edit] [ $S$ ] as [ $\frac{1}{\Omega}$ ]

"Mho" redirects here. It is not to be confused with **Mohs** (disambiguation).

A name that is used as an alternative to the *siemens* is the **mho** (*mohm*), the reciprocal of one ohm. It is derived from spelling *ohm* backwards and is written as an upside-down capital **Greek** letter omega:  $\omega$  mho. Unicode symbol U+2127 (Ω). According to Maver<sup>[2]</sup> the term *mho* was suggested by Sir William Thomson (Lord Kelvin). The *mho* was officially renamed to the *siemens*, replacing the old meaning of the "*siemens unit*", at a conference in 1881.<sup>[2]</sup>

NIST's *Guide for the Use of the International System of Units (SI)* refers to the mho as an "unaccepted special name for an SI unit", and indicates that it should be **strictly avoided**.<sup>[2]</sup>

EE101 Winter 2019 Quiz #1  
January 15, 2019

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_

Problem (10 points) For the circuit below, (1) find the voltage across the 6A current source with an appropriate polarity. (2) Find the total power generated in the circuit.

Answers:  
Answer (1) (6 points) Voltage = 12 [V]  
Mark the Polarity to the source figure with + and - signs.

Answer (2) (4 points) Total power generated in the circuit = 234 [W]

Handwritten calculations:  
Avg = 5.73  
α = 1.93  
68%  
P = -6 \* 3 = -18W  
P = -12 \* 12 = -144W  
144 + 18 + 72 = 234W  
Σ = 0







Handwritten calculation for equivalent resistance:






$$R_{eq} = \left\{ \left[ \left( (2 + 3) \parallel 5 \right) + 2.5 \right] \parallel 10 \right\}$$

$$= \left\{ \left[ \left( \frac{5 \times 5}{5 + 5} \right) + 2.5 \right] \parallel 10 \right\}$$

$$= \left\{ \left[ \frac{5 \times 10}{5 + 10} \right] \right\}$$
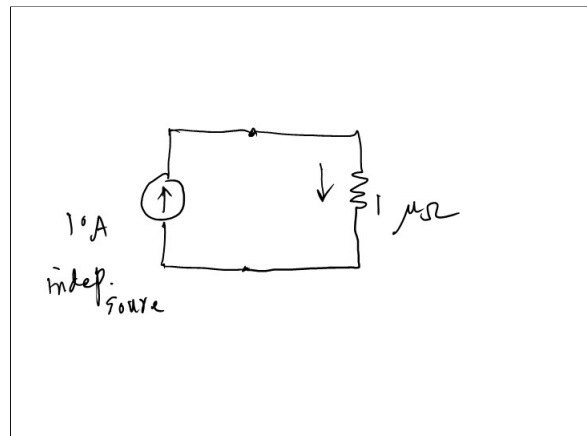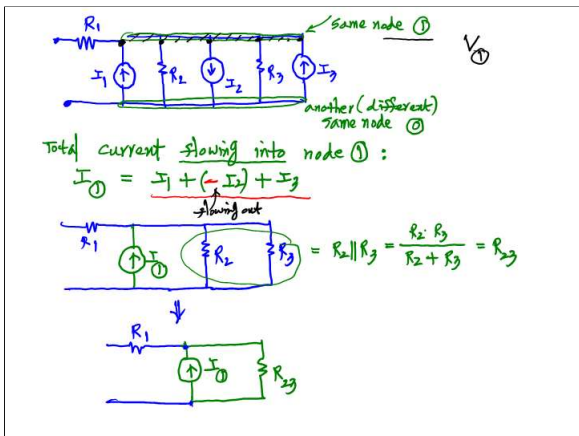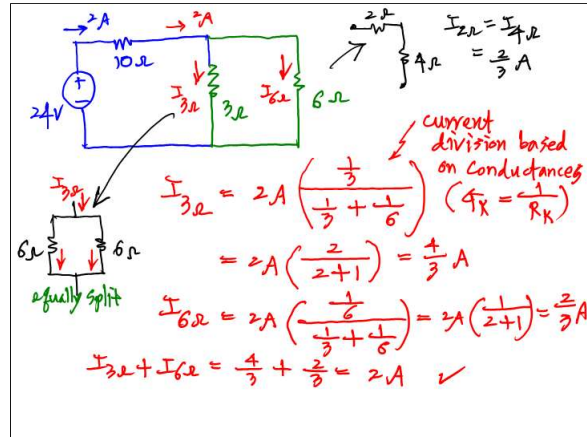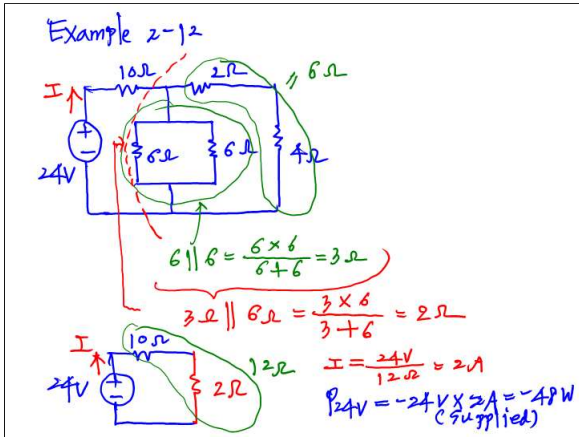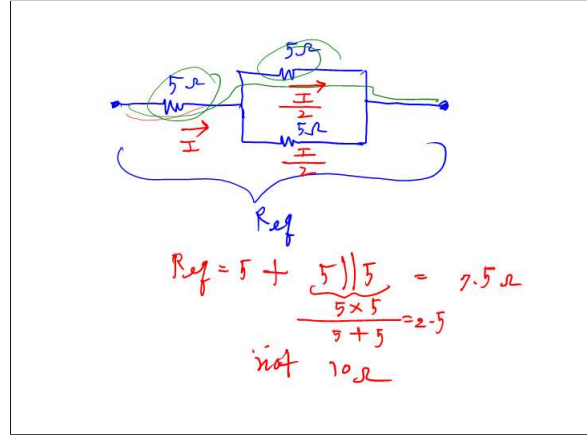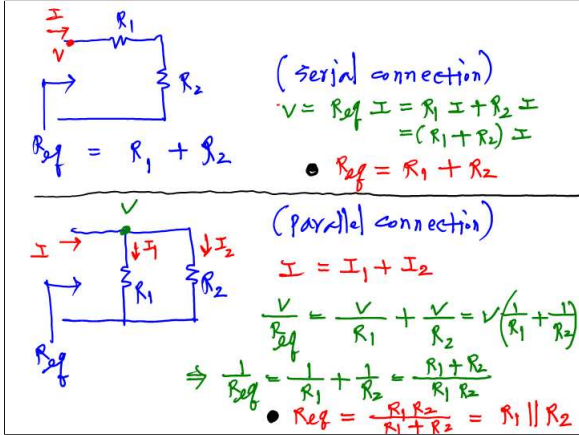
$$= \frac{10}{\left( \frac{10}{3} \right)} = 3 A$$



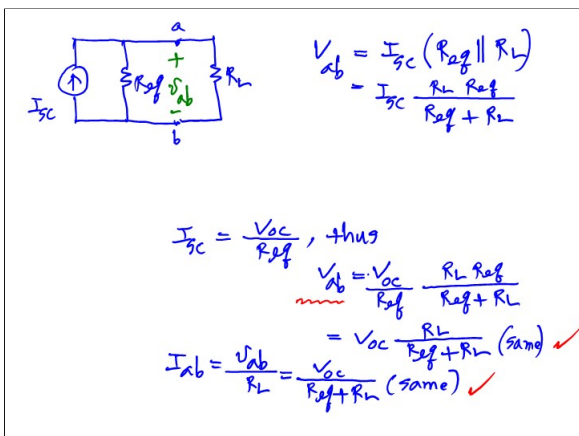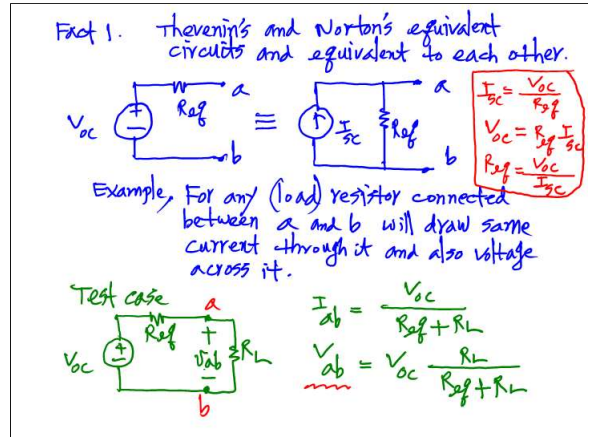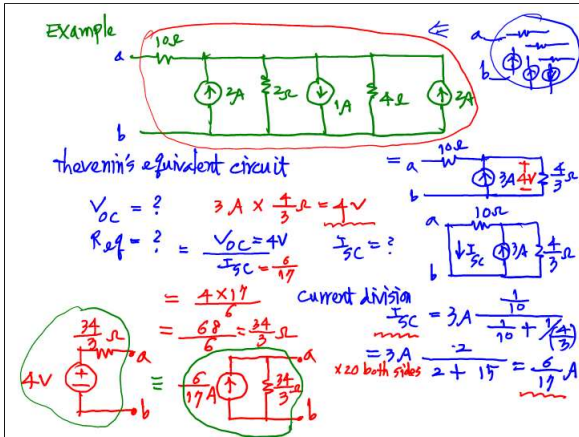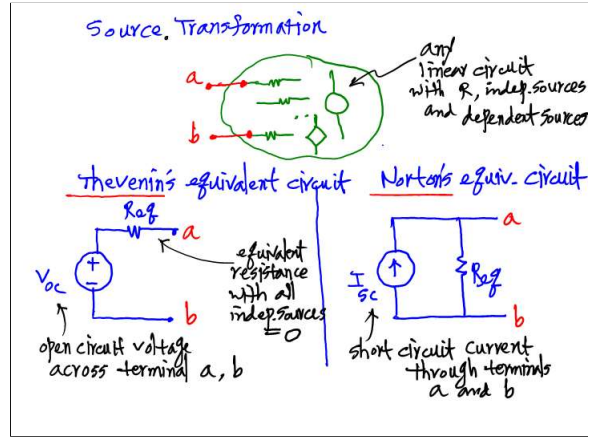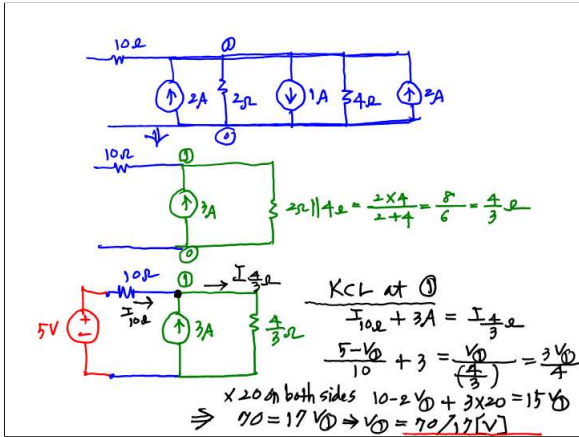

2.3. EQUIVALENT CIRCUITS

Table 2-5: Equivalent circuits.


Series	$R_1, R_2$	$R_1 + R_2$
Parallel	$R_1, R_2$	$\frac{R_1 R_2}{R_1 + R_2}$
Series	$i_1, i_2$	$i_1 + i_2$
Parallel	$i_1, i_2$	$i_1 - i_2$

### Y-Δ/Δ-Y transformation


$R_1 = \frac{R_2 R_3}{R_1 + R_2 + R_3}$   
 $R_2 = \frac{R_1 R_3}{R_1 + R_2 + R_3}$   
 $R_3 = \frac{R_1 R_2}{R_1 + R_2 + R_3}$   
 (same denom, same numerichy)  
 For  $R_1 = R_2 = R_3 \Rightarrow R_1 = R_2 = R_3 = R_{\Delta} / 3$   
 For  $R_1 = R_2 = R_3 \Rightarrow R_1 = R_2 = R_3 = 3R_{\Delta}$

Y-Δ/Δ-Y transformation  
(Wye-Delta)/(Delta-Wye)

Example

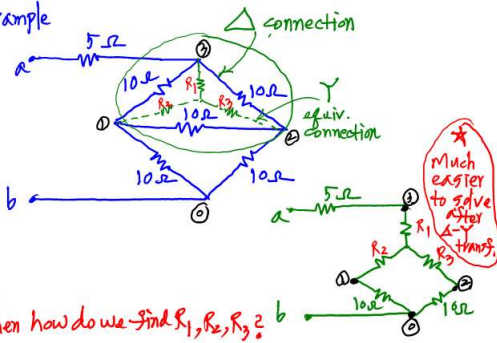

Δ-Y transformation formula

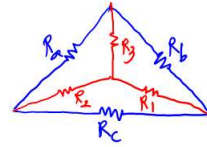


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Same Denom

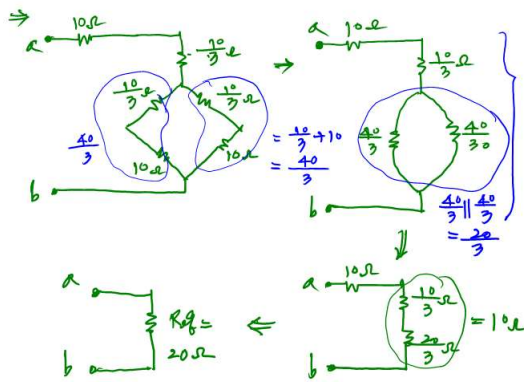In the previous example,  $R_a = R_b = R_c = 10\Omega$   
thus  $R_1 = \frac{10 \times 10}{10 + 10 + 10} = \frac{100}{30} = \frac{10}{3} = R_2 = R_3$



Conversely Y-Δ transformation

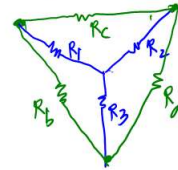




$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

(Same)

Example

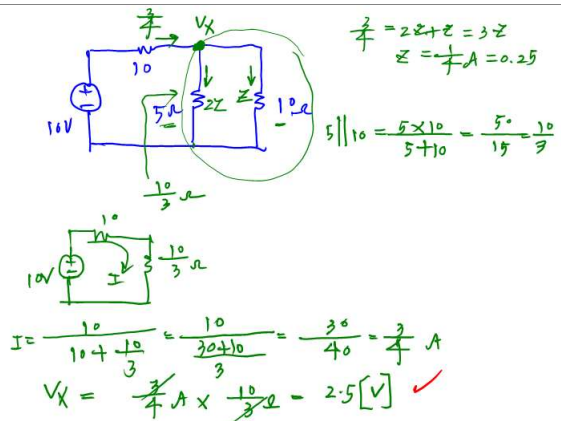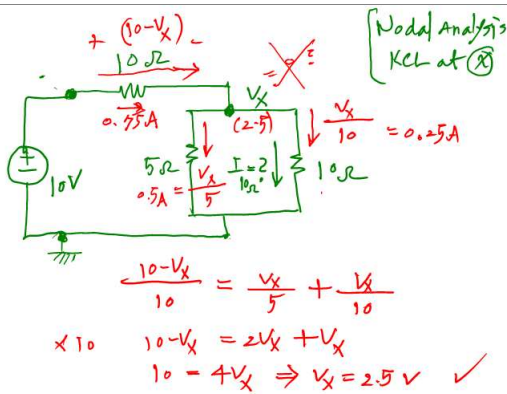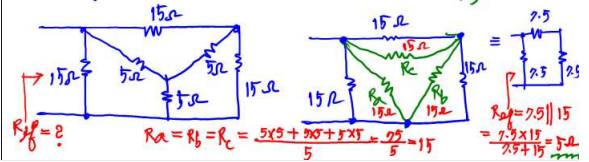

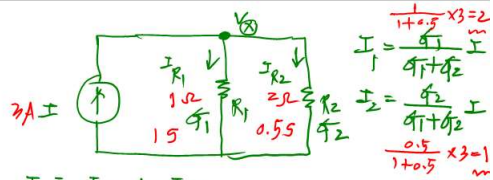

$$I = \frac{V_0}{R_1 + R_2}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

$\frac{1}{1+0.5} \times 3 = 2$   
 $\frac{0.5}{1+0.5} \times 3 = 1$

$$I = I_{R_1} + I_{R_2}$$

$$= \frac{V_0}{R_1} + \frac{V_0}{R_2} = V_0 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_0 = I (R_1 \parallel R_2) = I \frac{R_1 R_2}{R_1 + R_2}$$

$$I = V_0 \frac{R_1 + R_2}{R_1 R_2}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \cdot R_2}$$