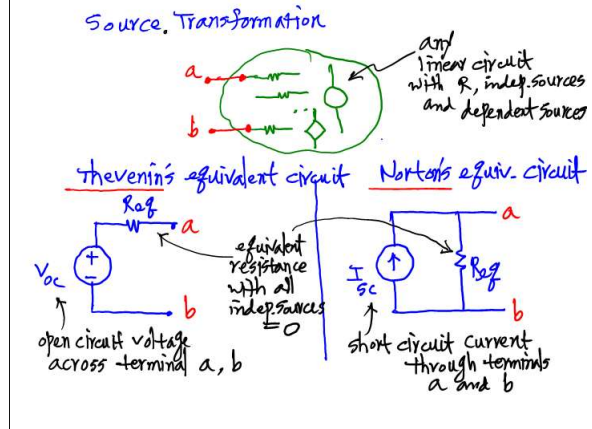


EE101 Lect 5 Jan 22, 2019
 Linear vs. nonlinear circuits (eBook pp 86-102)
 HW #3 (for Quiz 3 on Jan 29)

1. Prob. 3.3
2. Prob. 3.7
3. Prob. 3.9
4. Prob. 3.20
5. Prob. 3.26
6. Prob. 3.32
7. Prob. 3.48

8. Prob. 3.58



Fact 1. Thevenin's and Norton's equivalent circuits are equivalent to each other.

Example, For any (load) resistor connected between a and b will draw same current through it and also voltage across it.

Test case


$$I_{ab} = \frac{V_{oc}}{R_{eq} + R_L}$$

$$V_{ab} = V_{oc} \frac{R_L}{R_{eq} + R_L}$$

$$I_{sc} = \frac{V_{oc}}{R_{eq}}$$

$$V_{oc} = R_{eq} I_{sc}$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}}$$

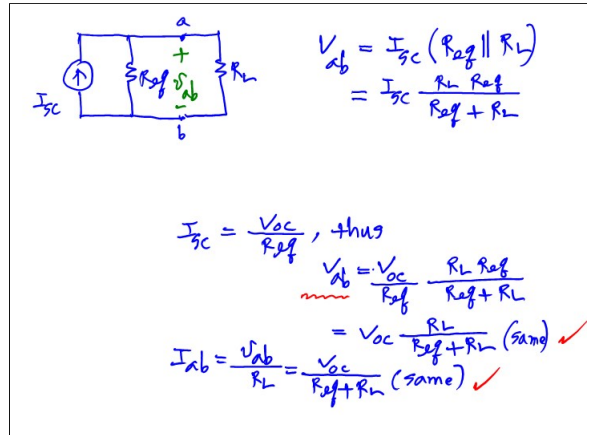

2.3. EQUIVALENT CIRCUITS

Table 2-5: Equivalent circuits.


Circuit	Equivalent
Series: R_1, R_2	$R_1 + R_2$
Parallel: R_1, R_2	$\frac{R_1 R_2}{R_1 + R_2}$
Series: v_1, v_2	$v_1 + v_2$
Parallel: i_1, i_2	$i_1 + i_2$
Source transformation	$\frac{V_{oc}}{R_{eq}}$

Y-Δ/Δ-Y transformation

same denom

same numerichy

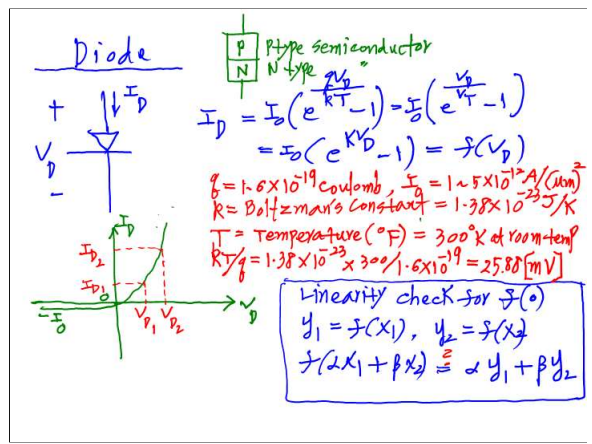For $R_1 = R_2 = R_3 \Rightarrow R_1 = R_2 = R_3 = R_{\Delta} / 3$
 For $R_1 = R_2 = R_3 \Rightarrow R_{\Delta} = R_1 = R_2 = R_3$



$$f(\alpha V_{D1} + \beta V_{D2}) = I_0 (e^{K(\alpha V_{D1} + \beta V_{D2})} - 1)$$

$$= I_0 (e^{\alpha K V_{D1}} e^{\beta K V_{D2}} - 1)$$

$$\neq \alpha \underbrace{I_0 (e^{K V_{D1}} - 1)}_{I_{D1}} + \beta \underbrace{I_0 (e^{K V_{D2}} - 1)}_{I_{D2}}$$

(nonlinear)

$$I_{D1} = I_0 (e^{K V_{D1}} - 1)$$

For $V_D = V_{D1} + \Delta V$

$$I_D = I_0 (e^{K(V_{D1} + \Delta V)} - 1)$$

$$= I_0 (e^{K V_{D1}} e^{K \Delta V} - 1)$$

$$= I_0 (e^{K V_{D1}} (1 + K \Delta V + \frac{(K \Delta V)^2}{2!} + \dots) - 1)$$

$$e^x = 1 + x + \frac{x^2}{2!} + \dots$$

$$\approx 0.5V, \Delta V \ll 1$$

$$= I_0 (e^{K V_{D1}} - 1 + e^{K V_{D1}} K \Delta V + \dots)$$

$$\approx I_{D1} + K I_0 e^{K V_{D1}} \Delta V$$

$$= I_{D1} + \frac{2 I_{D1}}{\Delta V} \Delta V$$

$$\left. \frac{\partial I_D}{\partial V_D} \right|_{V_{D1}} = \frac{\partial}{\partial V_D} [I_0 (e^{K V_D} - 1)] \Big|_{V_{D1}}$$

$$= K I_0 e^{K V_{D1}}$$

where $K = \frac{1}{K T} \approx \frac{1}{26 \text{ mV}}$
T = room temp.

For $V_{D1} = 0.7 \text{ V}$, $K V_{D1} = \frac{0.7}{0.026} = 26.9$

$$I_0 K e^{K V_{D1}} = 26.9 \times 4.927 \times 10^{11}$$

$$= 1.326 \times 10^{13} I_0 \approx 13 \text{ [A] huge!}$$

A simple diode model $I_0 = 1 \text{ nA case}$

A Diode Circuit

KVL

$$-5 + 100 I_D + V_D = 0$$



$$I_D = I_0 (e^{K V_D} - 1)$$

$$\Rightarrow 5 = 100 I_0 (e^{K V_D} - 1) + V_D = 0$$

nonlinear eq. !

$$I_D = \frac{5 - 0.7}{100} = \frac{4.3}{100} \text{ A}$$

$$= 43 \text{ mA}$$

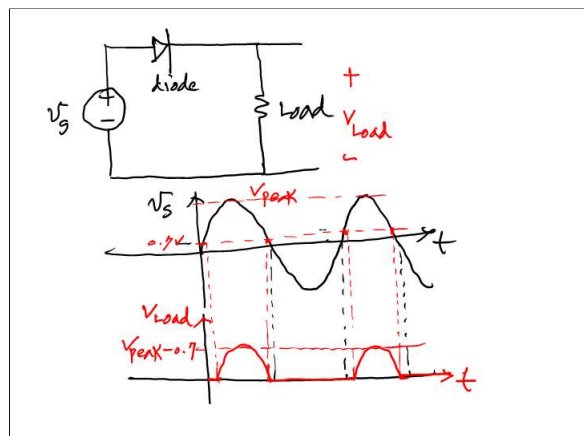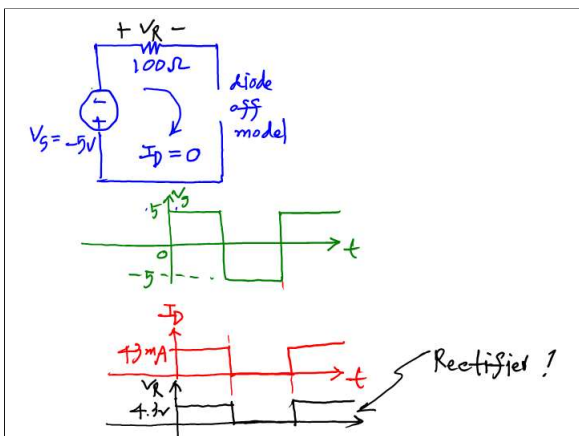

solution

$$KVL: -12 + 2kI + 0.7 + 3kI + 0.7 = 0$$

$$5kI = 12 - 0.7 - 0.7 = 10.6$$

$$I = \frac{10.6}{5k} = 2.12 \text{ [mA]}$$

If $I > 0$, diode 1 is on, but diode 2 off
 If $I < 0$, diode 1 off, diode 2 on
 If $I = 0$ both diodes off
 \Rightarrow In all cases, the circuit flows no current $I = 0$

Prob. 2.22

$$KVL: -10 + 2I + 3 \times I = 0$$

$$10 = 5I, I = \frac{10}{5} = 2A$$

Prob. 2.32, Find I_x

For $t < 0$,

ii) $3 \parallel 2 = \frac{3 \times 2}{3+2} = 1.2\Omega$
 iii) $3 \parallel 6 = \frac{3 \times 6}{3+6} = 2\Omega$
 iv) $4 \parallel 4 + 4 = 6\Omega$

$$I_x = \frac{15}{2+1.2} = \frac{15}{3.2} = 0.469A$$

For $t > 0$, $I_x = \frac{15}{2+2} = \frac{15}{4} = 3.75A$

Prob 2.67

Right side mesh : $KVL: -6 + 5I + 0.7 = 0$
 $I = \frac{6-0.7}{5} = 0.1A$

Left side mesh : $KVL?$ But diode is off!
 $I_1 = 0$

(If $I_1 < 0$, then KVL counterclockwise,
 $\Rightarrow +0.7 + 5I + 6 = 0$
 $I = -\frac{6+0.7}{5} = -0.126A$??
 this will violate KVL in the outer loop (not right) X

Prob. 2.70

$V_s(t)$

For $0 < t < 2$
 $I_2 = \frac{8-0.7}{14} = \frac{7.3}{14} = 50[mA]$
 $I_1 = 0$

For $2 < t < 4$
 $I_1 = -\frac{(8-0.7)}{7} = -100[mA]$
 $I_2 = 0$