
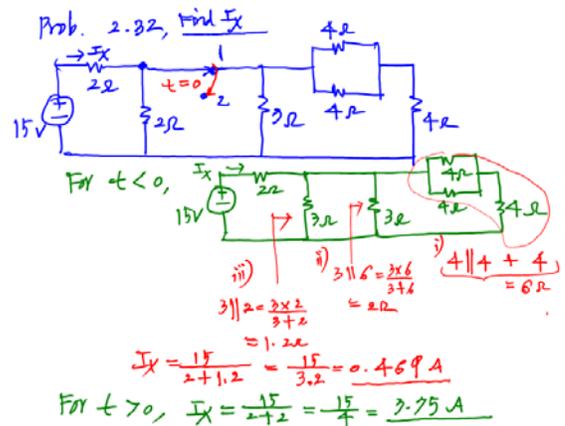
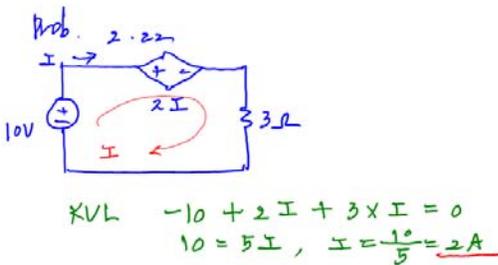
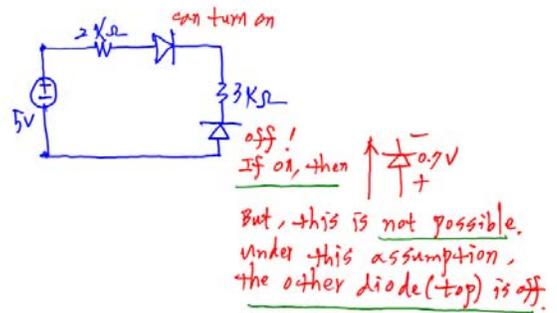
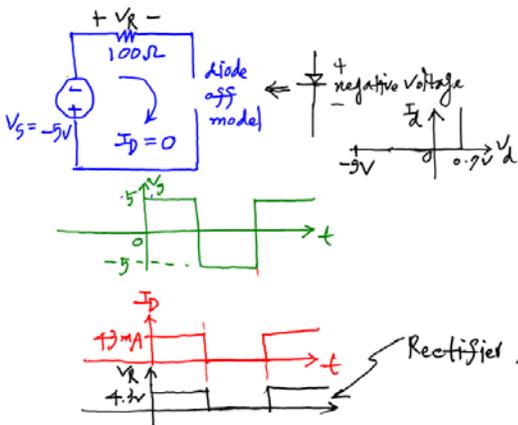


EE101 Lect 6 Jan 24, 2019

HW #3 (for Quiz 3 on Jan 29)

1. Prob. 3.3
2. Prob. 3.7
3. Prob. 3.11
4. Prob. 3.20
5. Prob. 3.26
6. Prob. 3.32
7. Prob. 3.48

A Diode Circuit

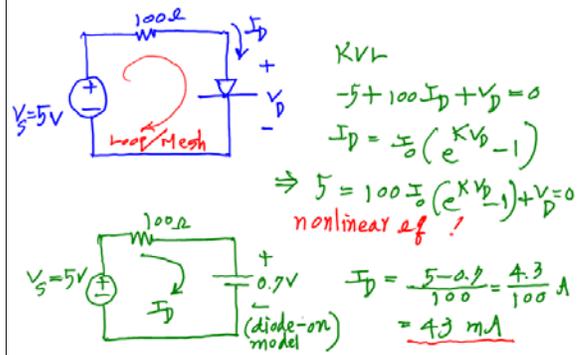

Prob. 2-67

Right side mesh : KVL  $-6 + 53I + 0.7 = 0$   
 $I = \frac{6-0.7}{53} = 0.1A$

Left side mesh : KVL ? But diode is off!  
 $I_1 = 0$

$I_D = I_1$  only at  $0[A]$  !  
 $\Rightarrow$  open circuit with  $0$  current !

Prob. 2-70

For  $0 < t < 2$   
 $I_2 = \frac{P-0.7}{146} = \frac{7.3}{146}$   
 $I_1 = 0$   
 $I_1 = 50[mA]$

For  $2 < t < 4$   
 $I_1 = -(8-0.7)/73 = -100[mA]$   
 $I_2 = 0$

Continued on Nodal Analysis,  
 Loop/Mesh analysis (Chap 3 pp. 115-143)

Prob. 2-37

If  $V_0/V_5 = 9$ , what is 'A'?

$V_{out} = 6\Omega \times I_{6\Omega} = 6\Omega \times A I_1 \left( \frac{1/6}{1/3 + 1/6} \right)$   
 $= 6 \times A I_1 \left( \frac{1}{2+1} \right) = 3A I_1$   
 $I_1 = \frac{V_5}{3+12} = \frac{V_5}{15}$   
 $\Rightarrow V_{out} = 2A \frac{V_5}{15}$   
 $\frac{V_{out}}{V_5} = 9 = \frac{2A}{15}, A = \frac{9 \times 15}{2} = 67.5$

Prob. 2-44

there can be a few different approaches to finding  $I$ .

(Method 1) Thevenin's equiv. ckt for the left side of terminals  $a + b$ .  
 open circuit voltage  $V_{oc} = ?$

Nodal analysis ( $V_2 = V_{oc}$ )  
 KCL at ①:  $5 = 3 + \frac{V_2}{2} + \frac{V_2 - 12}{10}$   
 KCL at ②:  $3 + \frac{V_2 - 12}{10} = \frac{V_2}{12}$  (1)

$5 = 3 + \frac{V_1}{2} + \frac{V_1 - V_2}{10}$  (1)  
 $\times 10 \Rightarrow 50 = 30 + 5V_1 + V_1 - V_2 \Rightarrow 6V_1 - V_2 = 20$  (1')  
 $3 + \frac{V_1 - V_2}{10} = \frac{V_2}{12}$  (2)  
 $\times 60 \Rightarrow 180 + 6V_1 - 6V_2 = 5V_2 \Rightarrow -6V_1 + 11V_2 = 180$  (2')  
 $(1)' + (2)' \Rightarrow 10V_2 = 20 \Rightarrow V_2 = 20V = V_{out}$

Next, let us find  $I_{SC}$ :

no current through 12Ω

KVL:  $2(I_{SC} - 3) + 10(I_{SC} - 3) = 0$   
 $12 I_{SC} = 40 \Rightarrow I_{SC} = 10/3 [A]$

Thus far, we found  $V_{OC} = 20 [V]$   
 $I_{SC} = 10/3 [A]$

Thevenin's equiv. ckt

$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{20 [V]}{10/3 [A]} = 6 [\Omega]$

$I = \frac{20}{6 + 4} = 2 [A]$  (ans)

Norton's equiv.

$I = \frac{10/3}{1 + 1} = \frac{10/3}{2} = 5/3 [A]$  (check)

Method 2: (By source transformation)

$10 \times 3 = 30V$

KVL:  $-10 + 2I_L - 30 + 10I_L + 3I_L = 0$   
 $14I_L = 40 \Rightarrow I_L = 40/14 = 20/7 [A]$

By current division  $I = I_L \frac{4}{4+12} = \frac{20}{7} \frac{4}{16} = 2/7 [A]$

Prob. 2.46  
 Determine I

Figure P2.46: Circuit for Problem 2.46.

Let's solve this prob. by first finding the Norton's equivalent circuit for a-b port (terminal)

Figure P2.46: Circuit for Problem 2.46.

Node Analysis

KCL at ①:  $2 = 3 + \frac{V_1}{4} + \frac{V_1 - V_2}{6}$  (1)  
 KCL at ②:  $3 + \frac{V_1 - V_2}{6} = \frac{V_2 - V_3}{3} + \frac{V_2 - 30 - V_3}{2}$  (2)  
 KCL at ③:  $\frac{V_2 - V_3}{3} + \frac{V_2 - 30 - V_3}{2} = \frac{V_3}{2}$  (3)

$$(1) \rightarrow 2V_1 - V_2 = -4 \quad (1)'$$

$$(2) \rightarrow -3V_1 + 9V_2 - 6V_3 = 156 \quad (2)'$$

$$(3) \rightarrow V_2 - 2V_3 = 20 \quad (3)'$$

$$3 \times (1)' + 2 \times (2)' \rightarrow$$

$$6V_1 - 3V_2 = -12$$

$$-6V_1 + 18V_2 - 12V_3 = 312$$

$$\hline 15V_2 - 12V_3 = 300 \quad (4)'$$

$$(4) - 15 \times (3)' \rightarrow$$

$$15V_2 - 12V_3 = 300$$

$$- (15V_2 - 30V_3 = 300)$$

$$\hline 18V_3 = 0 \quad \boxed{V_3 = 0 \text{ V}}$$

$$\text{From } (3)' \quad \boxed{V_2 = 20 \text{ V}}$$

$$\text{From } (1)' \quad 2V_1 - 20 = -4 \Rightarrow \boxed{V_1 = 8 \text{ V}}$$