

EE 101 Lecture 8, Jan 30, 2019.  
 Quiz #4 on Feb 5 (T) out of these

- [1] Prob. 3.58
- [2] Prob. 3.62
- [3] Prob. 3.64
- [4] Prob. 3.68
- [5] Prob. 3.72
- [6] Prob. 3.74
- [7] Prob. 3.77
- [8] Prob. 3.80

Quiz #3  
 Avg = 8.82  
 a = 2.08

Mesh Analysis

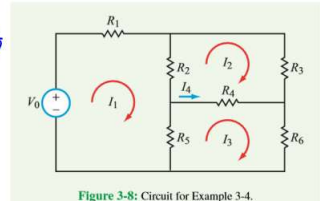


Figure 3-8: Circuit for Example 3-4.

Solution: (a) Applying the symmetry pattern inherent in the structure of the mesh-current equations, we have

$(R_1 + R_2 + R_3)I_1 - R_2I_2 - R_3I_3 = V_0$  (mesh 1), (3.15a)  
 $-R_2I_1 + (R_2 + R_3 + R_4)I_2 - R_4I_3 = 0$  (mesh 2), (3.15b)  
 $-R_3I_1 - R_4I_2 + (R_4 + R_5 + R_6)I_3 = 0$  (mesh 3), (3.15c)

negative because  $I_2, I_3$  are in opposite direction w.r.t.  $I_1$

total resistance in Mesh 1

Mesh 2 and Mesh 3

$I_1, I_3 \leftrightarrow I_2$   
 $I_1, I_2 \leftrightarrow I_3$

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & R_2 + R_3 + R_4 & -R_4 \\ -R_3 & -R_4 & R_4 + R_5 + R_6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_0 \\ 0 \\ 0 \end{bmatrix}$$

Figure 3-9: Mesh-current solution for a circuit containing a dependent source (Example 3-5).

$I_x = 4V_1$   
 $I_3 = I_x = 4V_1$   
 $V_1 = 2(I_1 - I_2)$   
 $I_3 = 8(I_1 - I_2)$

Mesh 1:  $-10 + 1(I_1 - I_3) + 2(I_1 - I_2) = 0$

Hence,  $I_3 = 4V_1 = 8(I_1 - I_2)$  (3.17)

After inserting Eq. (3.17) into Eqs. (3.16a and b) and collecting terms in  $I_1$  and  $I_2$ , we end up with

$-5I_1 + 6I_2 = 10$   
 $-10I_1 + 14I_2 = 0$


Solution of this pair of simultaneous equations gives

$I_1 = -14 \text{ A}, I_2 = -10 \text{ A}$

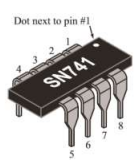
## CHAPTER 4 Operational Amplifiers

Contents

- Overview, 184
- 4-1 Op-Amp Characteristics, 184
- TB9 Display Technologies, 190
- 4-2 Negative Feedback, 195
- 4-3 Ideal Op-Amp Model, 196
- 4-4 Inverting Amplifier, 198
- 4-5 Inverting Summing Amplifier, 200
- TB10 Computer Memory Circuits, 203
- 4-6 Difference Amplifier, 206
- 4-7 Voltage Follower/Buffer, 208
- 4-8 Op-Amp Signal-Processing Circuits, 209
- 4-9 Instrumentation Amplifier, 214
- 4-10 Digital-to-Analog Converters (DAC), 216
- 4-11 The MOSFET as a Voltage-Controlled Current Source, 219
- TB11 Circuit Simulation Software, 225
- 4-12 Application Note: Neural Probes, 229
- 4-13 Multisim Analysis, 230
- Summary, 235
- Problems, 236



The introduction of the operational amplifier chip in the 1960s has led to the development of a wide array of signal processing circuits, enabling the creation of an ever-increasing number of electronic applications.

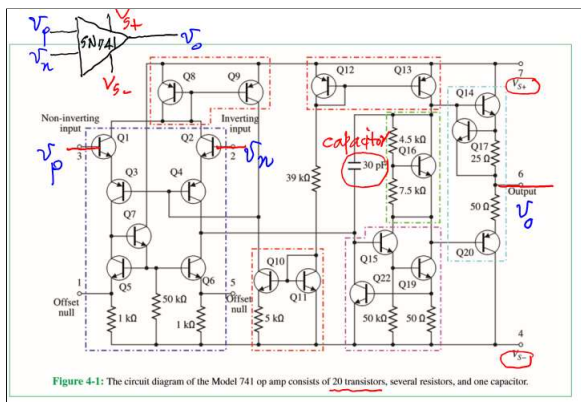

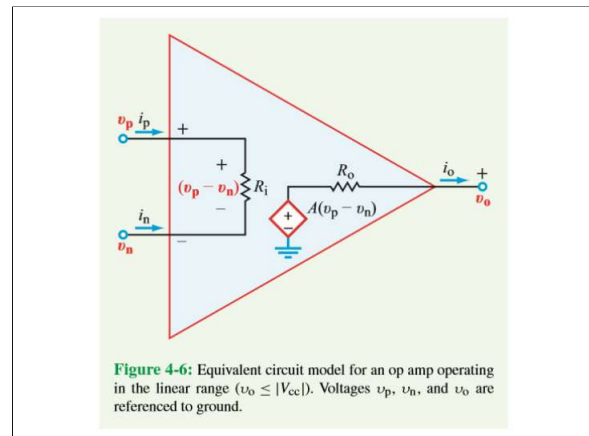
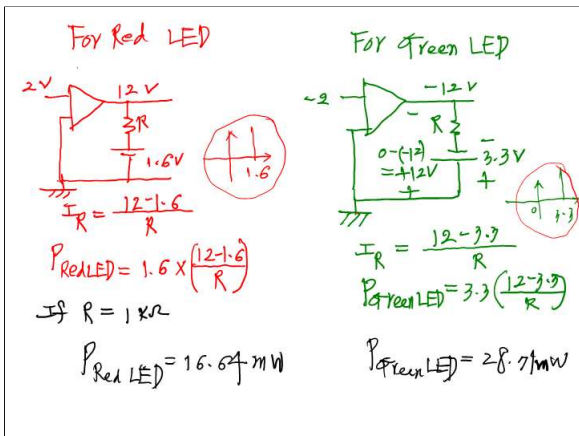
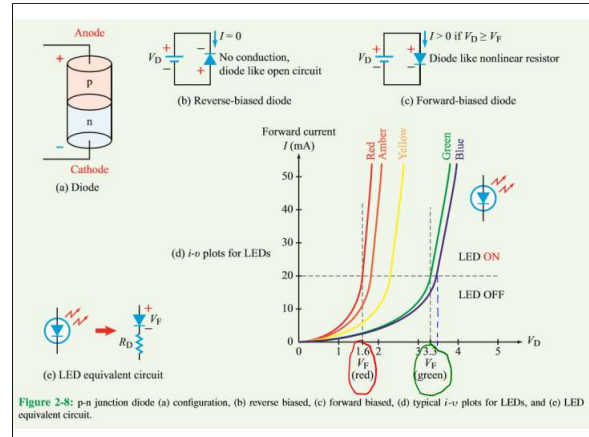
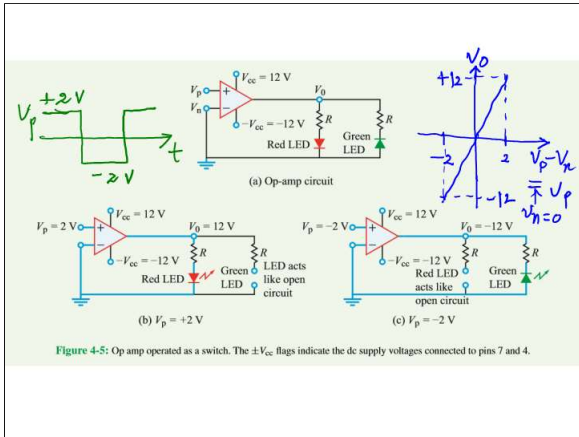
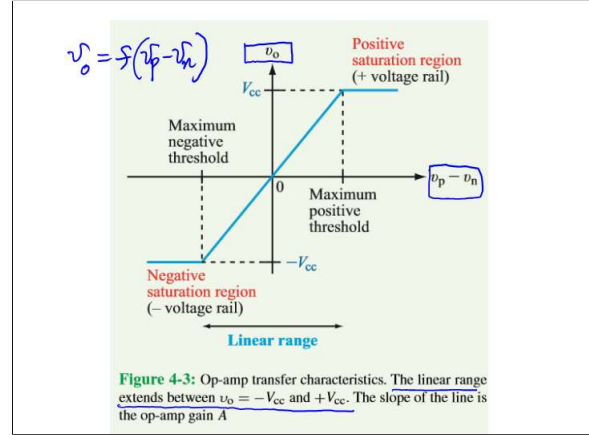
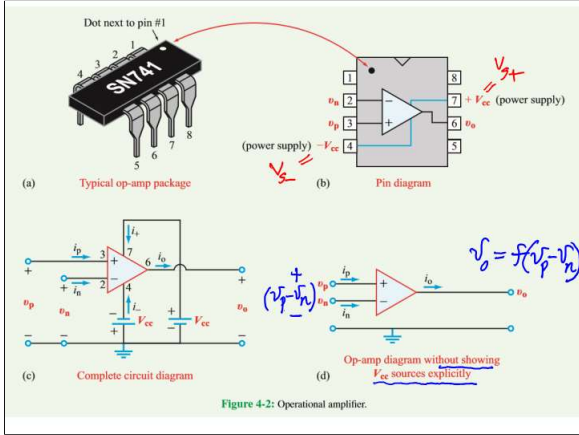


Table 4-1: Characteristics and typical ranges of op-amp parameters. The rightmost column represents the values assumed by the ideal op-amp model.

Op-Amp Characteristics	Parameter	Typical Range	Ideal Op Amp
• Linear input-output response	Open-loop gain $A$	$10^4$ to $10^5$ (V/V)	$\infty$
• High input resistance	Input resistance $R_i$	$10^9$ to $10^{13}$ $\Omega$	$\infty$ $\Omega$
• Low output resistance	Output resistance $R_o$	1 to 100 $\Omega$	0 $\Omega$
• Very high gain	Supply voltage $V_{cc}$	5 to 24 V	As specified by manufacturer



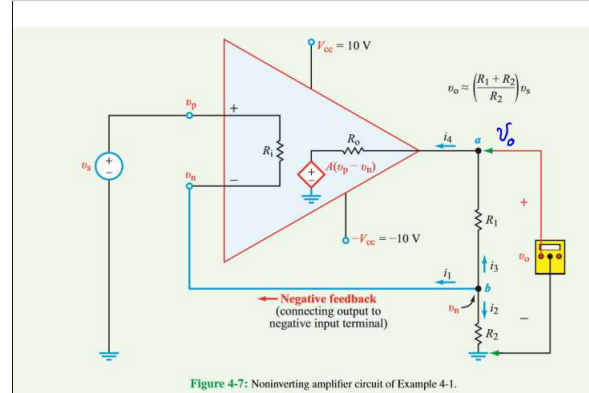


Figure 4-7: Noninverting amplifier circuit of Example 4-1.

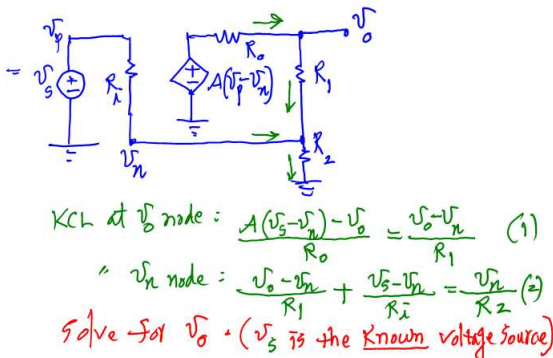

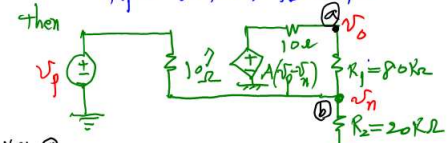For  $\begin{cases} R_i = 10^6 - 10^9 \Omega, \text{ let's assume } R_i = 10 \text{ M}\Omega = 10^7 \Omega \\ R_o = 1 \text{ to } 100 \Omega, \quad R_o = 10 \Omega \\ A = 10^4 \sim 10^5 \text{ [V/V]}, \quad A = 10^6 \\ R_1 = 80 \text{ k}\Omega, \quad R_2 = 20 \text{ k}\Omega \end{cases}$



KCL @  $v_o$

$$\frac{10^6(v_s - v_n) - v_o}{10} = \frac{v_o - v_n}{80 \times 10^3} \quad (2)$$

$$\frac{v_o - v_n}{80 \times 10^3} + \frac{v_s - v_n}{10^7} = \frac{v_n}{20 \times 10^3} \quad (3)$$

$$(2) \times (8 \times 10^3) \rightarrow 8 \times 10^9 (v_s - v_n) - 8 \times 10^3 v_o = v_o - v_n$$

$$8 \times 10^9 v_s = [8 \times 10^9 - 1] v_n + (8 \times 10^3 + 1) v_o$$

$$(3) \times (8 \times 10^7) \rightarrow 10^3 (v_o - v_n) + 8 (v_s - v_n) = 4 \times 10^4 v_n$$

$$8 v_s = (10^3 + 8 + 4 \times 10^4) v_n - 10^3 v_o$$

(2)' can be approximated as

$$8 \times 10^9 v_s = 8 \times 10^9 v_n + 8 \times 10^3 v_o \quad (4)$$

(3)'  $\Rightarrow 8 v_s = 41 \times 10^3 v_n - 10^3 v_o$  (5)

$$(4) + 8 \times (5) \Rightarrow (8 \times 10^9 + 64) v_s = (8 \times 10^9 + 328 \times 10^3) v_n$$

$$v_n = v_s \left( \frac{8 \times 10^9 + 64}{8 \times 10^9 + 328 \times 10^3} \right), \quad v_o = \frac{41 \times 10^3 v_n - 8 v_s}{10^3}$$

$$= 41 v_n - 8 \times 10^3 v_s$$

$$v_s - v_n = v_s \left( 1 - \frac{8 \times 10^9 + 64}{8 \times 10^9 + 328 \times 10^3} \right)$$

$$= v_s \frac{8 \times 10^9 + 328 \times 10^3 - 8 \times 10^9 - 64}{8 \times 10^9 + 328 \times 10^3}$$

$$= v_s \frac{328 \times 10^3 - 64}{8 \times 10^9 + 328 \times 10^3}$$

$$v_o = 41 v_n - 8 \times 10^3 v_s$$

$$= \left( 41 \times \frac{8 \times 10^9 + 64}{8 \times 10^9 + 328 \times 10^3} - 8 \times 10^3 \right) v_s$$

$$\frac{v_o}{v_s - v_n} = \frac{41(8 \times 10^9 + 64) - 8 \times 10^3}{328 \times 10^3 - 64}$$

$$\approx \frac{41 \times 8 \times 10^9}{328 \times 10^3} = 10^6$$

