

EE101 Lecture 9, Feb 5 2019
 Midterm Exam on Feb 7
 1 page of formulas, tables & Calculator allowed.
 coverage (up to Jan 31)

- Ohm's Law
 - KCL } for calculation of voltages (node, branch)
 - KVL } and currents (mesh, branch), Power (+, -)
 - Equivalent circuit (Thevenin's, Norton's)
 - Diodes, Diode circuits (including LEDs)
 - Op-Amp circuit.
- 5 Problems for 95 min examination

HW # 5 (for Quiz 5)

- [1] Prob 4.13 [6] 4.43
- [2] 4.18 [7] m 4.3
- [3] 4.20 [8] m 4.4
- [4] 4.25
- [5] 4.35

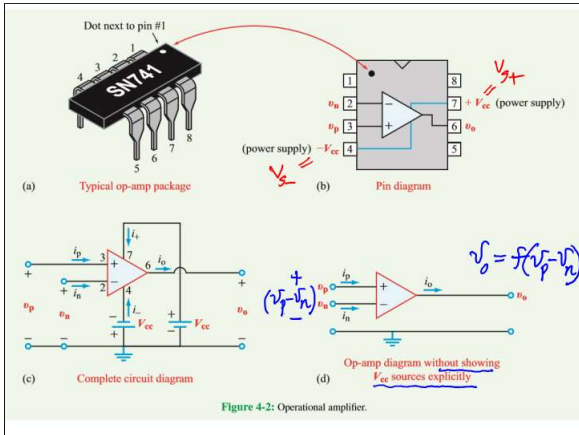


Figure 4-2: Operational amplifier.

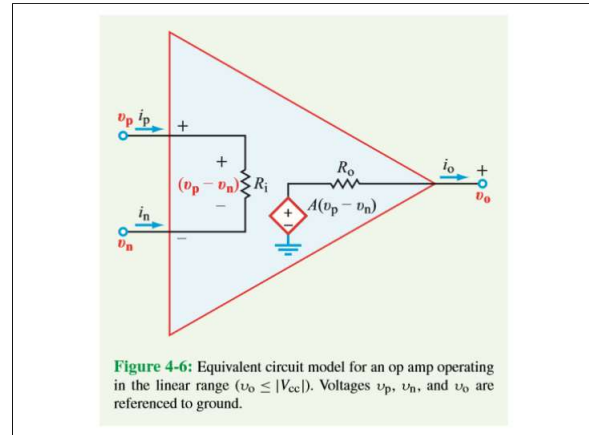


Figure 4-6: Equivalent circuit model for an op amp operating in the linear range ($v_o \leq |V_{cc}|$). Voltages v_p , v_n , and v_o are referenced to ground.

Table 4-1: Characteristics and typical ranges of op-amp parameters. The rightmost column represents the values assumed by the ideal op-amp model.

Op-Amp Characteristics	Parameter	Typical Range	Ideal Op Amp
• Linear input-output response	Open-loop gain A	10^4 to 10^5 (V/V)	∞
• High input resistance	Input resistance R_i	10^6 to 10^{13} Ω	∞ Ω
• Low output resistance	Output resistance R_o	1 to 100 Ω	0 Ω
• Very high gain	Supply voltage V_{cc}	5 to 24 V	As specified by manufacturer


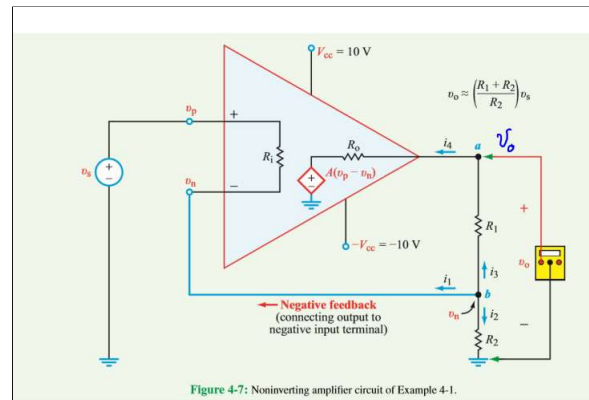
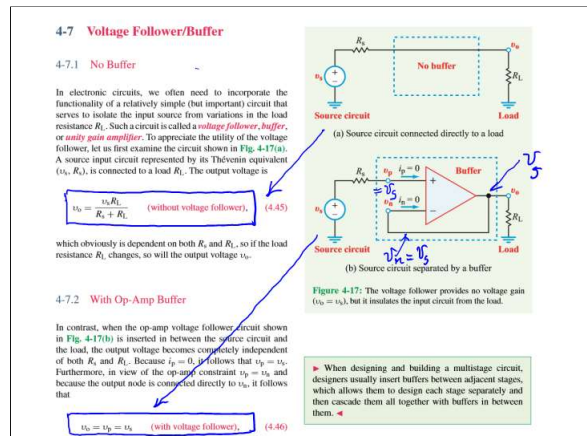
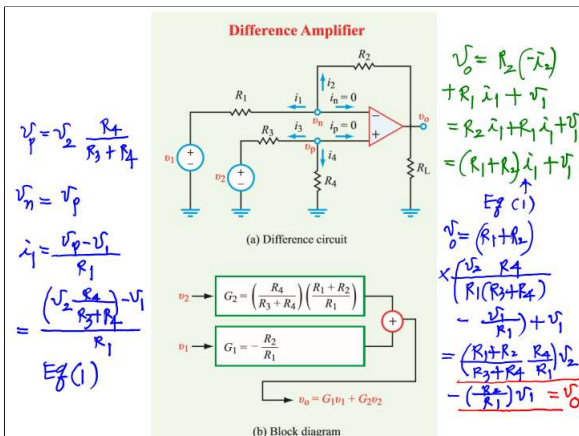
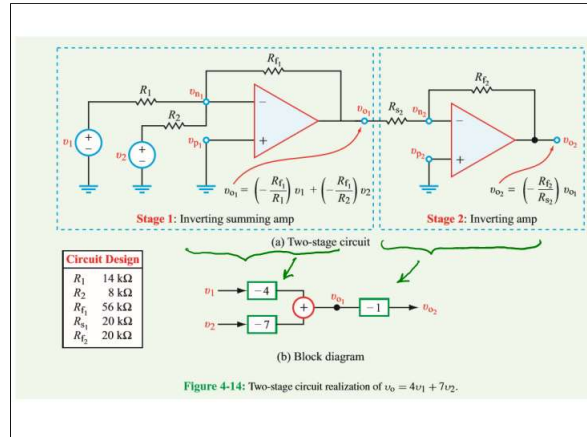
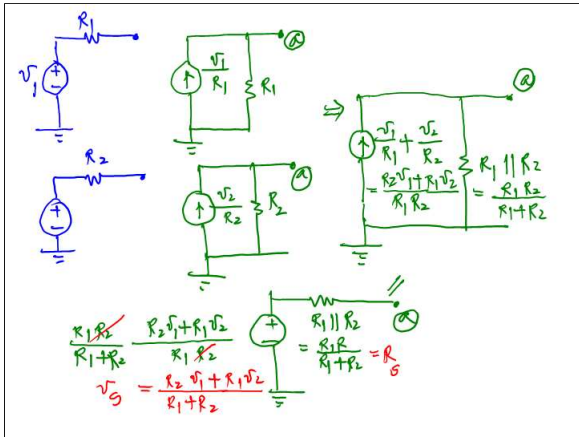
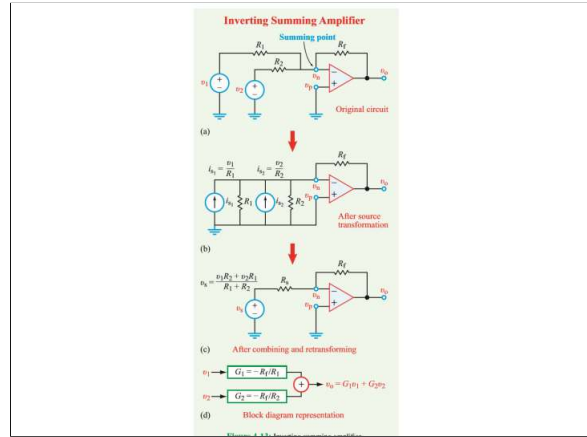


Figure 4-7: Noninverting amplifier circuit of Example 4-1.

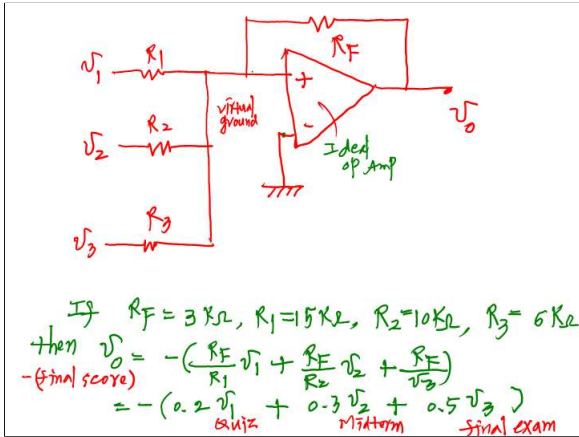

Basic Rules of Op-Amp Circuits

- (1) KCL and KVL always apply everywhere in the circuit, but KCL is inapplicable at the output node when applying the ideal op-amp model. All other circuit-analysis tools can be applied to op-amp circuits.
- (2) The op amp will operate in the linear range so long as $|v_o| < |V_{cc}|$.
- (3) The ideal op-amp model assumes that the source resistance R_s (connected to terminals v_p or v_n) is much smaller than the op-amp input resistance R_i (which usually is no less than $10\text{ M}\Omega$), and the load resistance R_L is much larger than the op-amp output resistance R_o (which is on the order of tens of ohms).
- (4) The ideal op-amp constraints are $i_p = i_n = 0$ and $v_p = v_n$.

4.11 Determine the output voltage for the circuit in Fig. P4.11 and specify the linear range for v_s , given that $V_{cc} = 15\text{ V}$ and $V_0 = 0$.

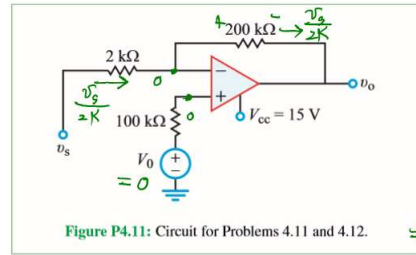


Figure P4.11: Circuit for Problems 4.11 and 4.12.


$$v_o = -\frac{v_s}{2k} \times 200k = -100v_s$$

$$v_o \text{ max} = 15V$$

$$v_o \text{ min} = -15V$$

$$\Rightarrow |v_s| < 150 \text{ mV}$$

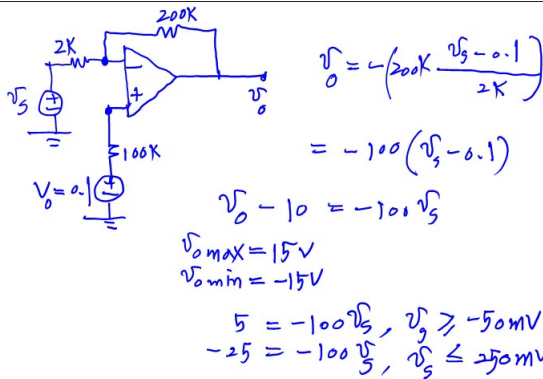4.12 Repeat Problem 4.11 for $V_0 = 0.1\text{ V}$.



* (b) If $R_L = 12\text{ k}\Omega$, choose R_f so that $G_i = -15$.

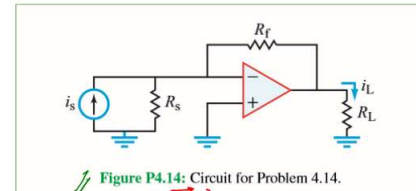


Figure P4.14: Circuit for Problem 4.14.

$$G_i = \frac{i_L}{i_s}$$

$$v_L = -R_f i_s$$

$$i_L = -\frac{R_f}{R_L} i_s$$

$$G_i = \frac{i_L}{i_s} = -\frac{R_f}{R_L} = -15$$

$$\Rightarrow R_f = 180k$$

4.17 Determine v_o across the $10\text{ k}\Omega$ resistor in the circuit of Fig. P4.17.


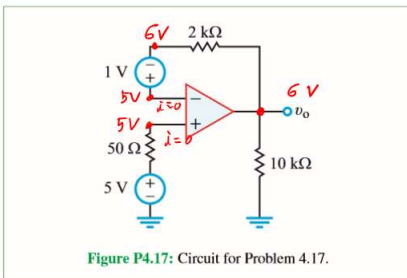


Figure P4.17: Circuit for Problem 4.17.

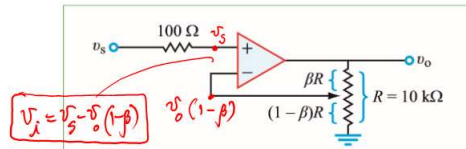4.22 The circuit in Fig. P4.22 uses a potentiometer whose total resistance is $R = 10\text{ k}\Omega$ with the upper section being βR and the bottom section $(1 - \beta)R$. The wiper can change β from 0 to 0.9. Obtain an expression for $G = v_o/v_s$ in terms of β and evaluate the range of G (as β is varied over its own allowable range).



$$v_i = v_s - v_o(1-\beta)$$

$$v_o = A v_i$$

$$= A [v_s - v_o(1-\beta)]$$

$$\frac{v_o}{v_s} = G = \frac{A}{1 + (1-\beta)A}$$

$$\text{when } A \rightarrow \infty, G = \frac{1}{1-\beta}$$

4.23 For the circuit in Fig. P4.23, obtain an expression for voltage gain $G = v_o/v_s$.

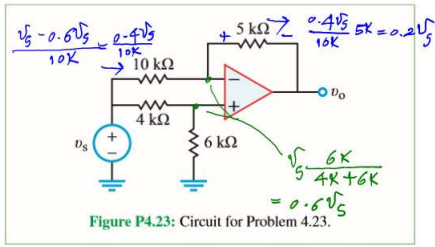


Figure P4.23: Circuit for Problem 4.23.

$$v_o = -0.2v_s + 0.6v_s = 0.4v_s$$

$$\frac{v_o}{v_s} = 0.4 = 4$$

*4.24 Find the value of v_o in the circuit in Fig. P4.24.

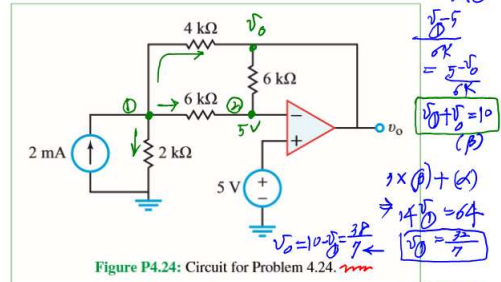


Figure P4.24: Circuit for Problem 4.24.

$$\text{KCL at } \textcircled{1} = 2 \times 10^{-3} = \frac{v_o}{2k} + \frac{v_o - 5}{6k} + \frac{v_o - v_o}{4k} \Rightarrow 11v_o - 30 = 24$$

$$\times 12k \quad 2 \times 12 = 6v_o + 2v_o - 10 + 3v_o - 3v_o \quad (2)$$