

solution

EE101 Final Examination, March 20, 2019

Name _____ Student ID _____

2 page of formulas and tables only are allowed. But, you must show all details of your work even when you apply formulas to get full credits. Otherwise, you will lose points.

Problem 1 [10] _____

Problem 2 [10] _____

Problem 3 [10] _____

Problem 4 [10] _____

Problem 5 [10] _____

Problem 6 [10] _____

Problem 7 [10] _____

Problem 8 [10] _____

Problem 9 [10] _____

Problem 10 [10] _____

Bonus Q1 [5] _____

Bonus Q2 [5] _____

TOTAL [100] _____

Bonus [10] _____

Screening Question:


Write down the voltage-current relations (voltage expressed in terms of current) for

Resistor R: $V = R i$


Inductor L: $V = L \frac{di}{dt}$

Capacitor C: $i = C \frac{dv}{dt}$

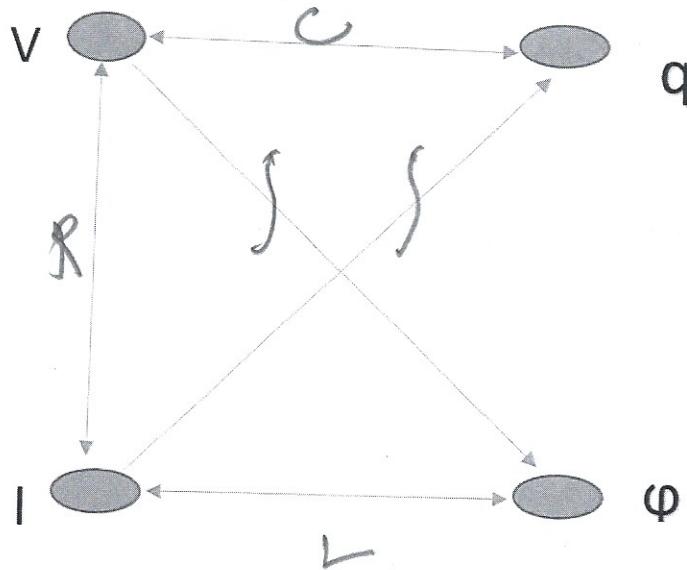Insert R, L, C into 3 links below, and integration or differentiation signs.



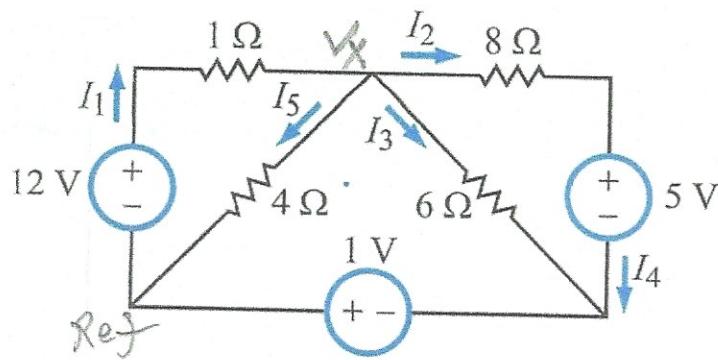[1] (10 points) Consider the following circuit with three independent voltage sources. Find the power consumed in the 4Ω resistor.



Answer= 592 [W].

$$\frac{12 - V_x}{1} = \frac{V_x}{4} + \frac{V_x - (-1)}{6} + \frac{V_x - (5 - 1)}{8}$$

$$\times 24 \Rightarrow 24(12 - V_x) = 6V_x + 4(V_x + 1) + 3(V_x - 4)$$

$$24 \times 12 + 2 \times 4 = (24 + 6 + 4 + 3)V_x$$

$$V_x = \frac{296}{37} = 8$$


$$P_{4\Omega} = \frac{V_x^2}{4} = \frac{8^2}{4} = 16 \text{ [W]}$$

ans

not correct
answer

-5

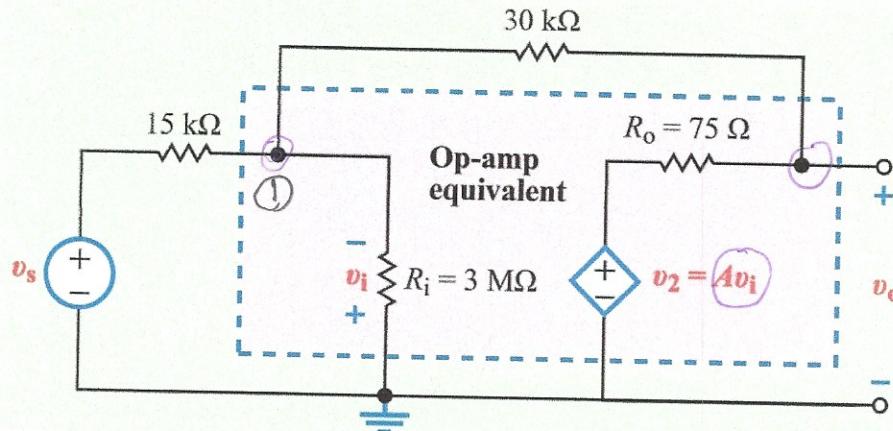[2] (10 points) Find the voltage gain $G = v_o/v_s$ for A=1001.



correct answer

but not correct
step

8

correct answer
& steps

10

1 — At node ①, KCL : $\frac{v_s - (-v_i)}{15k} = \frac{-v_i - v_o}{30k} + \frac{-v_i}{3000k}$

$$\times 3000k \Rightarrow 200(v_s + v_i) = -100(v_i + v_o) - v_i \quad (1)$$

2 — Also $v_o = 1001v_i + 75\left(\frac{-v_i - v_o}{30k}\right)$

$$v_o = 1001v_i - \frac{v_i + v_o}{400}$$
$$= \left(1001 - \frac{1}{400}\right)v_i - \frac{v_o}{400}$$

$$v_o \left(1 + \frac{1}{400}\right) = \left(1001 - \frac{1}{400}\right)v_i$$

$$\times 400 \Rightarrow 401v_o = (1001 \times 400 - 1)v_i$$

$$\therefore v_i = \frac{401}{1001 \times 400 - 1}v_o \quad (2)$$

From (1) & (2),


$$200v_s = -301v_i - 100v_o$$
$$= -\left[301\left(\frac{401}{1001 \times 400 - 1}\right) + 100\right]v_o$$

$$\frac{v_o}{v_s} = \frac{200}{-\left[301\left(\frac{401}{1001 \times 400 - 1}\right) + 100\right]} = -\frac{200}{100.3} = -1.99$$


$$= 9$$

Ans

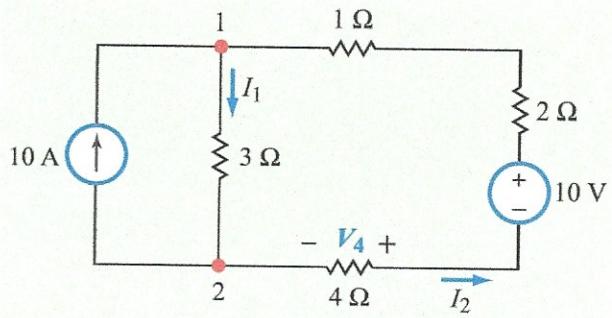[3] (10 points) Find the current I_2 in the circuit shown below.



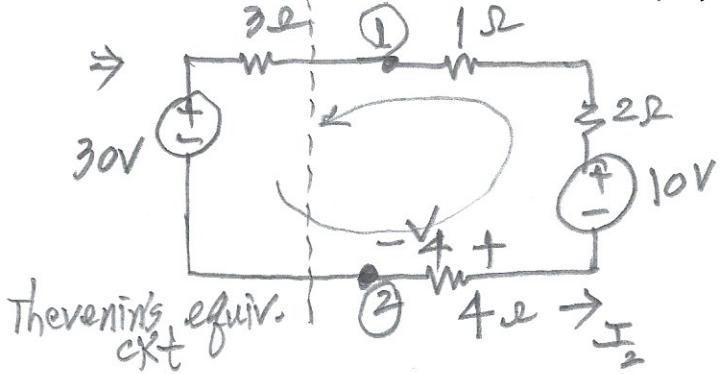Hint: A source transformation would simplify the problem.



Thevenin's equiv.
cxt

KVL


$$4I_2 - 10 + 2I_2 + 1I_2 + 3I_2 + 30 = 0$$

$$10I_2 = -20$$

$$\underline{\underline{I_2 = -2 [A]}}$$

(ans)

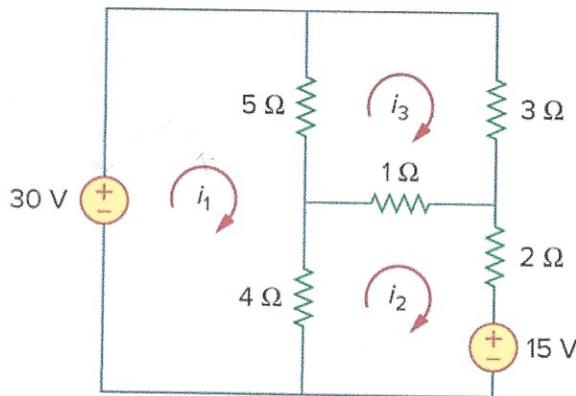[4] (10 points) Find the power supplied by the 30V voltage source by finding mesh currents i_1 , i_2 and i_3 .



$$P_{30V} = 30(-i_1)$$

(a) (5 points) Write down a matrix equation to find mesh currents as $Ax=b$, where A is a 3×3 matrix.

$$-30 + 5(i_1 - i_3) + 4(i_1 - i_2) = 0$$

$$4(i_2 - i_1) + 1(i_2 - i_3) + 2i_2 + 15 = 0$$

$$5(i_3 - i_1) + 3i_3 + 1(i_3 - i_2) = 0$$

$$\begin{bmatrix} 9 & -4 & -5 \\ -4 & 7 & -1 \\ -5 & -1 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30 \\ -15 \\ 0 \end{bmatrix} \quad A \begin{bmatrix} x \\ y \\ z \end{bmatrix} = b$$

(b) (5 points) Then find the mesh current i_1 and then the power supplied by the 30V voltage source.


$$i_1 = \frac{\begin{vmatrix} 30 & -4 & -5 \\ -15 & 7 & -1 \\ 0 & -1 & 9 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -5 \\ -4 & 7 & -1 \\ -5 & -1 & 9 \end{vmatrix}} = \frac{30 \times 7 \times 9 + (-1)(-15)(-5) + 0}{9 \times 7 \times 9 + (-4)(-1)(-5) + (-5)(-4)(-1)} = \frac{-30 \times (-15)(-4)9 - 30(-1)(-1)}{-(-5)(7)(-5) - (-4)(-4)9 - 9(-1)(-1)} = \frac{1245}{567 - 20 - 20 - 175 - 144 - 9} = 1.99$$

$$P_{30V} = -30(6.256) = -187.69 [W]$$


ans

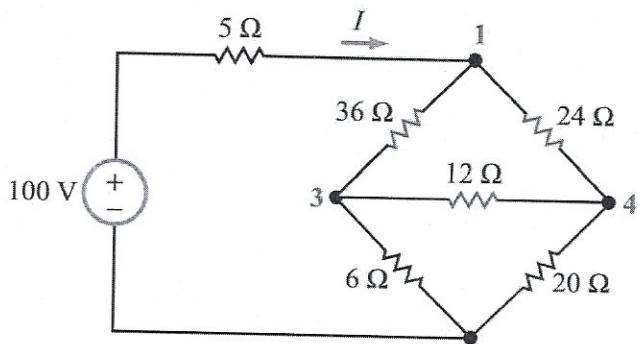187.69 [W] is supplied

[5] (10 points) Find the current I in the circuit below.





$\Delta - \gamma$ Transformation

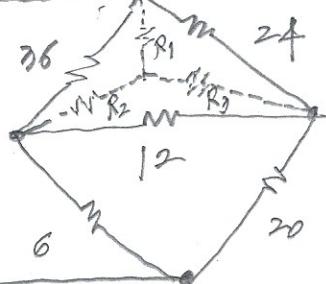

$$R_1 = \frac{36 \times 24}{36 + 24 + 12} = \frac{36 \times 24}{72} = 12 \Omega$$

$$R_2 = \frac{36 \times 12}{36 + 24 + 12} = \frac{36 \times 12}{72} = 6 \Omega$$
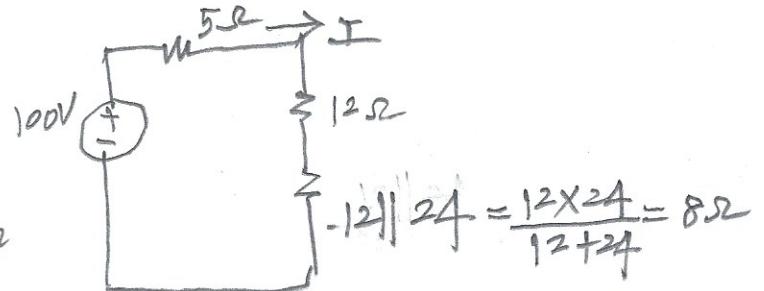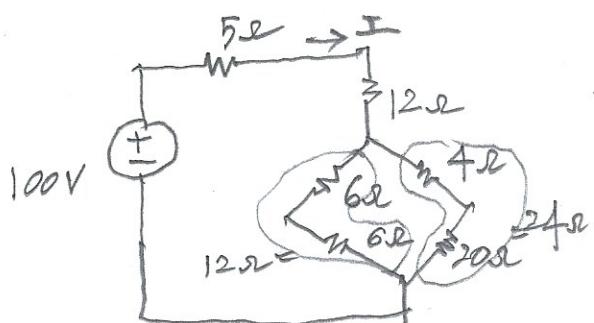
$$R_3 = \frac{24 \times 12}{36 + 24 + 12} = \frac{24 \times 12}{72} = 4 \Omega$$




$$I = \frac{100V}{(5 + 12 + 8)\Omega} = \frac{100V}{25\Omega} = 4 [A]$$

(ans)

[6] (10 points) Determine the range of the source voltage v_s for the output voltage v_o to be in the linear range without saturation. Assume that the Op amp is ideal.

Correct: 10

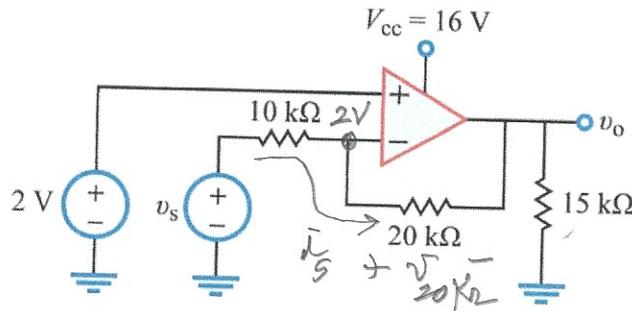

incorrect v_s : 5

try: 3

$$i_S = \frac{v_s - 2}{10k\Omega}$$

$$v_{20k\Omega} = 20k\Omega i_S = 20k\Omega \left(\frac{v_s - 2}{10k\Omega} \right) = 2v_s - 4$$

$$v_o = -v_{20k\Omega} + 2 = -2v_s + 4 + 2 = -2v_s + 6$$

$$-16V \leq v_o \leq 16V$$


$$-16 \leq -2v_s + 6 \leq 16V$$

$$-22 \leq -2v_s \leq 10V$$


$$22 \geq 2v_s \geq -10V$$

$$11V \geq v_s \geq -5V$$

(ans)

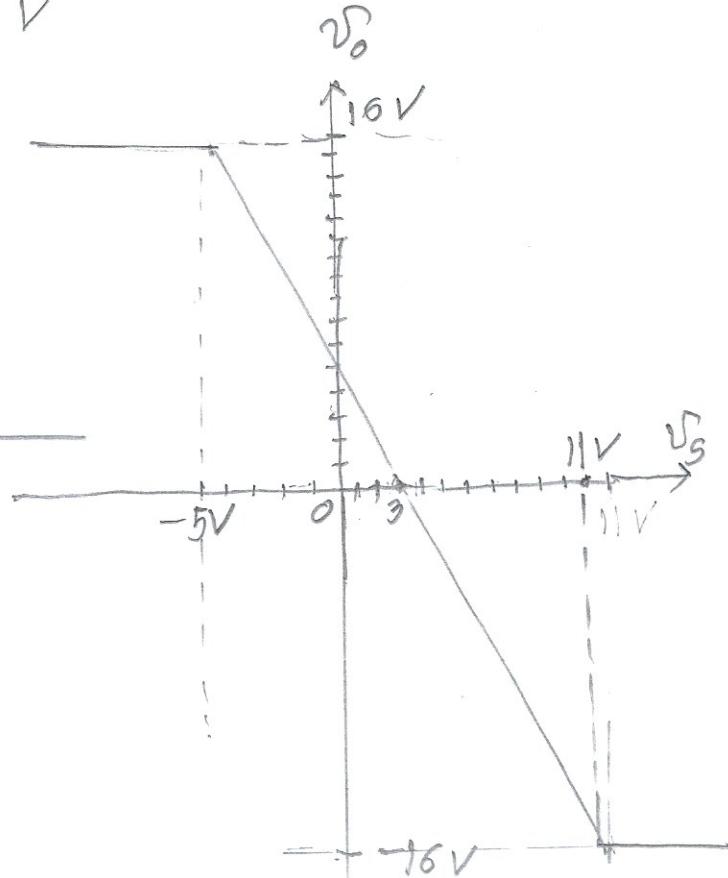

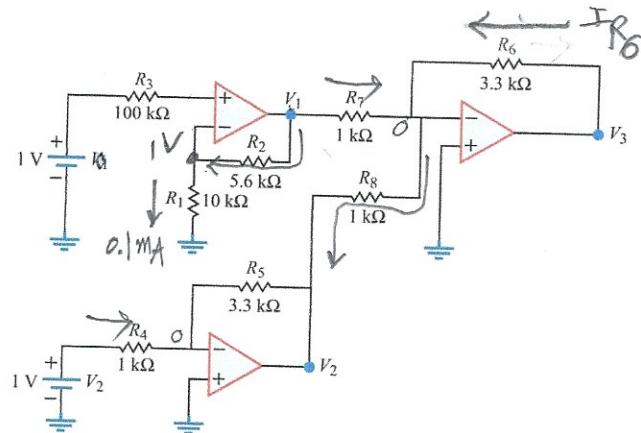[7] (10 points) Find the output voltage v_3 in the ideal Op amp circuit below.



correct : 10 / 8

incorrect : 5

try: 3

other: 0

$$V_1 = 1 + 5.6 \times (0.1 \text{ mA}) = 1.56 \text{ V}$$

$$I_{R_7} = \frac{V_1 - 0}{1 \text{ k}\Omega} = 1.56 \text{ mA}$$

$$I_{R_4} = \frac{1 - 0}{1 \text{ k}\Omega} = 1 \text{ mA} = I_{R_5}$$


$$V_2 = -3.3 \times I_{R_5} = -3.3 \text{ V}$$

$$I_{R_8} = \frac{0 - V_2}{1 \text{ k}\Omega} = \frac{3.3 \text{ V}}{1 \text{ k}\Omega} = 3.3 \text{ mA}$$


$$I_{R_6} = I_{R_8} - I_{R_7} = 3.3 \text{ mA} - 1.56 \text{ mA} = 1.74 \text{ mA}$$

$$V_3 = I_{R_6} R_6 = 1.74 \text{ mA} (3.3 \text{ k}\Omega) = + \underline{\underline{5.742 \text{ V}}} \\ (\text{ans})$$

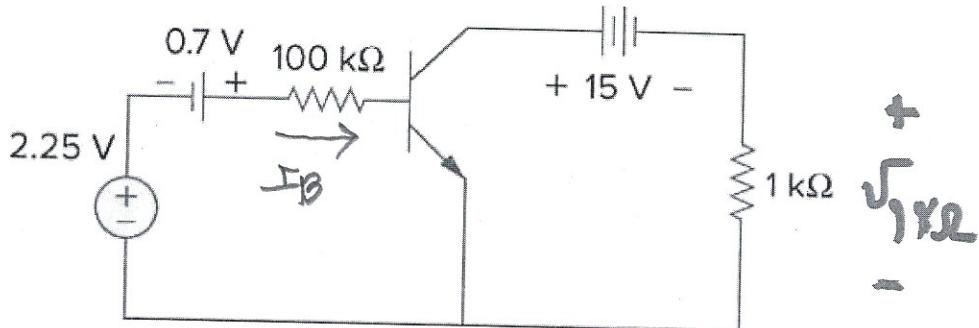[8] (10 points) Find the voltage across the load resistor $1\text{ k}\Omega$ and the power delivered to it.
 For BJT, $V_{BE(on)} = 0.7 \text{ V}$, $\beta = 100$



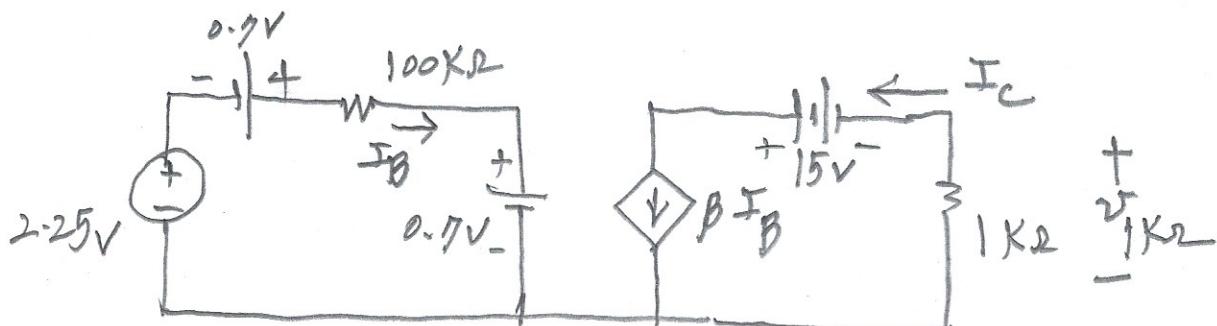Answer $V_{1\text{k}\Omega} = -2.25 \text{ [V]}$ Power = 5.06 [mW]



Using Mesh analysis; $-2.25 - 0.7 + 100\text{k}\Omega I_B + 0.7 = 0$

$$\Rightarrow I_B = \frac{-2.25 \text{ V}}{100\text{k}\Omega} = 22.5 \times 10^{-6} \text{ [A]} = 22.5 \text{ [mA]}$$


$$I_C = \beta I_B = 100 \times 22.5 \times 10^{-6} = 2.25 \text{ [mA]}$$

$$V_{1\text{k}\Omega} = -1\text{k}\Omega I_C = -1\text{k}\Omega \times 2.25 \text{ [mA]} = -2.25 \text{ [V]}$$

$$P_{1\text{k}\Omega} = I^2 R = \frac{V_{1\text{k}\Omega}^2}{1\text{k}\Omega} = \frac{2.25^2}{1 \times 10^3} = 5.06 \text{ [mW]}$$

[9] (10 points) Find $v_C(t)$ for $t > 0$ in the circuit below. Choose the time-domain solution method using the table attached. $C = 1 \text{ F}$, $L = 1 \text{ H}$

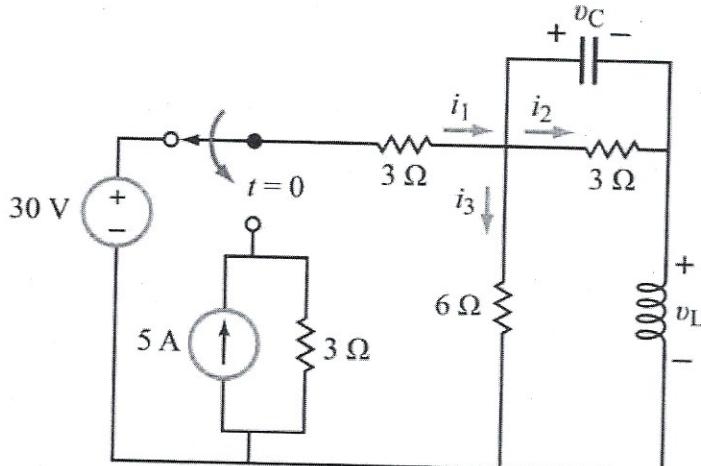Find a second-order differential equation in terms of $v_C(t)$.




(ans)

$$\frac{d^2v_C}{dt^2} + 3\frac{1}{3}\frac{dv_C}{dt} + 2v_C = 7.5$$

$$v_C(0) = 12 \text{ [V]}$$


$$v_C'(0) = 0$$

For $t < 0$

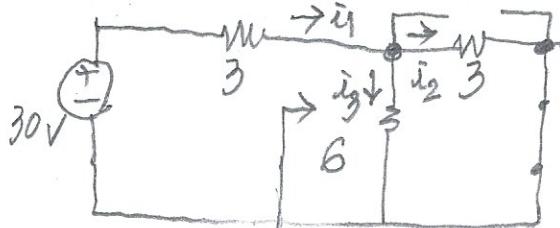


$$\begin{cases} i_1(0-) = \frac{30 \text{ [V]}}{(3+2) \text{ [Ω]}} = 6 \text{ [A]} \\ i_2(0) = i_L(0) = 6 \times \frac{6}{6+3} = 4 \text{ [A]} = i_L(0) \\ v_C(0) = 3 \times 4 = 12 \text{ [V]} = v_C(0) \end{cases}$$

For $t > 0$

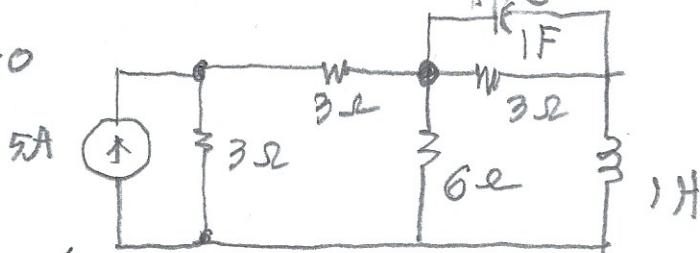

1H

source transformation

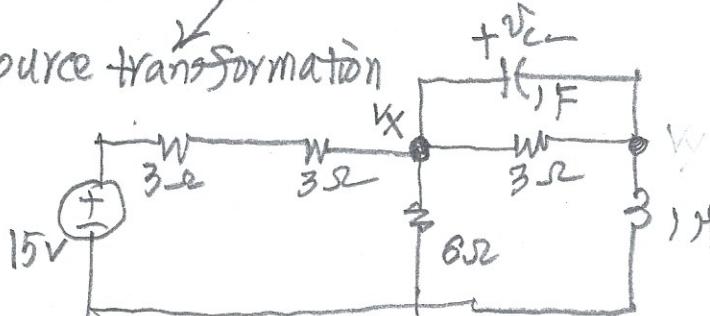

KCL at V_X node

$$\frac{15 - V_X}{6} = \frac{V_X}{6} + 1 \frac{dv_C}{dt} + \frac{v_C}{3} \quad (1)$$

$$V_X = V_C + 1 \frac{dv_C}{dt}$$

$$= V_C + \frac{d}{dt} \left(\frac{dv_C}{dt} + \frac{2v_C}{3} \right)$$

$$= V_C + \frac{d^2v_C}{dt^2} + \frac{1}{3} \frac{dv_C}{dt} \quad (2)$$

Multiply both sides of (1) by 6 \Rightarrow


$$15 - V_X = V_X + 6 \frac{dv_C}{dt} + 2v_C \quad (1')$$

$$15 = 2(V_C + \frac{d^2v_C}{dt^2} + \frac{1}{3} \frac{dv_C}{dt}) + 6 \frac{dv_C}{dt} + 2v_C \quad (1')$$


$$7.5 = \frac{d^2v_C}{dt^2} + 3\frac{1}{3} \frac{dv_C}{dt} + 2v_C \quad (\text{ans})$$

This problem was supposedly right problem for [9].

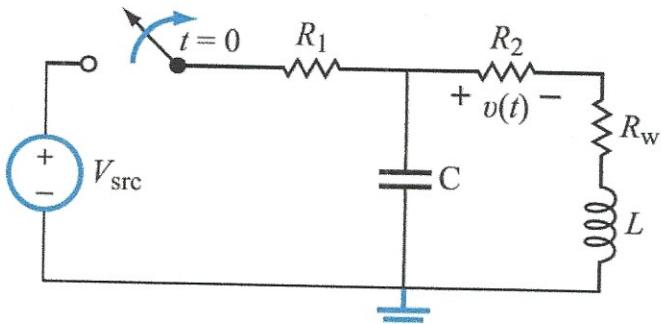[9] (10 points) Find $v_C(t)$ for $t > 0$ in the circuit below. Choose the time-domain solution method using the table attached. Use $V_{src} = 6 V$, $R_{1,2,w} = 400, 100, 100 \Omega$, $C = 1 \mu F$, $L = 10 mH$.




At $t=0^-$,

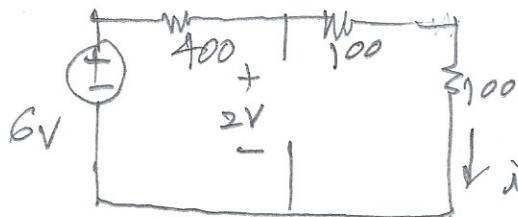

$$i_L(0^-) = \frac{6}{400+100+100} = \frac{6}{600} = 10 \text{ mA}$$

$$v_C(0^-) = 10 \text{ mA} \times 200 \Omega = 2 \text{ V}$$

At $t > 0$

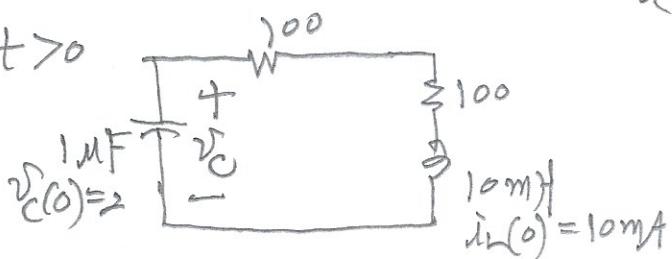

$$v_C = i_L(100+100) + 10 \times 10^3 \frac{d}{dt} i_L \quad (1) \quad \text{where } i_L = -\dot{v}_C$$

$$\dot{i}_L = -C \frac{d^2 v_C}{dt^2} = -10^{-6} \frac{d^2 v_C}{dt^2} \quad (2)$$

$$(2) \Rightarrow (1) \Rightarrow v_C = 200 \left(-10^{-6} \frac{d^2 v_C}{dt^2} \right) + 10^2 \frac{d}{dt} \left(-10^{-6} \frac{d^2 v_C}{dt^2} \right)$$

$$\times (-10^8) \Rightarrow -10^8 v_C = 2 \times 10^4 \frac{d v_C}{dt} + \frac{d^2 v_C}{dt^2}$$

$$\frac{d^2 v_C}{dt^2} + 2 \times 10^4 \frac{d v_C}{dt} + 10^8 v_C = 0$$

$$\omega = 10^4, \quad \omega_0 = \sqrt{10^8} = 10^4, \quad v_C(\infty) = 0$$

$\omega = \omega_0$, critically damped.

([9] solution continued)

$$v_c(t) = (B_1 + B_2 t) e^{-\alpha t} + v_c''^0$$

$$B_1 = v_c(0) - v_c''^0 = 2$$

$$B_2 = \frac{1}{10^6} \dot{v}_c(0) + \alpha [v_c(0) - v_c''^0]$$


$$= \frac{1}{10^6} [-\lambda_L(0) + \alpha v_c(0)] = \frac{1}{10^6} [-10 \times 10^{-3} + 10^4 \times 2] = 2 \times 10^{10}$$

$$\underline{v_c(t) = (2 + 2 \times 10^{10} t) e^{-10^4 t}}$$

(ans)

Series RLC	Parallel RLC
<p>Input: dc circuit with switch action @ $t = 0$</p>	<p>Input: dc circuit with switch action @ $t = 0$</p>
Total Response	Total Response
<p>Overdamped ($\alpha > \omega_0$)</p> $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \left[\frac{\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1} \right]$	<p>Overdamped ($\alpha > \omega_0$)</p> $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \left[\frac{\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1} \right]$
<p>Critically Damped ($\alpha = \omega_0$)</p> $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	<p>Critically Damped ($\alpha = \omega_0$)</p> $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
<p>Underdamped ($\alpha < \omega_0$)</p> $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	<p>Underdamped ($\alpha < \omega_0$)</p> $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations	
$\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$	$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

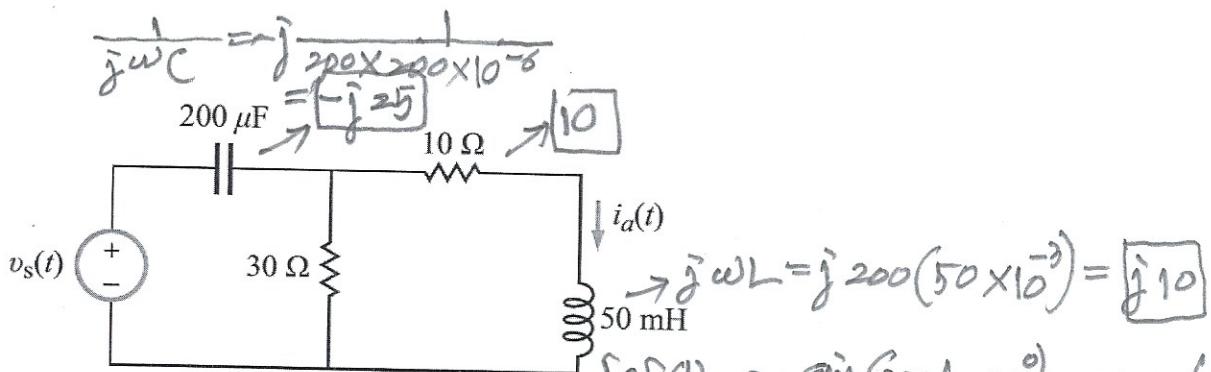[10] (10 points) Find $i_a(t)$ for $v_s(t) = 20 \sin(200t - 20^\circ)$ by using the phasor analysis method. Initial conditions are assumed to be zero.



Hint:


Step 1: Express v_s by using the phasor notation.

Step 2: Find the current (in phasor form) flowing out of the voltage source.

Step 3: Apply the current division law to find i_a in phasor form. (see below)

Step 4: Convert i_a in phasor form into its time-domain expression.

$$= 0.674 \cos(200t - 58.15^\circ)$$

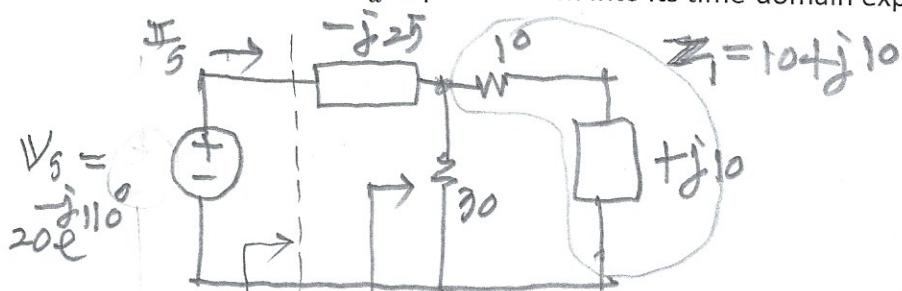

$$Z_5 | Z_{eq} = 30 || Z_1 = \frac{30(10 + j10)}{30 + (10 + j10)} = \frac{30(10 + j10)}{40 + j10} = \frac{30(1 + j1)}{4 + j1}$$

$$Z_5 = -j25 + Z_{eq} = -j25 + \frac{30(1 + j1)}{4 + j1}$$

$$= \frac{-j25(4 + j1) + 30 + j30}{4 + j1} = \frac{55 - j70}{4 + j1}$$

$$I_5 = \frac{V_s}{Z_5} = \frac{20 e^{-j110}}{55 - j70}$$

$$I_a = I_5 - \frac{30}{Z_1 + 30} = \frac{20 e^{-j110}(4 + j1)}{55 - j70} - \frac{30}{(10 + j10) + 30}$$


$$= \frac{20 e^{-j110}}{5(11 - j14)} \times 3 = 12 \frac{e^{-j110}}{\sqrt{11^2 + (-14)^2}} e^{j8.729 + (-11)}$$

$$= \frac{12}{17.80} e^{-j110 - (-j51.85)} = 0.674 e^{-j58.15^\circ}$$

$$\Rightarrow i_a(t) = 0.674 \cos(200t - 58.15^\circ)$$


Bonus Q1 (5 points) Find $v_{out}(t)$ for $v_c(0) = 0$ using Laplace transform method.

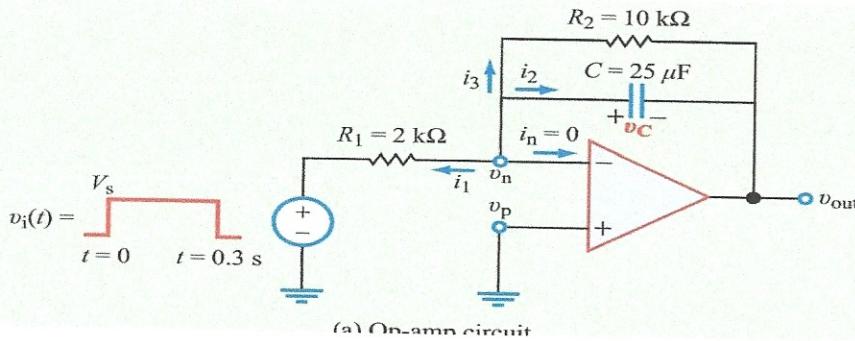Hint: Laplace transform $u(t) = 1/S$ and that of $e^{-at} = 1/(S+a)$.



$$v_i(t) = V_s (u(t) - u(t-0.3))$$
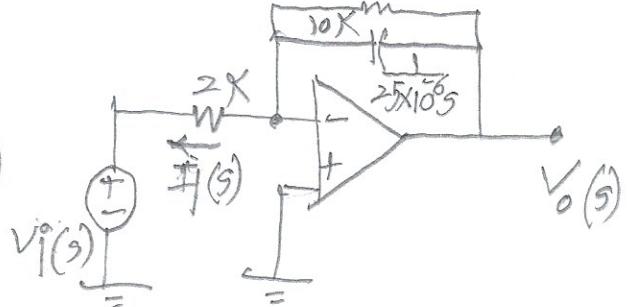
$$V_i(s) = V_s \left(\frac{1}{s} - \frac{1}{s} e^{-0.3s} \right)$$



$$I_1(s) = \frac{0 - V_i(s)}{2K}$$

$$I_2(s) = \frac{0 - V_o(s)}{25 \times 10^6 s} = -25 \times 10^{-6} s V_o(s)$$

$$I_3(s) = \frac{0 - V_o(s)}{10K}$$

$$\text{KCL} \Rightarrow I_1(s) + I_2(s) + I_3(s) = 0$$

$$-\frac{V_i(s)}{2K} - 25 \times 10^{-6} s V_o(s) - \frac{V_o(s)}{10K} = 0$$

$$V_o(s) \left[25 \times 10^{-6} s + \frac{1}{10K} \right] = -\frac{V_i(s)}{2K}$$

$$\times 10K \Rightarrow V_o(s) \left[25 \times 10^{-3} s + 1 \right] = -5 V_i(s)$$

$$V_o(s) = -\frac{5 V_i(s)}{25 \times 10^{-3} s + 1} = -\frac{200 V_i(s)}{s + 40} = -\frac{200 \left(\frac{1}{s} - \frac{1}{s} e^{-0.3s} \right)}{s + 40}$$

$$= -200 \left[\frac{1}{s(s+40)} - \frac{1}{s(s+40)} e^{-0.3s} \right] = -200 \left[\frac{\frac{1}{40}}{s} + \frac{-\frac{1}{40}}{s+40} \right]$$

$$V_o(t) = -5 \left(1 - e^{-40t} \right) u(t) + 5 \left(1 - e^{-40(t-0.3)} \right) u(t-0.3)$$

Personalized

Bonus Q2 (5 points): List 5 most significant concepts you have learned in EE101 this quarter.

Concept 1:

Concept 2:

Concept 3:

Concept 4:

Concept 5: