

Solution

EE101 Midterm Examination, February 7, 2019

Name _____ Student ID _____

1 page of formulas and tables only is allowed. But, you must show all your work even when you apply formulas to get full credits. Otherwise, you will lose points.

Problem 1 [20] _____

Problem 2 [20] _____


Problem 3 [25] _____

Problem 4 [15] _____

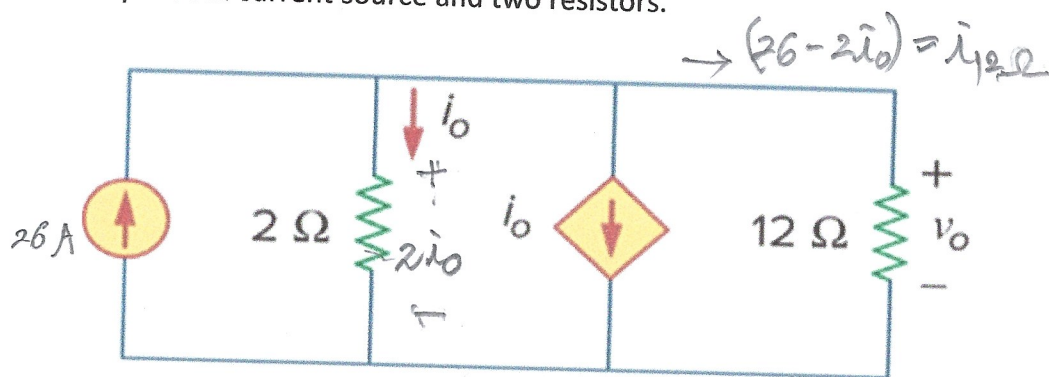Problem 5 [20] _____

TOTAL [100] _____

[1] (20 points) Consider the following circuit with one independent 26 [A]- current source, one dependent current source and two resistors.



Step 1 (10 points) Express v_0 in terms of i_0 and solve for i_0 for the given current source amount.

$$v_0 = 12 \times i_{12\Omega} = 12(26 - 2i_0) = 24i_0$$

$$12 \times 26 = (24 + 24)i_0 = 48i_0, \quad i_0 = \frac{12 \times 26}{48}$$

$$\Rightarrow \underline{i_0 = 12 \text{ [A]}}$$


Step 2 (10 points) Calculate the power delivered to or generated by the current-controlled current source. Is it generating or consuming power?

voltage across the dependent source $= v_0 = 2 \times 12 = 24 \text{ V}$

$$\text{Power} = 12 \text{ [A]} \times 24 \text{ [V]} = \underline{\underline{288 \text{ [W]}}}$$


consumed

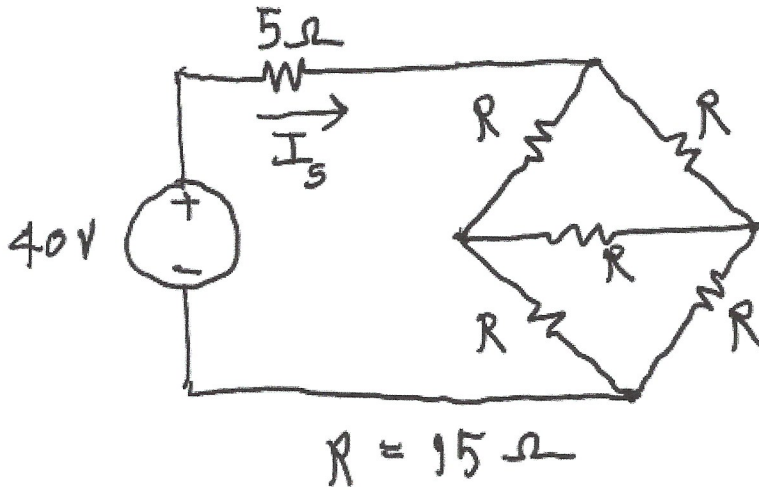[2] (20 points) Find the current I_5 from the 40V voltage source as shown in the figure.





Hint: One Delta-Wye transformation of (15Ω, 15Ω, 15Ω) resistors would simplify the problem.

Δ -Y transformation

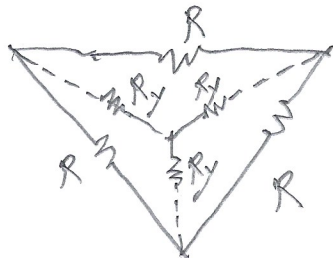

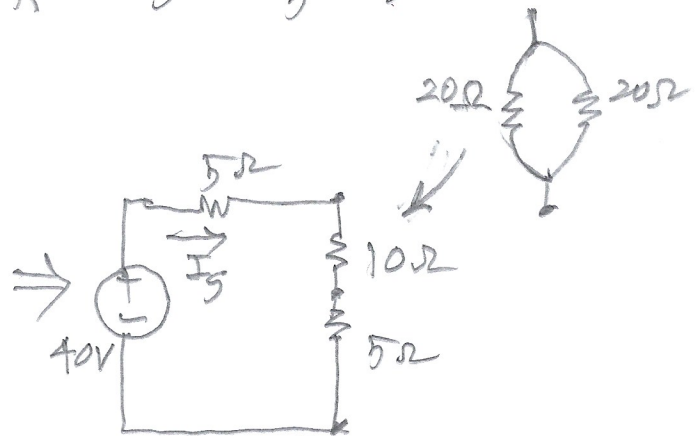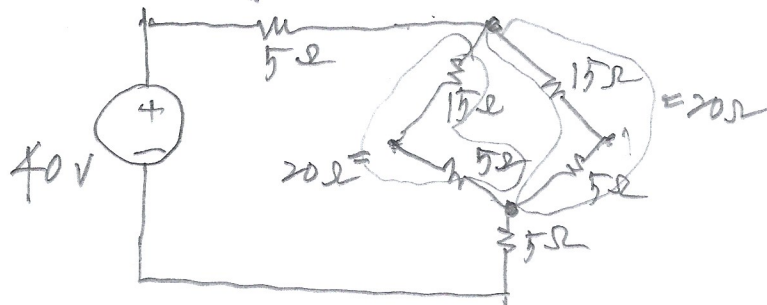
$$R_y = \frac{R \times R}{R + R + R} = \frac{R}{3} = \frac{15}{3} = 5\ \Omega$$



$$I_5 = \frac{40\ [V]}{(5 + 10 + 5)\ [\Omega]} = 2\ [A]$$

and

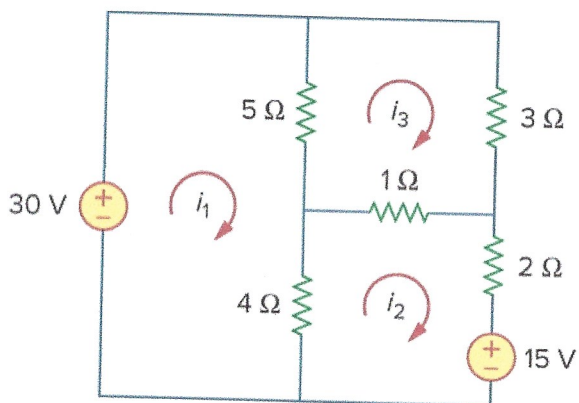[3] (25 points) Find the mesh currents i_1 , i_2 and i_3 .



(a) (15 points) Write down a matrix equation to find mesh currents as $Ax=b$, where A is a 3×3 matrix, x is a 3×1 matrix, and b is a source vector.

By inspection,

$$\begin{bmatrix} 9 & -4 & -5 \\ -4 & 7 & -1 \\ -5 & -1 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30 \\ -15 \\ 0 \end{bmatrix}$$

Alternatively, KVL in each mesh
 mesh 1
 $-30 + 5(i_1 - i_3) + 4(i_1 - i_2) = 0$
 mesh 2
 $+4(i_2 - i_1) + 1(i_2 - i_3) + 2i_2 + 15 = 0$
 mesh 3
 $+3i_3 + 1(i_3 - i_2) + 5(i_3 - i_1) = 0$

(b) (10 points) Then find the mesh currents.

$$\text{row 1} - \text{row 2} \times 5 \Rightarrow \begin{array}{ccc|c} 9 & -4 & -5 & 30 \\ -20 & 35 & -5 & -75 \\ \hline 29 & -39 & 0 & 105 \end{array} \quad \text{--- (1)}$$

$$\text{row 2} \times 9 + \text{row 3} \Rightarrow \begin{array}{ccc|c} -36 & 63 & -9 & -135 \\ -5 & -1 & 9 & 0 \\ \hline -41 & 62 & 0 & -135 \end{array} \quad \text{--- (2)}$$

$$(1) \times 41 + (2) \times 29 \Rightarrow$$

$$\begin{array}{ccc|c} 29 \times 41 & -39 \times 41 & 105 \times 41 & \\ +) & -41 \times 29 & 62 \times 29 & -135 \times 29 \\ \hline 0 & (-39 \times 41 + 62 \times 29) & 105 \times 41 - 135 \times 29 & \end{array}$$

$$0 \quad (-39 \times 41 + 62 \times 29) i_2 = 105 \times 41 - 135 \times 29$$

$$i_2 = \frac{105 \times 41 - 135 \times 29}{62 \times 29 - 39 \times 41} = \frac{390}{199} = 1.96 \text{ A} \quad (3)$$


$$(3) \rightarrow (1) \quad 29 i_1 = 39 \left(\frac{390}{199} \right) + 105$$

$$i_1 = \frac{39 \left(\frac{390}{199} \right) + 105}{29} = 6.26 \text{ A} \quad (4)$$

$$(3), (4) \rightarrow \text{3rd row} \quad i_3 = \frac{1}{9} (5 i_1 + i_2) = \frac{1}{9} (5 \times 6.26 + 1.96) = 3.69 \text{ A}$$

(continued)

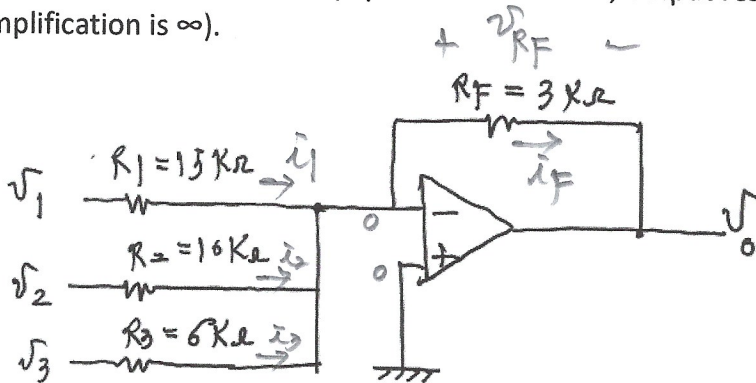[4]. (15 points) The OP amp circuit below calculates a weighted sum of input voltages V_1 , V_2 , and V_3 . Express the output voltage V_o as a function of three input voltages. In this calculation OP amp is assumed to be ideal (input resistance is ∞ , output resistance is zero and voltage amplification is ∞).



$$i_1 = \frac{V_1}{15\text{K}}, \quad i_2 = \frac{V_2}{10\text{K}}, \quad i_3 = \frac{V_3}{6\text{K}}$$

$$i_F = i_1 + i_2 + i_3$$



$$V_{RF} = R_F i_F$$

$$V_o = -V_{RF} = -3\text{K} \left[\frac{V_1}{15\text{K}} + \frac{V_2}{10\text{K}} + \frac{V_3}{6\text{K}} \right]$$

$$= \underline{\underline{-(0.2V_1 + 0.3V_2 + 0.5V_3)}}$$

(ans)

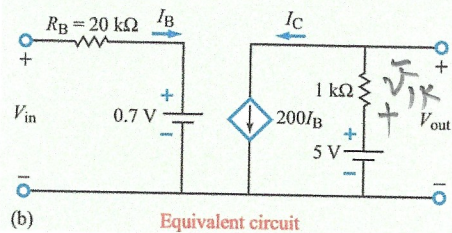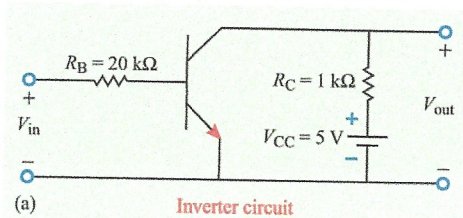[5]. (20 points) A bipolar junction transistor circuit (Figure (a)) and its equivalent circuit (Figure (b)) is shown below. For $V_{in} = 2.7$ [V], find the corresponding output voltage V_{out} .



$$I_B = \frac{2.7 - 0.7}{20k} = \frac{1}{10k} \text{ [A]} = 0.1 \text{ mA}$$

$$I_C = 200 I_B = 200 (0.1 \text{ mA}) = 20 \text{ mA}$$

$$V_{out} = 5 \text{ V} - 20 \text{ mA} (1 \text{ k}\Omega) = \underline{\underline{-15 \text{ V}}}$$

(me)