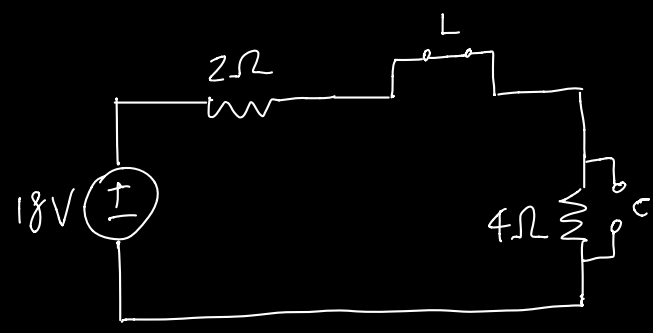


6.2


$t = 0^-$




$$i_L(0^-) = \frac{18}{2+4} = 3 \text{ A}$$

$$V_C(0^-) = 18 \times \frac{4}{2+4} = 12 \text{ (v)}$$

$t = 0$

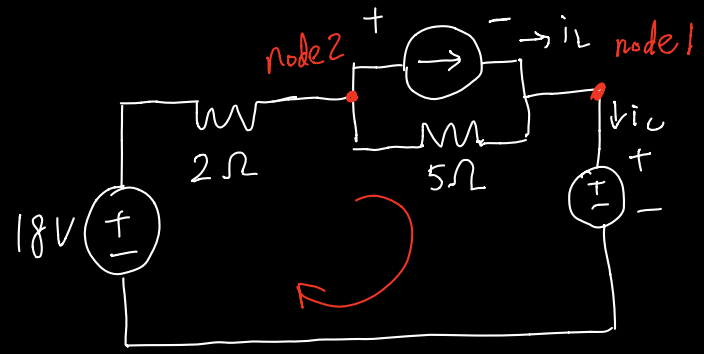

$t = \infty$

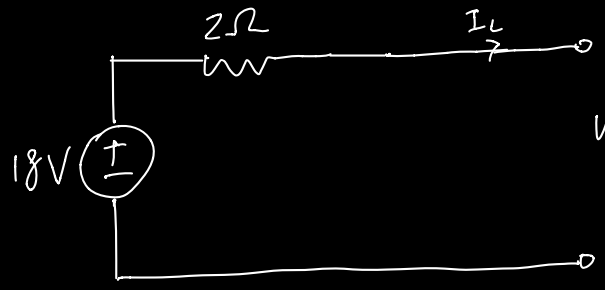

$$i_L(\infty) = 0 \text{ A}$$

$$V_C(\infty) = 18 \text{ V}$$

$$V_C(0) = V_C(0^-) = 12 \text{ (v)}$$

$$i_L(0) = i_L(0^-) = \frac{18}{2+4} = 3 \text{ A}$$

According to KCL at node 1:  $i_L(0) + i_{5\Omega}(0) = i_C(0)$

where  $i_{5\Omega}(0) = \frac{V_L(0)}{5\Omega}$

According to KCL at node 2:  $\frac{V_{2\Omega}}{2} = i_L(0) + i_{5\Omega}(0)$

According to KVL:  $-18 + V_{2\Omega} + V_L(0) + V_C(0) = 0$

Using these 3 equations:


$$\begin{cases} 3 + \frac{V_L(0)}{5} = i_c(0) \\ \frac{V_{2\Omega}}{2} = 3 + \frac{V_L(0)}{5} \\ -18 + V_{2\Omega} + V_L(0) + 12 = 0 \end{cases} \Rightarrow$$

$$\begin{cases} V_L(0) = 0 \\ i_c(0) = 3 \end{cases}$$

$$\begin{cases} V_c(\infty) = 12 \text{ (V)} \\ i_L(\infty) = 0 \text{ (A)} \end{cases}$$

6.3


$t=0^-$

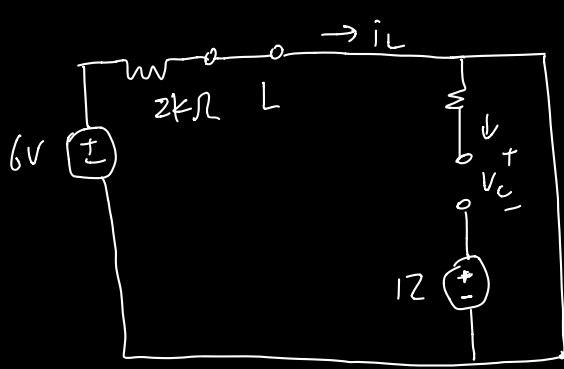


$$V_C(0^-) = -12 \text{ V}$$

$$i_L(0^-) = \frac{6}{2k} = 3 \text{ mA}$$

$t=0$

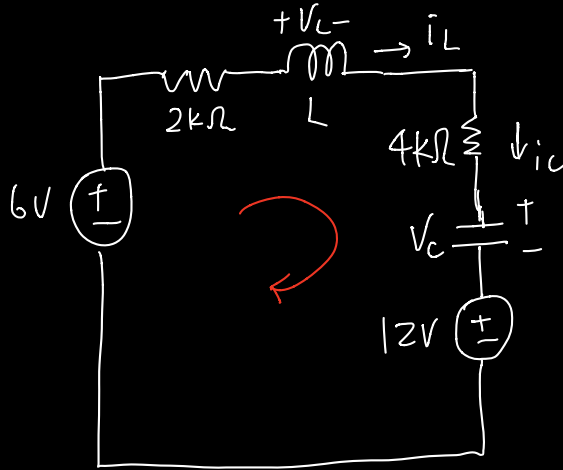

$t=\infty$

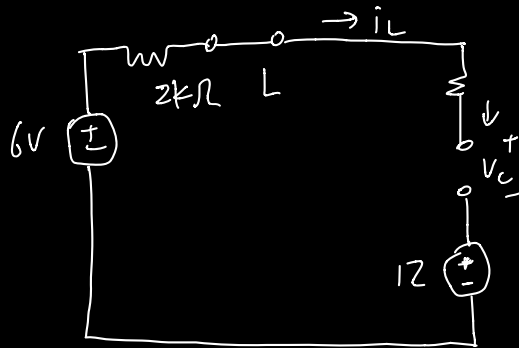

$$V_C(0) = V_C(0^-) = -12 \text{ V}$$

$$i_L(0) = i_L(0^-) = 3 \text{ mA}$$

$$\text{KVL: } -6 + 2k \times 3m + V_L(0) + 4k \cdot 3m - 12 + 12 = 0$$


$$\Rightarrow V_L(0) = -12 \text{ V}$$

$$i_C(0) = i_L(0) = 3 \text{ mA}$$

$$V_C(\infty) = -6 \text{ V}$$

$$i_L(\infty) = 0 \text{ A}$$

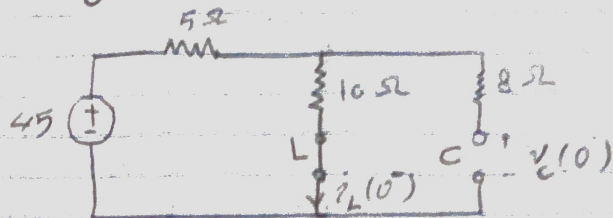6.4) At time  $t = 0^-$ , the capacitor acts as open circuit and the inductor as short circuit, because both are fully charged, thus at  $t = 0^-$




6.4.a)

$$v_C(0) = v_C(0^-) = 45 \times \frac{10}{5+10} = 30 \text{ (V)}$$

$$i_L(0) = i_L(0^-) = \frac{45}{5+10} = 3 \text{ (A)}$$

6.4.b) At time  $t = 0$  as we disconnect the power supply, the inductor acts as current power source and the capacitor acts as voltage power source:

at  $t = 0$ :

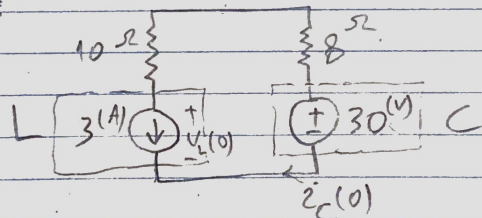


$$i_C(0) = -i_L(0) = -3 \text{ (A)}$$

$$\text{KVL: } -v_L(0) - 3 \times 10 - 3 \times 8 + 30 = 0$$

$$\Rightarrow v_L(0) = -24 \text{ (V)}$$

6.45) At time  $t = \infty$  both inductor and the capacitor are fully discharged. As, we do not have any power source thus,




at  $t = \infty$

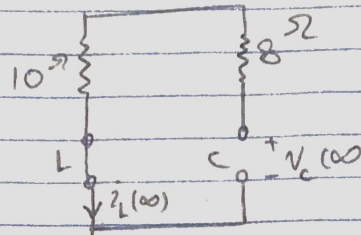

$$V_C(\infty) = 0$$

$$i_L(\infty) = 0$$

6.5

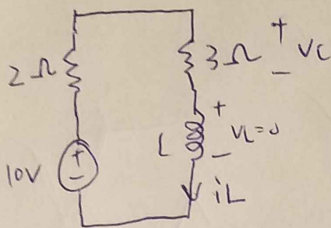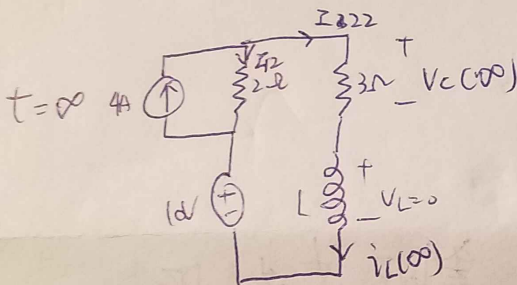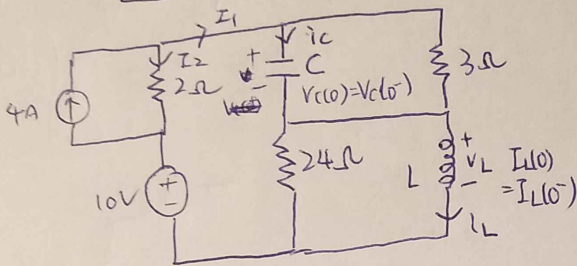 $t=0^-$  $t=0$ 

$$(a) V_C(0) = V_C(0^-) = 10V \times \frac{3\Omega}{3\Omega + 2\Omega} = 6V$$

$$i_L(0) = i_L(0^-) = \frac{10V}{3\Omega + 2\Omega} = 2A$$

$$(b) \begin{cases} 4A = I_1 + I_2 \\ I_2 \cdot 2\Omega + 10V = V_C(0) + [I_1 - i_L(0)] \cdot 24\Omega \end{cases} \Rightarrow \begin{cases} I_1 = \frac{30}{13} A \\ I_2 = \frac{22}{13} A \end{cases}$$

$$i_C(0) = I_1 - \frac{V_C(0)}{3\Omega} = \frac{4}{13} A \quad V_L(0) = [I_1 - i_L(0)] \times 24\Omega = \frac{96}{13} V$$

$$(c) \begin{cases} 4A = I_{12} + I_{22} \\ I_{12} \times 2\Omega + 10V = I_{22} \times 3\Omega \end{cases} \Rightarrow \begin{cases} I_{12} = \frac{2}{5} A \\ I_{22} = \frac{18}{5} A \end{cases}$$

$$V_C(\infty) = I_{22} \times 3\Omega = \frac{54}{5} V$$

$$i_L(\infty) = I_{22} = \frac{18}{5} A$$