
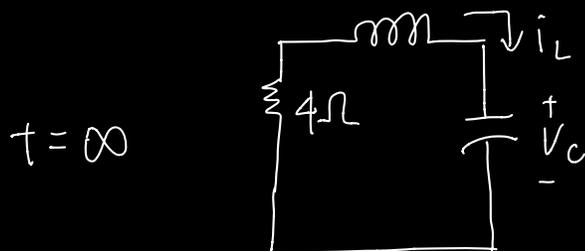
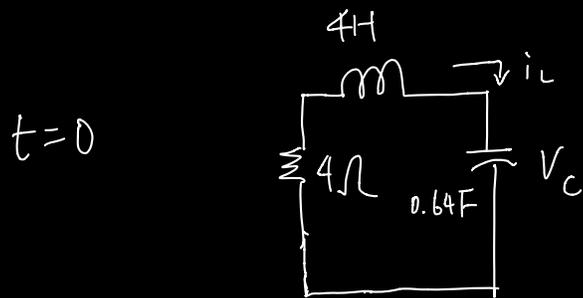


6.18)

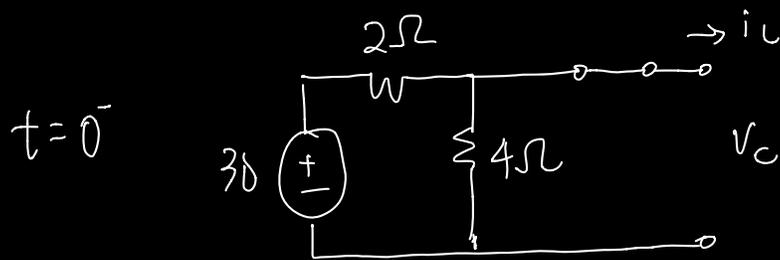

At the beginning of the stage, the circuit is at steady state, and the inductor behaves like a short circuit, the capacitor behaves like an open circuit. As a result,

$$i_L(0^-) = 0 \text{ A}$$

$$V_C(0^-) = 30 \times \frac{4}{2+4} = 20 \text{ V}$$

At the time $t=0$, the switch changes from close to open, and the current across inductor and

Voltage across capacitor remains the same because they cannot change instantaneously.

$$i_L(0) = i_L(0^-) = i_C(0) = 0 \text{ A}$$

$$V_C(0) = V_C(0^-) = 20 \text{ V}$$

Notice this is a series RLC circuit and the capacitor will discharge all the way to 0 V.

$$V_C(\infty) = 0$$

With this in mind, the damping coefficient and resonant frequency is

$$\alpha = \frac{R}{2L} = \frac{4}{2.4} = 0.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times 0.64}} = 0.625$$

Since $\alpha < \omega$, it is underdamped.

$$\begin{cases} i_C(t) = C \frac{dV_C(t)}{dt} \\ V_C = e^{-\alpha t} [D_1 \cos \omega_d t + D_2 \sin \omega_d t] + V_C(\infty) \end{cases}$$

where $\omega_d^2 = \omega_0^2 - \alpha^2 = 0.140625 \Rightarrow \omega_d = 0.375 = \frac{3}{8}$

$$D_1 = V_C(0) - V_C(\infty) = 20 - 0 = 20 \text{ V}$$

$$D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [V_C(0) - V_C(\infty)]}{\omega_d}$$

$$= \frac{\frac{1}{0.64} \times 0 + 0.5 [20 - 0]}{\frac{3}{8}}$$

$$= \frac{80}{3}$$

$$\therefore V_c = e^{-0.5t} \left[20 \cos \frac{3}{8}t + \frac{80}{3} \sin \frac{3}{8}t \right]$$


$$\begin{aligned} \dot{V}_c &= -0.5 e^{-0.5t} \cdot 20 \cos \frac{3}{8}t - e^{-0.5t} \cdot 20 \cdot \frac{3}{8} \cdot \sin \frac{3}{8}t \\ &\quad - 0.5 e^{-0.5t} \cdot \frac{80}{3} \cdot \sin \frac{3}{8}t + e^{-0.5t} \cdot \frac{80}{3} \cdot \frac{3}{8} \cdot \cos \frac{3}{8}t \\ &= -\frac{500}{24} e^{-0.5t} \sin \frac{3}{8}t \end{aligned}$$

$$i_c = C \dot{V}_c$$


$$= 0.64 \left(-\frac{500}{24} e^{-0.5t} \sin \frac{3}{8}t \right)$$

$$= -\frac{40}{3} e^{-0.5t} \sin \left(\frac{3}{8}t \right)$$

6.22)

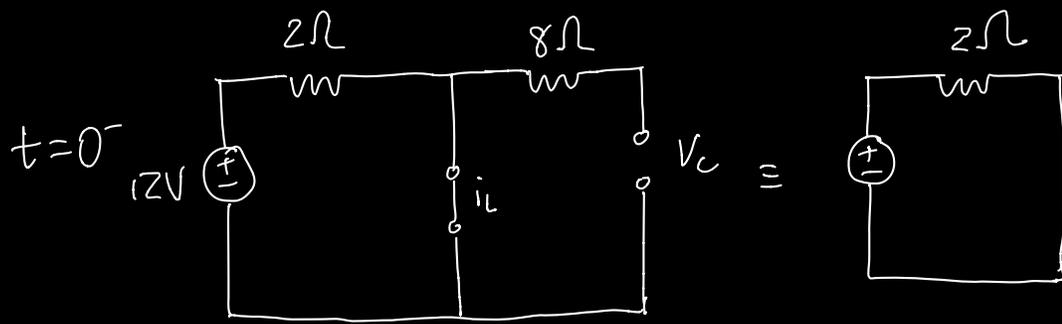

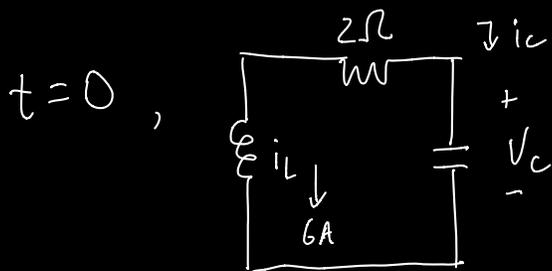
$$i_L(0^-) = \frac{12V}{2} = 6A, \quad V_c(0^-) = 0$$



$$V_c(0) = V_c(0^-) = 0$$

$$i_L(0) = i_L(0^-) = i_c(0) = 6A$$

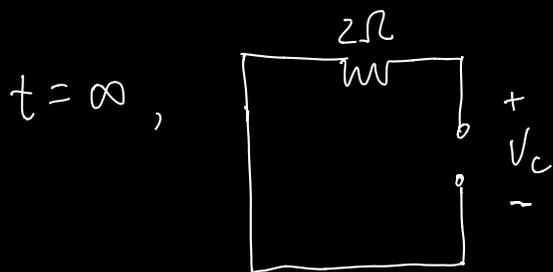

$$V_c(\infty) = 0V$$

$$i_c(\infty) = 0A$$

Remember that inductor and capacitor **store** energy, at $t=0$, the energy is stored in the inductor and the capacitor is fully discharged. At $t=\infty$, inductor fully discharged and capacitor was charged at beginning and discharged in the end because all energy is dissipated by the resistor.

Let's calculate α (damping coefficient) and ω (resonant frequency) first to find out what type of damping is this RLC circuit.

$$\alpha = \frac{R}{2L} = \frac{8}{2 \cdot 2} = 2, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \cdot 0.1}} = 2.23$$

Since $\alpha < \omega$, the circuit is underdamped. We

apply rule according to Table 6.1 (like what we did in problem 6.18)

$$\omega_d = \sqrt{\omega_o^2 - d^2} = 1$$

$$D_1 = V_c(0) - V_c(\infty) = 0 + 12 = 12 \text{ V}$$

$$D_2 = \frac{\frac{1}{C} i_c(0) + d [V_c(0) - V_c(\infty)]}{\omega_d}$$

$$= \frac{-\frac{1}{0.1} \cdot 6 + 2 \cdot (0)}{1}$$

$$= -60$$

$$\therefore V_c(t) = e^{-dt} [D_1 \cos \omega_d t + D_2 \sin \omega_d t] + V_c(\infty)$$

$$= e^{-2t} \cdot (-60) \cdot \sin t = -60 e^{-2t} \sin(t)$$


$$\dot{V}_c(t) = -2e^{-2t} (-60) \sin t + e^{-2t} \cdot (-60) \cdot \cos t$$

$$i_c(t) = C \dot{V}_c(t) = 0.1 (120 e^{-2t} \sin t - 60 e^{-2t} \cos t)$$

$$= 12 e^{-2t} \sin t - 6 e^{-2t} \cos t$$

$$= (12 \sin t - 6 \cos t) e^{-2t}$$
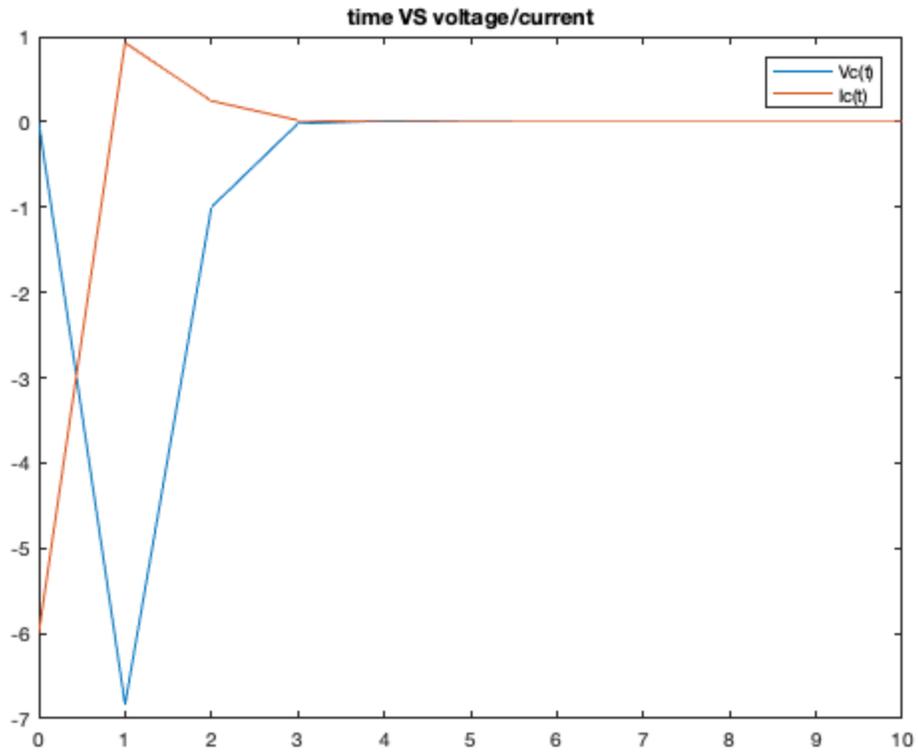
```
close all; clear all;
t = 0:10;
vc = -60*exp(-2*t).*sin(t);
ic = (12*sin(t) - 6*cos(t)).*exp(-2*t); figure;
plot(t, vc); hold on;
plot(t,ic);
legend('Vc(t)', 'Ic(t)');
title('time VS voltage/current');
```



Published with MATLAB® R2016b

$$6.12 \quad t=0^- \quad V_C(t=0^-) = V_0 \cdot \frac{R_2}{R_1+R_2} = 9 \text{ V}$$


$$I_L(t=0^-) = 0$$

$$t=0^+ \quad V_C(t=0^+) = V_C(t=0^-) = 9 \text{ V}$$

$$I_C(t=0^+) = I_L(t=0^+) = I_L(t=0^-) = 0$$

$$t = \infty \quad V_C(t=\infty) = 0$$

$$I_C(t=\infty) = 0$$

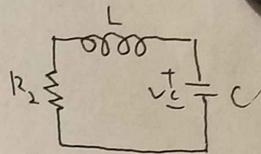

$$\text{When } t > 0 \quad \begin{cases} R_2 I_C + L \frac{dI_C}{dt} + V_C = 0 \\ I_C = C \frac{dV_C}{dt} \end{cases} \Rightarrow R_2 C \frac{dV_C}{dt} + LC \frac{d^2 V_C}{dt^2} + V_C = 0 \quad (1)$$

$$\text{Assume } V_C(t) = A e^{st}, \quad (1) \rightarrow (2): R_2 C A s e^{st} + LC A s^2 e^{st} + A e^{st} = 0$$

$$\Rightarrow V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = \frac{-R_2 C + \sqrt{(R_2 C)^2 - 4 \times LC}}{2 \times LC} = -6 + \sqrt{11} \approx -2.68$$

$$s_2 = \frac{-R_2 C - \sqrt{(R_2 C)^2 - 4 \times LC}}{2 \times LC} = -6 - \sqrt{11} \approx -9.32$$

$$\text{When } t=0^+ \quad V_C(0^+) = A_1 + A_2 = 9$$

$$\begin{cases} I_C(0^+) = C \frac{dV_C}{dt} \Big|_{t=0^+} = C C s_1 A_1 + s_2 A_2 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} A_1 = \frac{99 + 54\sqrt{11}}{22} \approx 12.64 \\ A_2 = \frac{-99 + 54\sqrt{11}}{22} \approx -3.64 \end{cases}$$

$$\therefore V_C(t) \approx 12.64 e^{-2.68t} - 3.64 e^{-9.32t}$$

6.16

 $t = 0^-$
 before
 switch at 1

$$V_C(0^-) = V_0$$

$$I_L(0^-) = 0$$

 $t = 0^+$
 Switch at 2

$$V_C(0^+) = V_C(0^-) = V_0$$

$$I_L(0^+) = I_L(0^-) = 0$$

$$I_C(0^+) = I_L(0^+)$$

$$\begin{cases} L \frac{dI_C}{dt} + V_C = 0 \\ I_C = C \frac{dV_C}{dt} \end{cases}$$

$$\Rightarrow LC \frac{d^2 V_C}{dt^2} + V_C = 0$$

$$\Rightarrow V_C(t) = A \cos(\omega t) + B \sin(\omega t), \quad \omega = \frac{1}{\sqrt{LC}}$$

$$t = 0^+, V_C(0^+) = A = V_0 \quad \Rightarrow A = V_0$$

$$I_C(0^+) = C \left. \frac{dV_C}{dt} \right|_{t=0^+} = B\omega = 0 \quad \Rightarrow B = 0$$

$$\therefore V_C(t) = V_0 \cos(\omega t), \quad \omega = \frac{1}{\sqrt{LC}}$$