

6.29) At  $t=0^-$ :  $i_L(0^-) = \frac{18-12}{6+6} = 0.5 \text{ A}$

$$V_c(0^-) = 6 \times 0.5 + 12 = 15 \text{ V}$$

At  $t=0$ :  $V_c(0) = V_c(0^-) = 15$

$$i_c(0) = -i_L(0) = -i_L(0^-) = -0.5 \text{ A}$$

$$\dot{V}_c(0) = \frac{i_c(0)}{C} = -\frac{0.5}{C}$$

At  $t > 0$ :

$$\alpha = \frac{R}{2L} = \frac{6+6}{2 \times 0.1} = 60 \text{ Np/s}$$

In order to have a critically damped circuit response

$$\alpha = \omega = \frac{1}{\sqrt{LC}} = 60$$

$$\Rightarrow C = \frac{1}{360} \text{ F}$$

$\therefore \dot{V}_c(0) = -\frac{0.5}{C} = -0.5 \times 360 = -180 \text{ V/s}$

$\therefore V_c(t) = V_c(\infty) + (B_1 + B_2 t) e^{-\alpha t}$   
 $= 12 + (B_1 + B_2 t) e^{-60t}$

where  $B_1 = V_c(0) - V_c(\infty) = 15 - 12 = 3 \text{ V}$

$$B_2 = \dot{V}_c(0) + \alpha [V_c(0) - V_c(\infty)]$$
$$= -180 + 60 [15 - 12]$$
$$= 0$$

$\therefore V_c(t) = 12 + 3e^{-60t}$ , for  $t \geq 0$

$$\underline{6.35}) \quad \text{At } t=0^-: \quad V_C(0^-) = 8 \\ i_L(0^-) = 0$$

$$\text{At } t \geq 0: \quad V(\infty) = \frac{4}{3} V \\ i_C(0) = i_L(0) = i_L(0^-) = 0$$

$$\alpha = \frac{R}{2L} = \frac{2/3}{2 \times 0.5 \times 10^{-3}} = 666.7 \text{ Np/s}$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 10^{-3} \times 2 \times 10^{-3}}} = 1000 \text{ rad/s}$$

Since  $\alpha < \omega_0$ , the response is underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 745.4 \text{ rad/s}$$

$$D_1 = V_C(0) - V_C(\infty) = 8 - \frac{4}{3} = \frac{20}{3}$$

$$D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [V_C(0) - V_C(\infty)]}{\omega_d} = 5.96$$

$$V_C(t) = V_C(\infty) + [D_1 \cos(\omega_d t) + D_2 \sin(\omega_d t)] e^{-\alpha t}$$

$$= \frac{4}{3} + \left[ \frac{20}{3} \cos(745.4t) + 5.96 \sin(745.4t) \right] e^{-666.7t}, \\ \text{for } t \geq 0$$

$$638 \quad t=0^- \quad i_L(0^-) = 1.5 \text{ mA}$$

$$v_C(0^-) = 0$$

$$t=0^+ \quad i_L(0^+) = i_L(0^-) = 1.5 \text{ mA}$$

$$v_C(0^+) = v_C(0^-) = 0 = v_C(0^+) = L \frac{di_L}{dt} \Big|_{t=0^+}$$

$$\Rightarrow i_L'(0^+) = 0$$

$$t = \infty \quad i_L(\infty) = 1.5 \text{ mA}$$

$\Rightarrow$   $i_L$  keeps same value when  $t=0$  and  $t=\infty$ , and since  $i_L'(0^+) = 0$ ,  
 ~~$i_L$~~   $i_L$  doesn't change when  $t=0$ .

$$\Rightarrow i_L(t) = 1.5 \text{ mA}$$

$$6.50. \quad V'' + 5V' + 6V = 144$$

Solve this ODE  $\Rightarrow V(t) = c_1 e^{-3t} + c_2 e^{-2t} + c_3$ ,  $c_1, c_2, c_3$  are constants

$$\therefore V(0) = 16V \quad \therefore c_1 + c_2 + c_3 = 16 \quad (1)$$

$$\therefore V'(0) = 9.6V/s \quad \therefore V'(t)|_{t=0} = -3c_1 e^{-3t} - 2c_2 e^{-2t}|_{t=0} = -3c_1 - 2c_2 = 9.6 \quad (2)$$

$$\therefore V(0) = 16V, V'(0) = 9.6V/s \quad \therefore \cancel{V(0)} V''(0) + 5V'(0) + 6V(0) = 144$$

$$\Rightarrow V''(0) + 5 \times 9.6 + 6 \times 16 = 144$$

$$\Rightarrow \cancel{V''(0)} V''(0) = V''(t)|_{t=0} = 0$$


$$\Rightarrow 9c_1 e^{-3t} + 4c_2 e^{-2t}|_{t=0} = 0$$

$$\Rightarrow 9c_1 + 4c_2 = 0 \quad (3)$$

$$\therefore \begin{cases} c_1 + c_2 + c_3 = 16 & (1) \\ -3c_1 - 2c_2 = 9.6 & (2) \\ 9c_1 + 4c_2 = 0 & (3) \end{cases} \Rightarrow \begin{cases} c_1 = 64 \\ c_2 = -14.4 \\ c_3 = 24 \end{cases}$$

$$\therefore V(t) = (64e^{-3t} - 14.4e^{-2t} + 24) V$$


6.54 1)  $t=0^-$   
( $t < 0$ )

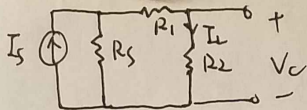

$$I_L(t=0^-) = I_s \cdot \frac{R_s}{R_s + R_1 + R_2} = 0 \text{ A}$$

$$V_c(t=0^-) = I_L(t=0^-) \cdot R_2 = 2 \text{ V}$$

2)  $t=0^+$

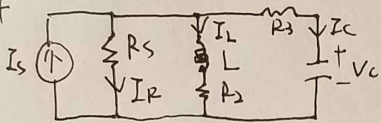

$$I_L(t=0^+) = I_L(t=0^-) = 0 \text{ A}$$

$$V_c(t=0^+) = V_c(t=0^-) = 2 \text{ V}$$


$$\text{KCL: } I_s = I_R(t=0^+) + I_C(t=0^+) + I_L(t=0^+)$$

$$\text{KVL: } I_C(t=0^+) \cdot R_3 + V_c(t=0^+) = I_R(t=0^+) \cdot R_3$$

$$\Rightarrow I_C(t=0^+) = C \frac{dV_c}{dt} \Big|_{t=0^+} = 0.02 \text{ A}$$

$$\frac{dV_c}{dt} \Big|_{t=0^+} = 4 \text{ V/s}$$


3)  $t=\infty$

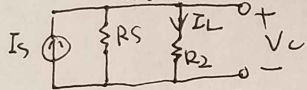

$$I_L(t=\infty) = I_s \cdot \frac{R_s}{R_s + R_2} = 0.12 \text{ A}$$

$$V_c(t=\infty) = I_L(t=\infty) \cdot R_2 = 2.4 \text{ V}$$

4)  $t > 0$

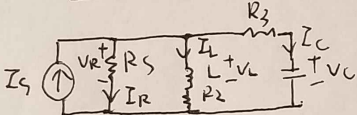

$$\text{KCL: } I_s = I_R + I_L + I_C \quad (1)$$

$$\text{Using } I_R = \frac{V_R}{R_s} = \frac{V_c + I_C R_3}{R_s} \quad (2) \text{ into } (1), \text{ leads to } I_s = I_L + C \frac{dV_c}{dt} + \frac{V_c + C \frac{dV_c}{dt} \cdot R_3}{R_s} \quad (4)$$

$$I_C = C \frac{dV_c}{dt} \quad (3)$$

$$\Rightarrow I_L = I_s - C \frac{dV_c}{dt} - \frac{V_c}{R_s} - C \frac{R_3}{R_s} \frac{dV_c}{dt} \quad (5)$$

$$\frac{dI_L}{dt} = -\frac{C(R_3 + R_s)}{R_s} \frac{d^2V_c}{dt^2} - \frac{1}{R_s} \frac{dV_c}{dt} \quad (6)$$

$$\text{KVL: } V_L + I_L \cdot R_2 = V_c + I_C R_3 \quad (7)$$

$$\text{Using } (3) \text{ and } V_L = L \frac{dI_L}{dt} \quad (8) \text{ into } (7), \text{ leads to } L \frac{dI_L}{dt} + I_L R_2 = V_c + R_3 C \frac{dV_c}{dt} \quad (9)$$

$$\text{Using } (5) \text{ and } (6) \text{ into } (9), \text{ leads } \frac{d^2V_c}{dt^2} + 12 \frac{dV_c}{dt} + 50 V_c = 120$$

and plugging ~~the~~ numbers into (9)

$$\alpha = \frac{12}{2} = 6, \quad \omega_0 = \sqrt{50} = 5\sqrt{2} \approx 7.07 \Rightarrow \alpha < \omega_0, \text{ under damped}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{14} \approx 3.74$$

$$D_1 = V_c(0) - V_c(\infty) = -0.4$$

$$D_2 = \frac{V_c'(0) + \alpha [V_c(0) - V_c(\infty)]}{\omega_d} = \frac{4 \cdot 6 \times 0.4}{\sqrt{14}} = \frac{9.6}{\sqrt{14}} \approx 2.54$$

$$\text{At } t > 0 \Rightarrow V_c(t) = V_c(\infty) + e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t)$$

$$= 2.4 + e^{-6t} \left( -0.4 \cos \sqrt{14} t + \frac{4\sqrt{14}}{35} \sin \sqrt{14} t \right) \text{ V}$$

$$\approx 0.428$$

$$\begin{aligned}
 7. | \quad V(t) &= -4 \sin(8\pi \times 10^3 t - 45^\circ) \text{ V} \\
 &= -4 \cos(8\pi \times 10^3 t - 45^\circ - 90^\circ) \text{ V} \\
 &= 4 \cos(8\pi \times 10^3 t - 45^\circ - 90^\circ + 180^\circ) \text{ V} \\
 &= 4 \cos(8\pi \times 10^3 t + 45^\circ) \text{ V} \\
 &= A \cos(2\pi f t + \phi) \text{ V}
 \end{aligned}$$

$$\therefore A = 4 \text{ V}$$

$$f = 4 \text{ KHz}$$

$$\phi = 45^\circ$$

$$T = \frac{1}{f} = 2.5 \times 10^{-4} \text{ s}$$

7.22

1).

$$V_1(t) = 4 \cos(377t - 30^\circ)$$

$$V_1 = 4 e^{-j30^\circ} \text{ V}$$

2).

$$V_2(t) = -2 \sin(8\pi \times 10^4 t + 18^\circ) \text{ V}$$

$$= 2 \cos(8\pi \times 10^4 t + 18^\circ + 90^\circ)$$

$$V_2 = 2 e^{j108^\circ} \text{ V}$$

3).

$$V_3(t) = 3 \sin(1000t + 53^\circ) - 4 \cos(1000t - 17^\circ)$$

$$= 3 \cos(1000t + 53^\circ - 90^\circ) + 4 \cos(1000t - 17^\circ + 180^\circ)$$

$$V_3 = 3 e^{-j37^\circ} + 4 e^{j163^\circ}$$

$$= 3 \cos 37^\circ - j 3 \sin 37^\circ + 4 \cos 163^\circ + j 4 \sin 163^\circ$$

$$= 2.4 - j 1.81 - 3.83 + j 1.17$$

$$= -1.43 - j 0.64$$

$$= 1.57 e^{-j155.9^\circ}$$

7.10) Not:  $z = a + jb \Rightarrow r = \sqrt{a^2 + b^2}$ ,  $\theta = \begin{cases} \tan^{-1} \frac{b}{a} & \text{for } a > 0 \\ \tan^{-1} \frac{b}{a} + 180^\circ & \text{for } a < 0 \end{cases}$

a)  $z_1 = 3 + j4 = 5 \angle 53.13^\circ$

$r = \sqrt{3^2 + 4^2} = 5$ ,  $\theta = \tan^{-1} \frac{4}{3} = 53.13^\circ$

$\Rightarrow$  polar form:  $z_1 = 5(\cos(53.13^\circ) + j \sin(53.13^\circ)) = 5 \angle 53.13^\circ$

b)  $z_2 = -6 + j8 = 10 \angle 126.87^\circ$

$r = \sqrt{(-6)^2 + 8^2} = 10$ ,  $\theta = \tan^{-1} \frac{8}{-6} + 180^\circ = 126.87^\circ$

polar form:  $z_2 = 10(\cos(126.87^\circ) + j \sin(126.87^\circ)) = 10 \angle 126.87^\circ$

c)  $z_3 = -6 - j4 = 7.21 \angle -146.31^\circ$  or  $7.21 \angle 213.69^\circ$

$r = \sqrt{(-6)^2 + (-4)^2} = 7.21$ ,  $\theta = \tan^{-1} \frac{-4}{-6} + 180^\circ = -146.31^\circ$

d)  $z_4 = j2 = 2 \angle 90^\circ$

$r = \sqrt{0^2 + 2^2} = 2$ ,  $\theta = \tan^{-1} \frac{2}{0} = \tan^{-1} \infty = 90^\circ$

e)  $z_5 = (2 + j)^2 = 4 + j2 + j^2 = 4 + j2 - 1 = 3 + j2$

$r = \sqrt{3^2 + 2^2} = 3.61$ ,  $\theta = \tan^{-1} \frac{2}{3} = 33.69^\circ$

$\Rightarrow z_5 = 3.61 \angle 33.69^\circ$



$$\begin{aligned}
 f) z_6 &= (3-j2)^3 = 27 - 3(9)(j2) + 3(3)(j2)^2 - (j2)^3 \\
 &= 27 - j54 - 36 + j8 \\
 &= -9 - j46
 \end{aligned}$$

$$r = \sqrt{(-9)^2 + (-46)^2} = 46.87 \quad \theta = \tan^{-1} \frac{-46}{-9} + 180^\circ = -101.07^\circ$$

$$\Rightarrow z_6 = 46.87 \angle -101.07^\circ$$

$$g) z_7 = (-1+j)^{1/2} \Rightarrow z_7^2 = (-1+j)$$

$$\text{for } z_7^2: r = \sqrt{(-1)^2 + 1^2} = 1.41, \quad \theta = \tan^{-1} \frac{1}{-1} + 180^\circ = 135^\circ$$

If we multiply two complex numbers in polar form

$$\text{we get: } z_1 z_2 = r_1 r_2 \angle (\theta_1 + \theta_2)$$

$$\text{thus, } z_7^2 = z_7 z_7 = \frac{r^2}{7} \angle 2\theta_7$$


therefore,

$$r_7^2 = 1.41 \Rightarrow r_7 = \sqrt{1.41} = 1.19$$

$$2\theta_7 = 135^\circ \Rightarrow \theta_7 = 67.5^\circ$$

$$\Rightarrow z_7 = (-1+j)^{1/2} = 1.19 \angle 67.5^\circ$$

7.36) Transferring to phasor domain:

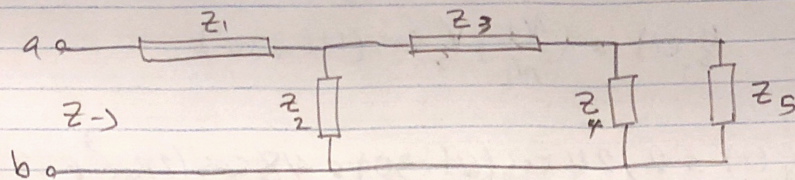

$$Z_1 = 5 \Omega, \quad Z_2 = \frac{1}{j\omega C} = \frac{j}{400 \times 2 \times 10^3} = -j1.25 \Omega$$

$$Z_3 = j\omega L = j400 \times 3 \times 10^3 = j1.2 \Omega$$

$$Z_4 = 5 \Omega, \quad Z_5 = j\omega L = j400 \times 9 \times 10^3 = j3.6 \Omega$$

$$Z_{45} = Z_4 \parallel Z_5 = \frac{j18}{5 + j3.6} = 2.92 e^{j54.24^\circ} \Omega$$

$$Z_{345} = Z_{45} + Z_3 = 2.92 e^{j54.24^\circ} + j1.2 = 1.71 + j3.57 \Omega$$

$$Z = Z_1 + Z_2 \parallel Z_{345} = 5 + (-j1.25) \parallel (1.71 + j3.57)$$

$$= 5 + \frac{(-j1.25)(1.71 + j3.57)}{1.71 + j2.32} = 5.32 - j1.69 \Omega$$

$$\Rightarrow Z = 5.32 - j1.69 \Omega$$

7.86) The voltage in secondary winding of the transformer

$$is: V_{s_1}(t) = \left(\frac{N_2}{N_1}\right) V_s \cos(\omega t + 30^\circ)$$

$$\Rightarrow V_{s_1}(t) = 2 \times 24 \cos(\omega t + 30^\circ) = 48 \cos(2\pi \times 10^3 t + 30^\circ)$$

Thus,  $V_{s_1} = 48$  is greater than zener voltage  $V_z = 42$  (V)

This will enable the zener diode to limit the output

voltage at,  $V_{out} = V_z = 42$  (V)

we know that,  $R_z \parallel R_L = \frac{20 \times 20^k}{20 + 20^k} = 19.98 \Omega$

From equation 7.147 in textbook we can find the peak-to-peak ripple voltage:

$$V_r = \frac{[(V_{s_1} - 1.4) - V_z] T_{rect}}{R_s C} \times \frac{R_z \parallel R_L}{R_s + R_z \parallel R_L}$$

$$As \omega = 2\pi \times 10^3 \Rightarrow \omega_{rect} = 2\omega = 4\pi \times 10^3$$

$$\Rightarrow T_{rect} = \frac{2\pi}{\omega_{rect}} = \frac{2\pi}{4\pi \times 10^3} = \frac{1}{2 \times 10^3} = 0.5 \times 10^{-3} = 0.5 \text{ ms}$$

$$\Rightarrow V_r = \frac{[(48 - 1.4) - 42] \times (0.5 \times 10^{-3})}{50 \times 0.1 \times 10^{-3}} \times \frac{19.98}{50 + 19.98}$$

$$\Rightarrow V_r = 0.1313 \text{ (V)} \quad (\text{peak-to-peak})$$