

EE101 Final Examination, 4-7 p.m. March 20, 2018

Name _____ Student ID _____

2 pages of formulas and tables only are allowed. But, you must show all your work even when you apply formulas to get full credits. Otherwise, you will lose points.

Problem 1 [10] _____

Problem 2 [5] _____

Problem 3 [10] _____

Problem 4 [10] _____

Problem 5 [10] _____

Problem 6 [10] _____

Problem 7 [10] _____

Problem 8 [5] _____

Problem 9 [5] _____


Problem 10[10] _____

Problem 11[5] _____

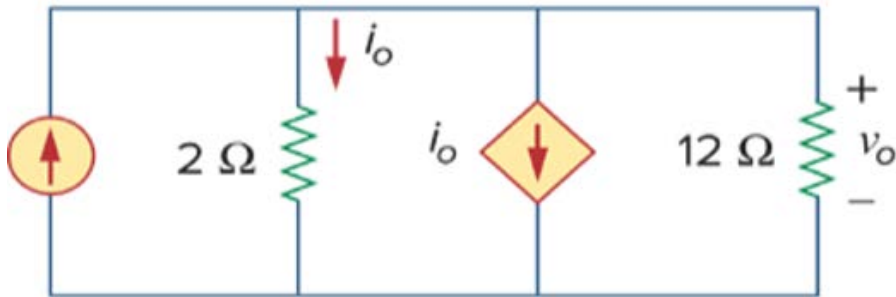
Problem 12[10] _____

TOTAL [100] _____


[1] (10 points) Find **the current i_o and voltage v_o** for a current source of 13 A.



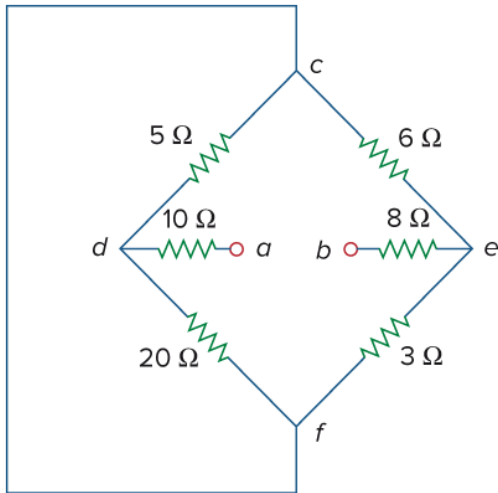
[2] (5 points) Find the equivalent resistance between **terminal a** and **terminal b**.



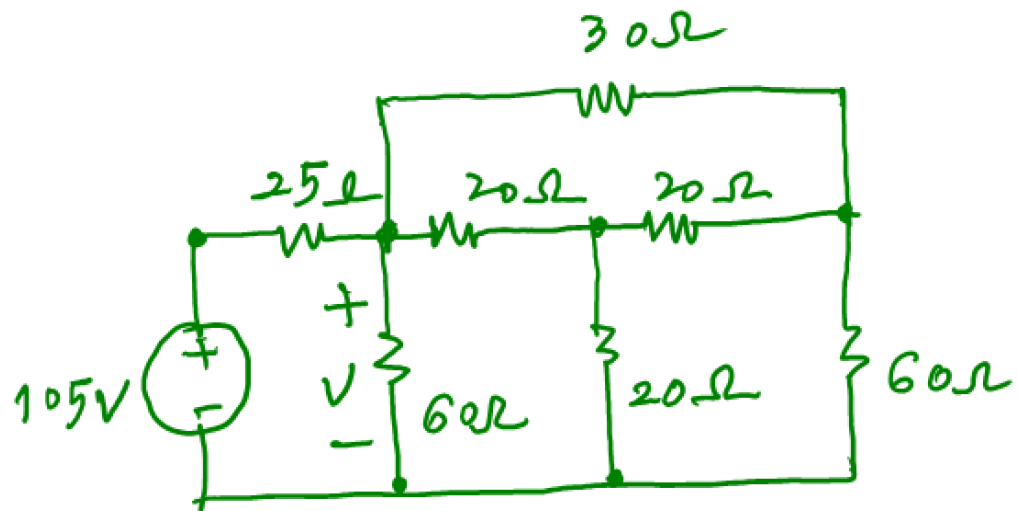[3] (10 points) Calculate **the voltage V** in the circuit below.



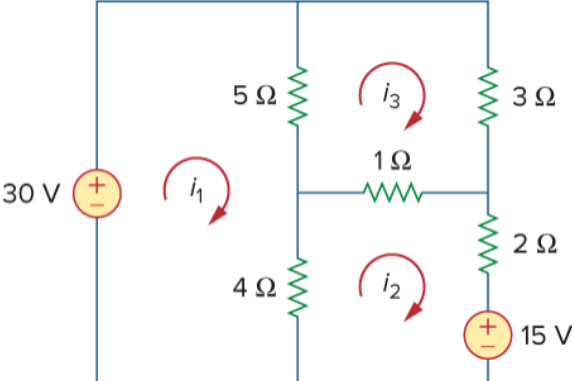
[4] (10 points) Find the mesh current i_1 .




(for continuation of problem 4 solution)

[5] (10 points) (a). (8 points) Find an **expression for V_o** in terms of $V_1, V_2,$ and V_3 .

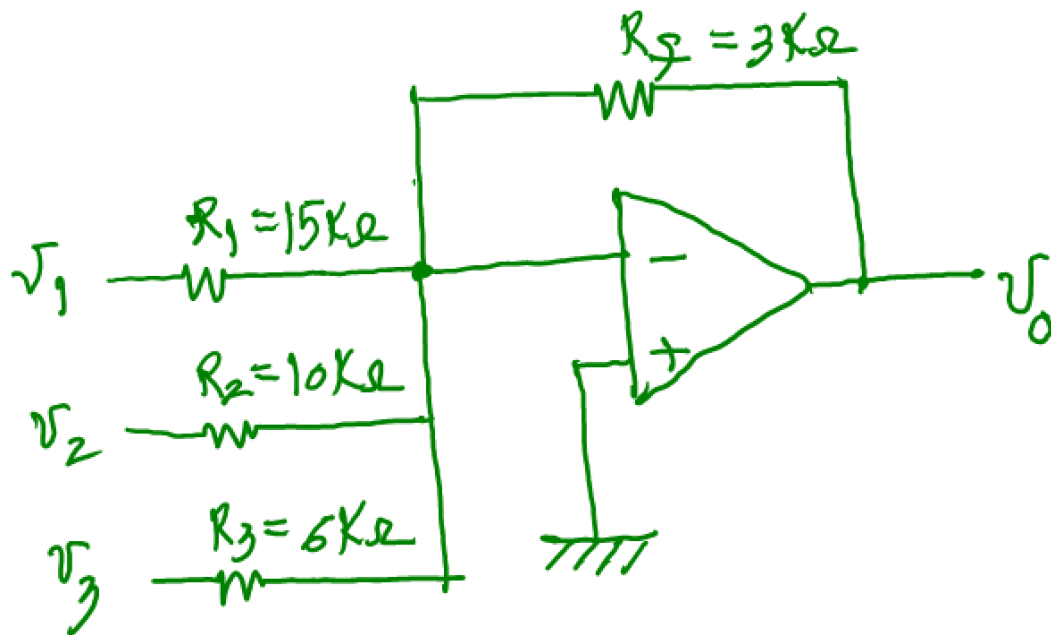(b). (2 points) What is **the value of V_o** when $(V_1, V_2, V_3) = (75, 80, 90)$?




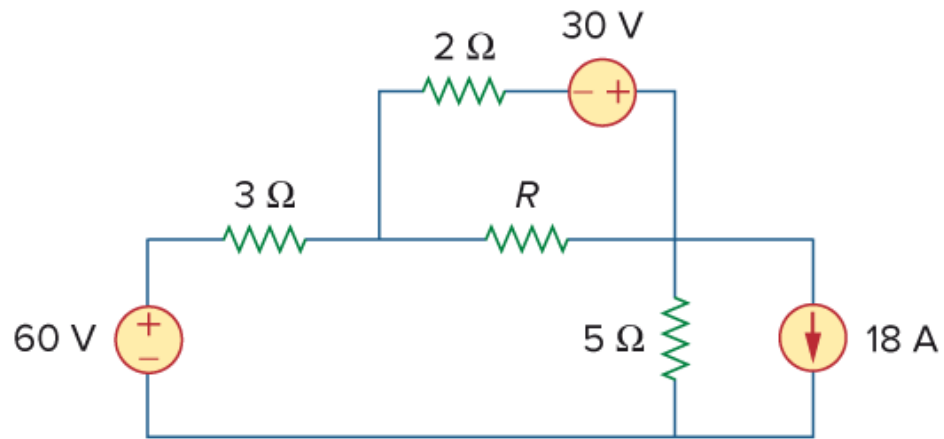[6] (10 points) Find the maximum power that can be transferred to resistor **R** in the circuit below and **find its maximum power dissipation**.




(continuation of problem 6 solution)

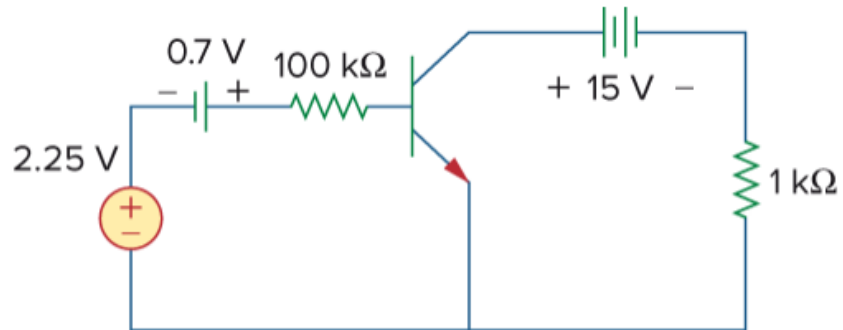[7] (10 points) Find the voltage across the collector and emitter terminals (V_{CE}) of the bipolar junction transistor (BJT) below with $\beta=100$ and $V_{BE}=0.7$ V for the circuit below.




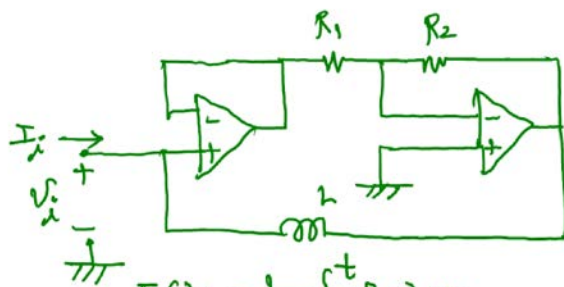[8] (5 points) Find an **expression** for L_{eq} in terms of R_1 , R_2 and L .




$$I_i(t) = \frac{1}{R_{eq}} \int_{-\infty}^t v_i(t) dt$$

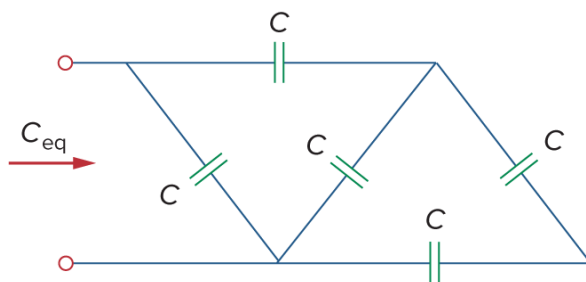[9] (5 points) Find C_{eq} of the following capacitor network.




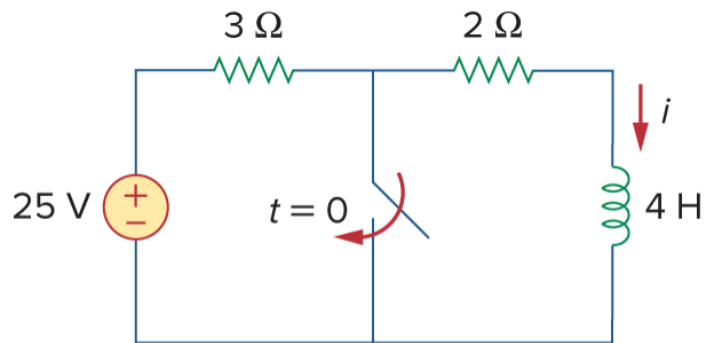[10] (5 points) Find the inductor current $i(t)$ and $\frac{di(t)}{dt}$ for $t = 0^-$ and for $t = 0^+$.




[11] (5 points) Determine **the transformer ratio n** for maximum power transfer to the $8\ \Omega$ load when the Thevenin's equivalent voltage and the equivalent resistance for the amplifier circuit are 10V and $128\ \Omega$. Assume that the transformer is an **ideal transformer** which is lossless, unity coupled and its self-inductances of the primary and secondary ports are infinitely large.

(Hint: $V_2 = n V_1$ and $I_2 = I_1/n$)

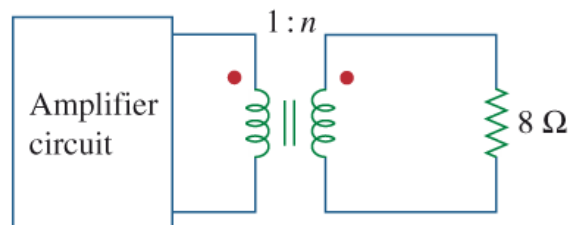

[12] (10 points) Find the voltage across 1F capacitor $v(t)$ for $t > 0$.

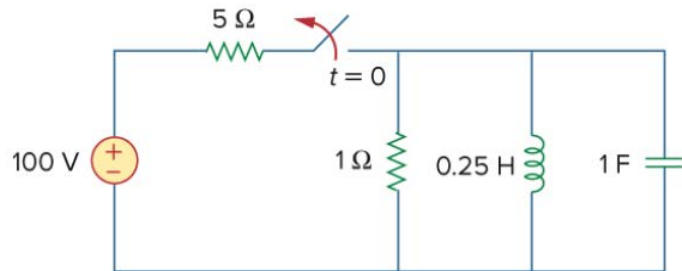(Hint: determine for $t > 0$ whether the circuit is overdamped, critically damped or underdamped so that you can start solving for $v(t)$ with a particular equation form.)



(Prob. 12 solution continued)