

Solution


EE101 Winter 2019 Quiz #3

January 29, 2019

Name _____ Student ID _____

This Problem consists of two parts, Part A and Part B in solving for I_x .

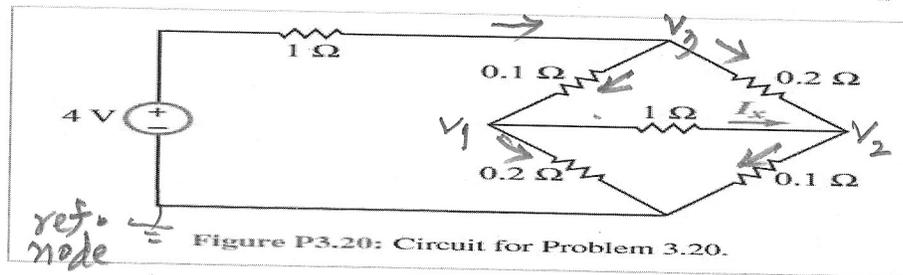*3.20 For the circuit in Fig. P3.20, determine the current I_x .



Part A (4 points) Let us solve for I_x as $I_x = \frac{V_1 - V_2}{1\Omega}$, where the two voltages are node voltages at both ends of the 1Ω resistor through which I_x flows. Write down two KCL equations to solve for V_1, V_2 .

$$\text{KCL node 3: } \frac{4 - V_3}{1} = \frac{V_3 - V_1}{0.1} + \frac{V_3 - V_2}{0.2}$$

$$\Rightarrow 4 - V_3 = 10V_3 - 10V_1 + 5V_3 - 5V_2$$

$$\underline{4 = -10V_1 - 5V_2 + 16V_3} \quad (1)$$

$$\text{node 1: } \frac{V_3 - V_1}{0.1} = \frac{V_1 - V_2}{1} + \frac{V_1}{0.2}$$

$$10V_3 - 10V_1 = V_1 - V_2 + 5V_1$$

$$\Rightarrow \underline{16V_1 - V_2 - 10V_3 = 0} \quad (2)$$

$$\text{node 2: } \frac{V_1 - V_2}{1} + \frac{V_3 - V_2}{0.2} = \frac{V_2}{0.1}$$

$$V_1 - V_2 + 5V_3 - 5V_2 - 10V_2 = 0$$

$$\underline{V_1 - 16V_2 + 5V_3 = 0} \quad (3)$$

(continued)

Part B (6 points) Solve for V_1 , V_2 and then I_x .

We want to remove V_3 first

From (2) & (3), (2) + 2x(3) \Rightarrow

$$\begin{array}{r} 18V_1 - V_2 - 10V_3 = 0 \\ 2V_1 - 32V_2 + 10V_3 = 0 \\ \hline 18V_1 - 33V_2 = 0 \end{array} \quad (4)$$

From (1) & (3), (1) x 5 - (3) x 16 \Rightarrow

$$\begin{array}{r} 20 = -50V_1 - 25V_2 + 80V_3 \\ \rightarrow 0 = 16V_1 - 256V_2 + 80V_3 \\ \hline 20 = -66V_1 + 231V_2 \end{array} \quad (5)$$

From (4) & (5)

(4) x 11 + (5) x 3

$$\begin{array}{r} 18 \times 11 V_1 - 33 \times 11 V_2 = 0 \\ -66 \times 3 V_1 + 231 \times 3 V_2 = 60 \\ \hline 0 \quad (693 - 363) V_2 = 60 \end{array} \quad V_2 = \frac{60}{330} = \frac{2}{11} [V]$$

$V_2 \rightarrow$ (4)

$$18V_1 - 33 \frac{66}{330} = 0$$

$$18V_1 = 6$$

$$V_1 = \frac{6}{18} = \frac{1}{3} [V]$$

$$V_1 - V_2 = \frac{1}{3} - \frac{2}{11} = \frac{11 - 6}{33} = \frac{5}{33} [V]$$

$$I_x = \frac{V_1 - V_2}{1 \Omega} = \frac{5}{33} [A]$$

Ans

Ans