

Solution

EE101 Quiz 6 February 19, 2019

Name _____ Student ID No. _____

Problem (10 points)

- 5.16 Determine the voltages across the two capacitors in the circuit of Fig. P5.16 under dc conditions.


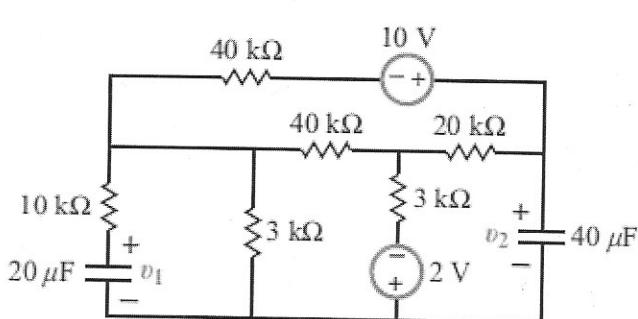


Figure P5.16: Circuit for Problem 5.16.

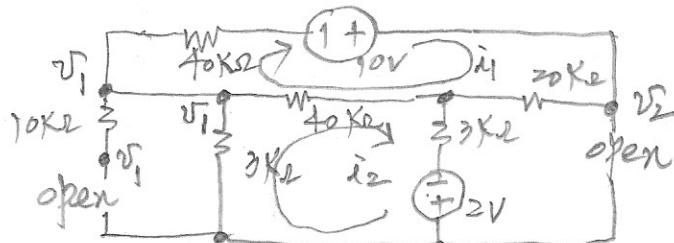Part 1 (2 points) Draw a simplified circuit diagram under dc conditions.



Part 2 (8 points) Use mesh analysis to find branch currents from which you can find v_1 and v_2 .

Part 2a (4 points) Write down two equations using KVL

$$\text{Mesh 1: } -10 + i_1 \cdot 20\text{k} + (i_1 - i_2)40\text{k} + i_1 \cdot 40\text{k} = 0 \\ \Rightarrow [100\text{k} \cdot i_1 - 40\text{k} \cdot i_2 = 10] \quad (1)$$

$$\text{Mesh 2: } 3\text{k} \cdot i_2 + 40\text{k}(i_2 - i_1) + 3\text{k} \cdot i_2 - 2 = 0 \\ \Rightarrow [-40\text{k} \cdot i_1 + 46\text{k} \cdot i_2 = 2] \quad (2)$$

Part 2b (4 points) Solve for two mesh currents, and then find v_1 and v_2 .

$$(1) + 2.5 \times (2) \Rightarrow 100\text{k} i_1 - 40\text{k} i_2 = 10 \\ -100\text{k} i_1 + 115\text{k} i_2 = 5$$

$$65\text{k} + (115 - 40)\text{k} i_2 = 15$$

$$i_2 = \frac{15}{75} \times 10^{-3} = 0.2 \text{ mA}$$

$$\text{From (1) & } i_2 = 0.2, \quad 100\text{k} i_1 - 40\text{k}(0.2 \text{ mA}) = 10$$

$$i_1 = \frac{10}{100\text{k}} = 0.18 \text{ mA}$$

$$v_1 = -3\text{k}(i_2) = -0.6 \text{ V}$$

$$v_2 = 3\text{k} \cdot i_2 - 2 + 20\text{k} \cdot i_1 = 0.6 - 2 + 3.6 = 2.2 \text{ V}$$