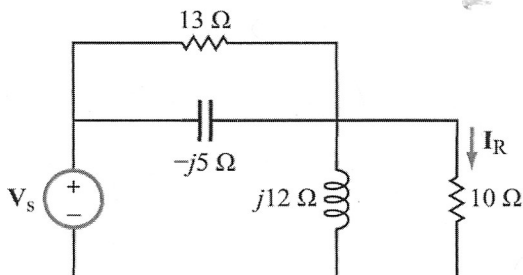


solution

EE101 Quiz 9, March 12, 2019

Name _____ Student ID Number _____

Consider the following phasor domain circuit.



Part A (2 points) Find a phasor representation for $v_s = 25 \sin \omega t$.

(Answer) $V_s = 25 e^{-j90^\circ} = -j25$ $v_s = 25 \sin \omega t = 25 \cos(\omega t - 90^\circ)$
 $V_s = 25 e^{-j90^\circ} = -j25$

Part B (5 points) Find I_R

(Answer) $I_R =$ _____

Show your detailed calculations.

$$I_R = I_s \frac{j12}{10 + j12}$$

$$= -j25 \frac{(13-j5)(5+j6)}{690 + j455} \frac{j6}{(5+j6)}$$

$$= 150 \frac{13-j5}{690 + j455} = 150 \frac{13.93 e^{-j21.1^\circ}}{826.51 e^{j33.4^\circ}}$$

$$= 2.53 e^{-j54.3^\circ}$$

$$Z = \frac{13(-j5)}{13-j5} + \frac{j12}{10+j12}$$

$$= \frac{-j65(5+j6) + j60(13-j5)}{(13-j5)(5+j6)}$$

$$= \frac{690 + j455}{(13-j5)(5+j6)}$$

$$I_s = V_s / Z = -j25 \frac{(13-j5)(5+j6)}{690 + j455}$$

Part C (3 points) Express $i_R(t)$ as $A \sin(\omega t + \theta)$

(Answer) $i_R(t) = 2.53 \cos(\omega t - 54.3^\circ) = 2.53 \sin(\omega t - 54.3^\circ + 90^\circ)$
 $= 2.53 \sin(\omega t + 35.7^\circ)$
ans